

## Tutorial Sheet 2 (Transient)

1. The switch in the circuit of Fig.1 is closed at  $t = 0$ . Before that the circuit was in steady state. Assuming that the inductance is ideal, find the current through the inductor at  $t = 10$  s.

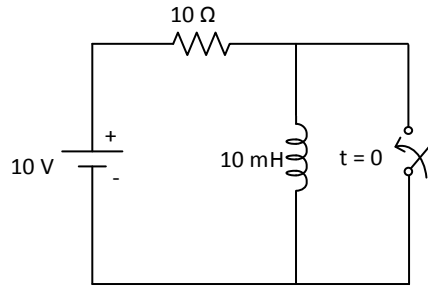


Fig. 1

2. The switch in Fig.2 was in open condition for a long time and closed at time  $t = 0$ . Find current  $i_{AB}$  as function of time thereafter.

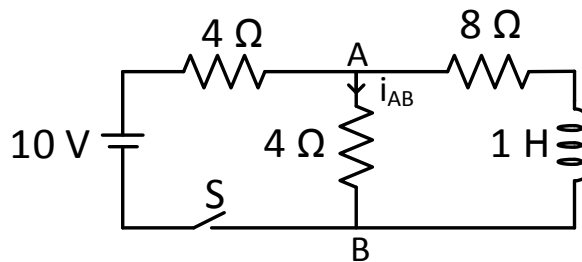


Fig. 2

3. The circuit in Fig.3 was in steady-state for  $t < 0$ , and the switch is opened at  $t = 0$ . Find the voltage  $V_x$  at  $t = 100 \mu\text{s}$ .

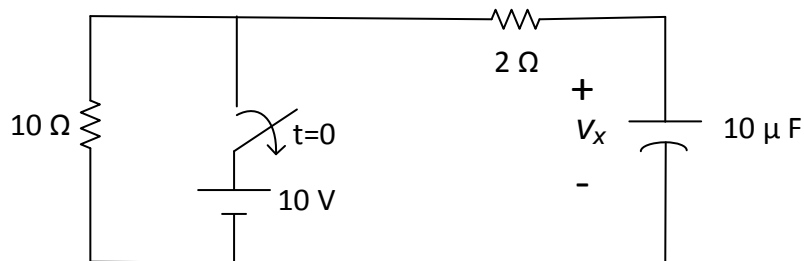


Fig. 3

4. The circuit in Fig.4 was in steady-state for  $t < 0$ , and the switch is closed at  $t = 0$ . Find the values of  $i_L$ ,  $i_1$  and  $i_2$  at  $t = 20$  sec.

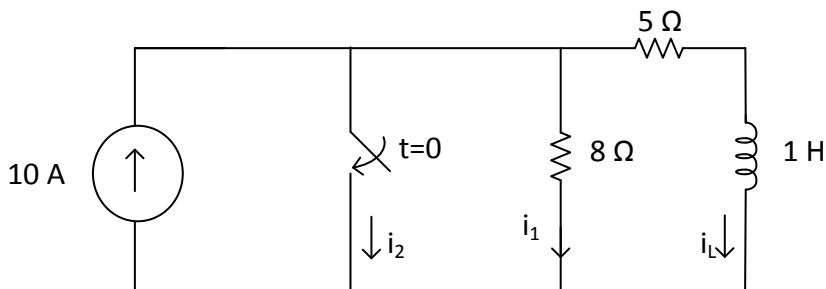


Fig. 4

5. The circuit in Fig.5 was in steady-state for  $t < 0$ , and the position of the switch is changed at  $t = 0$ . Find the capacitor voltage  $V_c(t)$  and the current  $i(t)$  in the  $100\ \Omega$  resistor for all time.

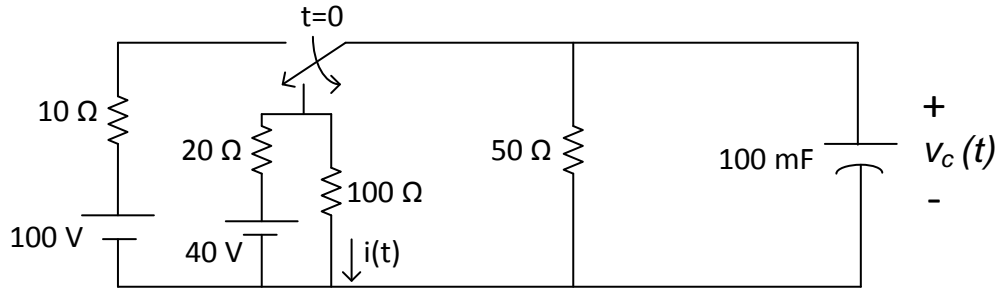


Fig. 5

6. In the circuit of Fig.6, the switch was open and the circuit was operating at steady state. At  $t=0$ , the switch is closed. Derive the expression for inductor current  $i(t)$  for  $t > 0$ .

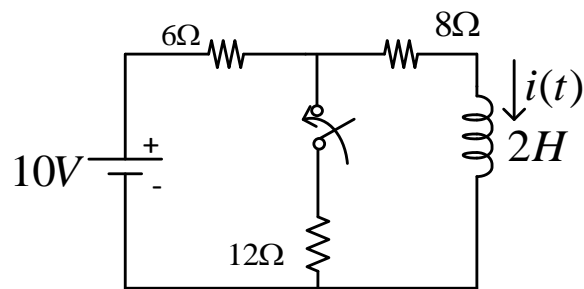


Fig. 6

7. In the circuit of Fig.7, the switch was open and the circuit was operating at steady state. At  $t=0$ , the switch is closed. Obtain the expression for inductor current  $I_L(t)$  for  $t > 0$ .

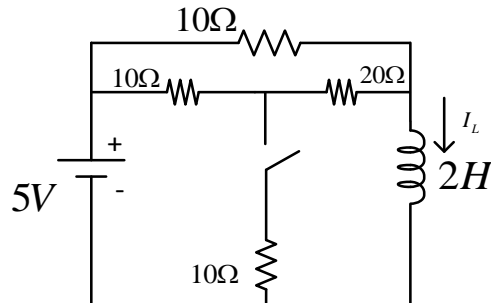


Fig. 7

8. The circuit in Fig.8 was in steady state and the switch  $S$  was open. At  $t=0$ , and the switch is closed. Find the expression of the current  $i(t)$  through the inductor of  $2\text{ H}$  for  $t > 0$ .

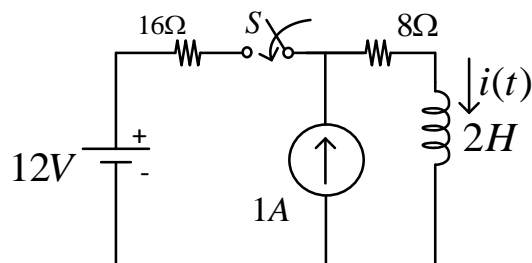


Fig. 8

9. The circuit in Fig.9 was in steady state and the switch S was open. At  $t=0$ , and the switch is closed. Find the expression of the current  $i_c(t)$  through the capacitor for  $t>0$ .

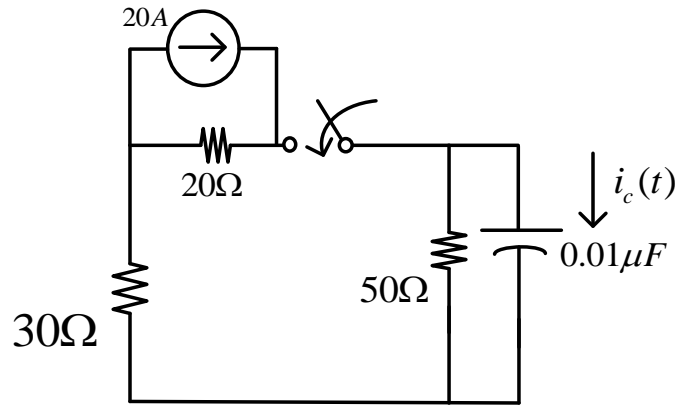


Fig. 9

10. The network in Fig.10 was at steady-state and the switch was open. Obtain the expression of the current  $i(t)$  for  $t>0$  when an AC voltage source  $v(t) = V \sin \omega t$  is connected at  $t=0$ .

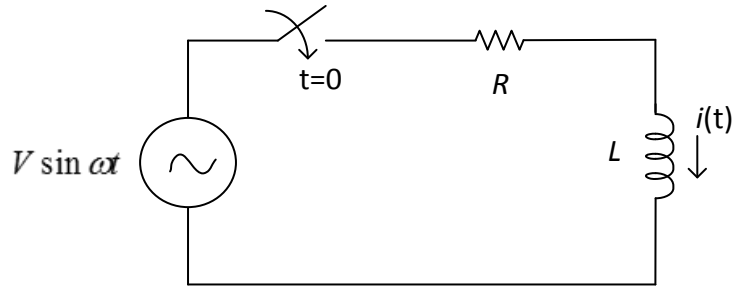


Fig. 10

11. In the circuit shown in Fig.11, assume that, initially the switch is not connected to either A or B terminal and the capacitor voltage is zero. At  $t=0$  sec, the switch is connected to A terminal. Then, at  $t=1$ s, the switch is disconnected from A terminal and connected to B terminal. Calculate  $V_C(0+)$ ,  $\frac{dV_C(0+)}{dt}$ ,  $V_C(1-)$ ,  $\frac{dV_C(1-)}{dt}$  and  $V_C(1+)$ ,  $\frac{dV_C(1+)}{dt}$  and  $V_C(+\infty)$ . Also, calculate the value of  $V_C(t)$  at 2s.

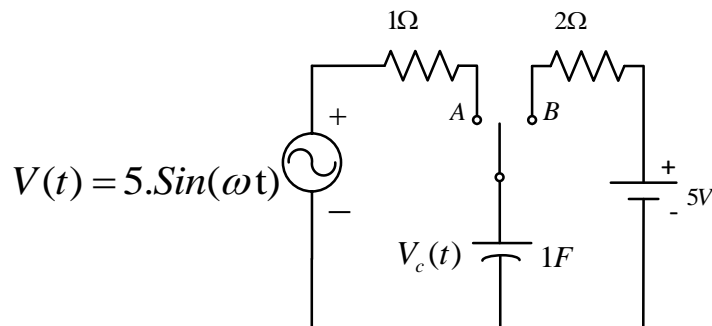


Fig. 11