

$$\therefore v_{TH} = 20i_2 + 40i_1 = 100i_2 = 100 \times \frac{18}{65} \text{ Volt}$$

(45)

$$\therefore v_{TH} = \frac{360}{13} \text{ Volt.}$$

From Fig. 4.50(b),

$$R_{TH} = (40 \parallel 50 + 20) \parallel 30 = \frac{228}{13} \Omega$$

Current through 10Ω resistor,

$$i = \frac{v_{TH}}{R_{TH} + 10} = \frac{360/13}{\left(\frac{228}{13} + 10\right)} = \frac{360}{358} \text{ Amp.}$$

EX-4.20: Obtain the current in 2Ω resistor of the circuit shown in Fig. 4.51. Use Thevenin's theorem.

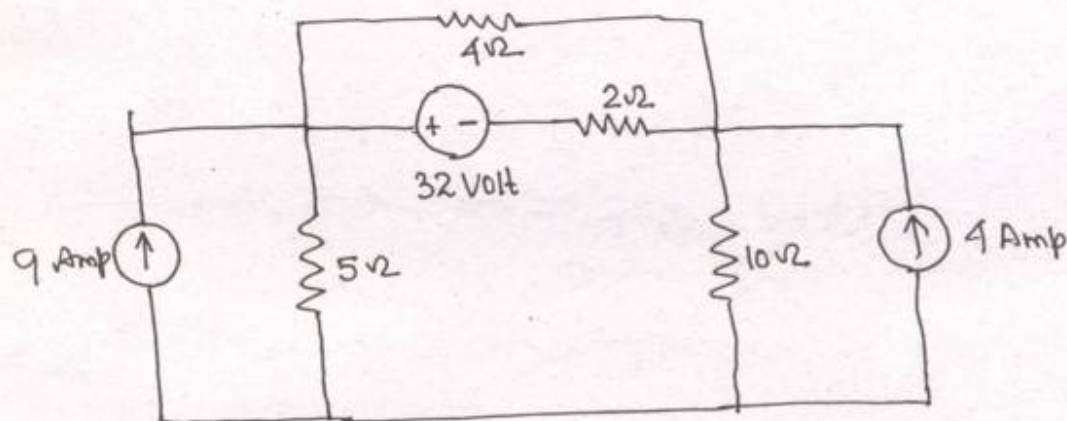


Fig. 4.51: Circuit for EX-4.20

Soln.

2Ω resistor is removed from Fig. 4.51 and the resulting circuit is shown in Fig. 4.52 to determine v_{TH} .

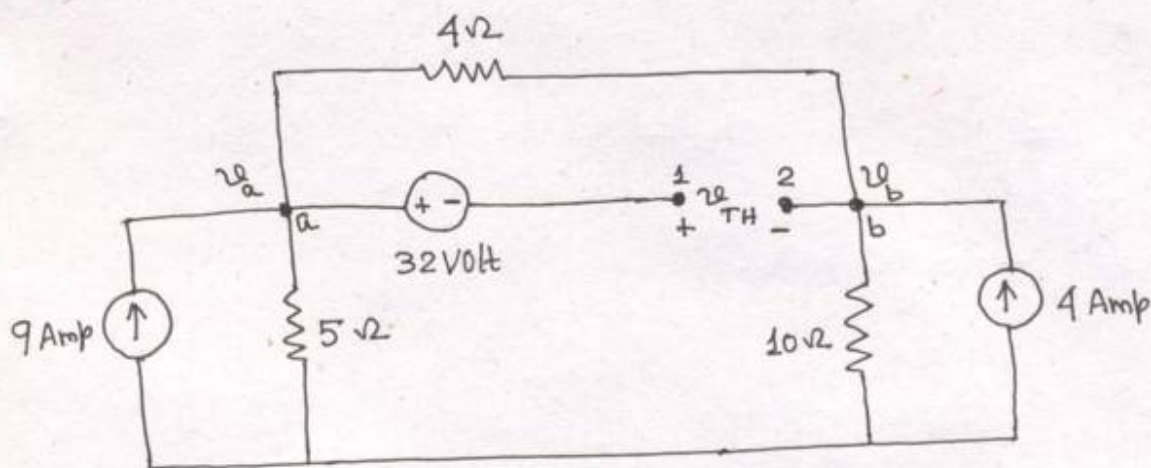


Fig. 4.52: Finding V_{TH} for EX-4.20

At ~~node~~ node a,

$$\frac{V_a}{5} + \frac{V_a - V_b}{4} = 9 \quad \text{--- (i)}$$

At node b

$$\frac{V_a - V_b}{4} + 4 = \frac{V_b}{10} \quad \text{--- (ii)}$$

Solving eqns. (i) and (ii), we get,

$$V_a = \frac{830}{19} \text{ Volt}; \quad V_b = \frac{810}{19} \text{ Volt.}$$

Thus,

$$V_a - V_b - V_{TH} - 32 = 0$$

$$\therefore V_{TH} = \frac{830}{19} - \frac{810}{19} - 32 = -30.947 \text{ Volt.}$$

For determining R_{TH} , resulting circuit is shown in Fig. 4.53.

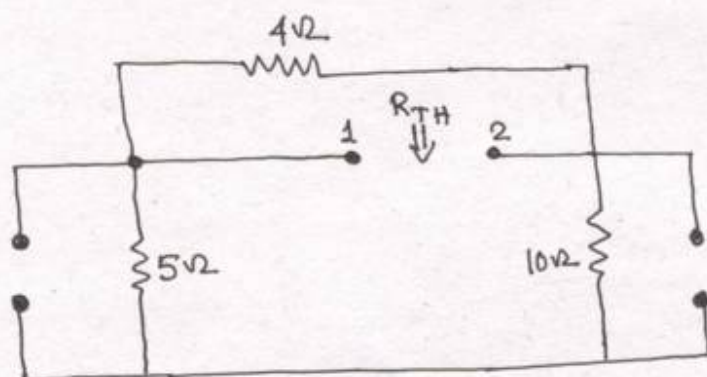


Fig. 4.53: Finding R_{TH} for EX-4.20

From Fig. 4.53, we have,

(47)

$$R_{TH} = \frac{(10+5) \times 4}{(10+5) + 4} = \frac{60}{19} \Omega$$

Thevenin equivalent circuit is shown in Fig. 4.54


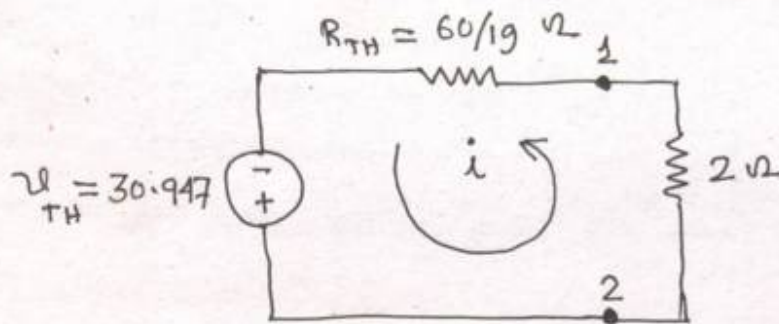


Fig. 4.54: Thevenin equivalent circuit for Ex-4.20


$$\therefore i = \frac{V_{TH}}{R_{TH} + 2} = \frac{30.947}{\left(\frac{60}{19} + 2\right)} = 6 \text{ Amp.}$$

Ex-4.21 : Obtain the Thevenin voltage shown in the circuit of Fig. 4.51 - for Ex-4.20

Soln.

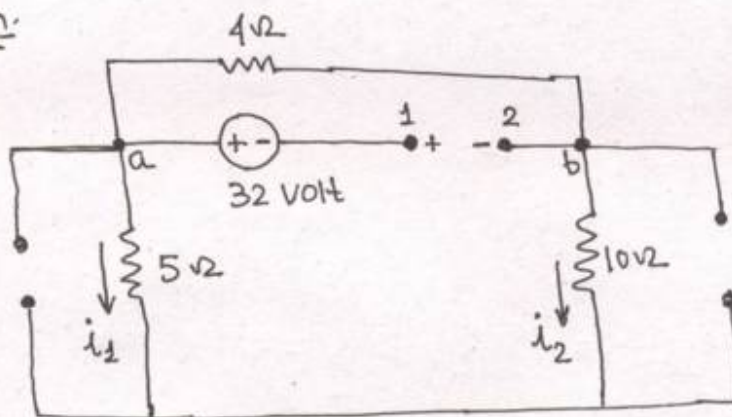

(a)

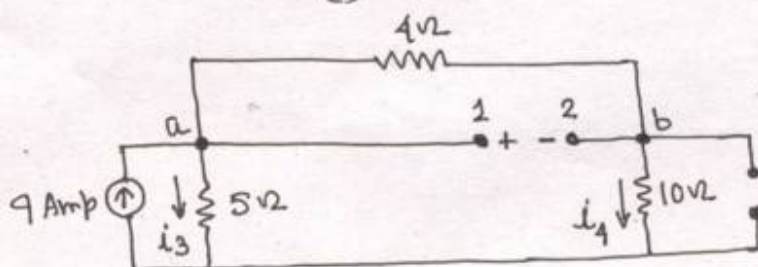

(b)

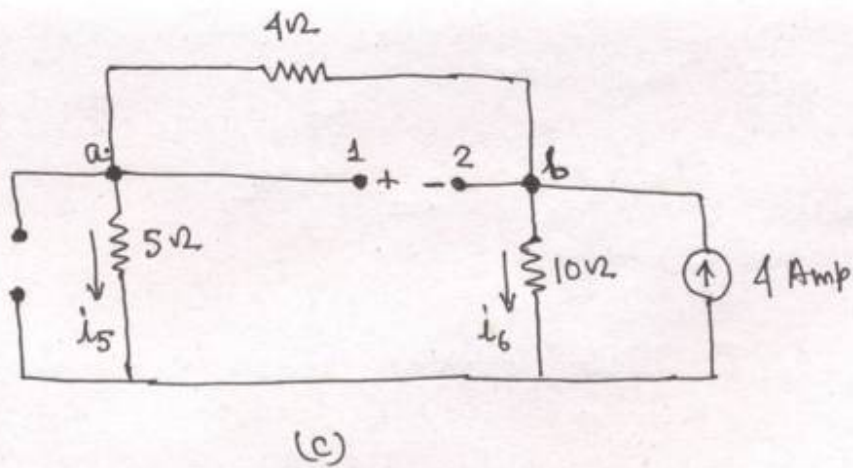


Fig. 4.55: (a) Two independent current sources are turned off
 (b) Voltage source and 4 Amp current sources are turned off
 (c) Voltage source and 9 Amp current source are turned off.

~~Fig. 4.55~~ Fig. 4.55 gives three different circuits for obtaining V_{TH} using superposition theorem.

From Fig. 4.55(a),

$$i_1 = 0.0; \quad i_2 = 0.0$$

From Fig. 4.55(b),

$$i_3 = \left(\frac{10 + 4}{10 + 4 + 5} \right) \times 9 = 6.63 \text{ Amp}; \quad i_4 = 9 - i_3 = 9 - 6.63 = 2.37 \text{ Amp}$$

From Fig. 4.55(c),

$$i_5 = \frac{10}{(10 + 5 + 4)} \times 4 = 2.11 \text{ Amp}; \quad i_6 = 4 - 2.11 = 1.89 \text{ Amp}$$

$$\therefore i_{5\Omega} = i_1 + i_3 + i_5 = 0 + 6.63 + 2.11 = 8.74 \text{ Amp}$$

$$i_{10\Omega} = i_2 + i_4 + i_6 = 0 + 2.37 + 1.89 = 4.26 \text{ Amp}$$

$$\therefore V_a = 5 \times i_{5\Omega} = 5 \times 8.74 = 43.7 \text{ Volt}$$

$$V_b = 10 \times i_{10\Omega} = 10 \times 4.26 = 42.6 \text{ Volt}$$

Thus

$$V_{TH} = V_a - V_b - 32 = 43.7 - 42.6 - 32 = -30.9 \text{ Volt.}$$

4.5: NORTON'S THEOREM

Norton's theorem states that a linear two terminal circuit can be replaced by an equivalent circuit consisting of a current source i_N in parallel with a resistor R_N .

where,

i_N = short circuit current through the terminals

R_N = input or equivalent resistance at the terminals when the independent sources are turned off.

consider the circuit given in Fig. 4.56(a). This circuit can be replaced by the one given in Fig. 4.56(b). We find R_N in the same way we find R_{TH} . In fact, Thevenin and Norton resistances are equal, that is

$$R_N = R_{TH} \quad \dots \quad (4.9)$$

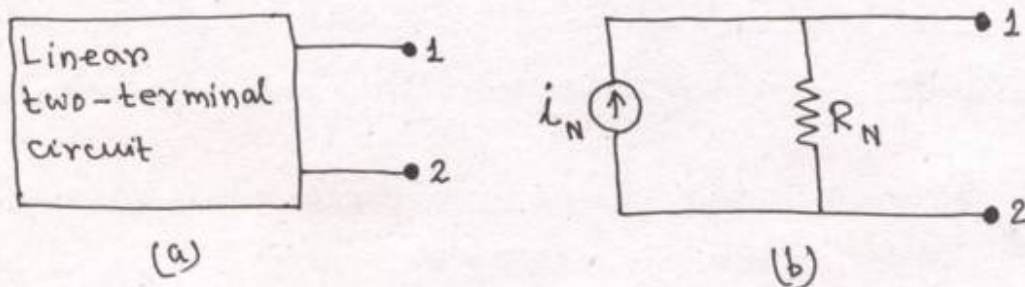


Fig. 4.56: (a) Original circuit (b) Norton equivalent circuit.

To determine the Norton current i_N , first compute the short circuit current flowing from terminal 1 to 2 in both circuits in Fig. 4.56

It is evident that the short circuit current in Fig. 4.56(b) is i_N and this must be the same short circuit current from terminal 1 to 2 in Fig. 4.56(a). Since the circuits of Fig. 4.56(a) and Fig. 4.56(b) are equivalent, thus,

$$i_N = i_{sc} \quad \dots \quad (4.10)$$

Fig. 4.57 shows the circuit for finding Norton current i_N .

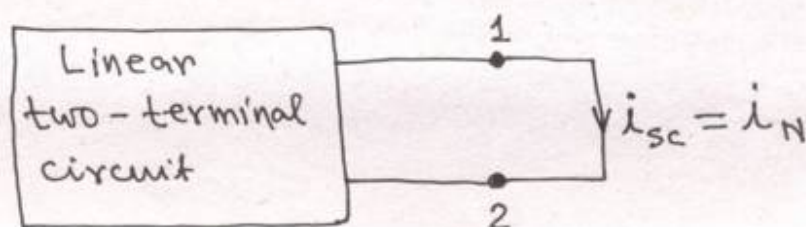


Fig. 4.57: Finding Norton current i_N

Also

$$i_N = \frac{v_{TH}}{R_{TH}} \quad \dots \quad (4.11)$$

Note that dependent and independent sources are treated the same way as in Thevenin's theorem.

The Thevenin and Norton equivalent circuits are related by a source transformation. For this reason, source transformation is often called Thevenin - Norton transformation.

To determine the Thevenin or Norton equivalent circuits require that we find:

1. The open circuit voltage v_{oc} across terminals 1 and 2.

2. The short circuit current i_{sc} at terminals 1 and 2.
3. The equivalent or input resistance R_{in} at terminals 1 and 2 when all independent sources are turned off.

We summarize the relationships:

$$V_{TH} = V_{oc} \quad \dots (4.12)$$

$$i_N = i_{sc} \quad \dots (4.13)$$

$$R_{TH} = \frac{V_{oc}}{i_{sc}} = R_N \quad \dots (4.14)$$

Open circuit and short circuit tests are sufficient to find any Thevenin or Norton equivalent.

Ex-4.22: Determine Norton equivalent circuit of the circuit shown in Fig.4.58



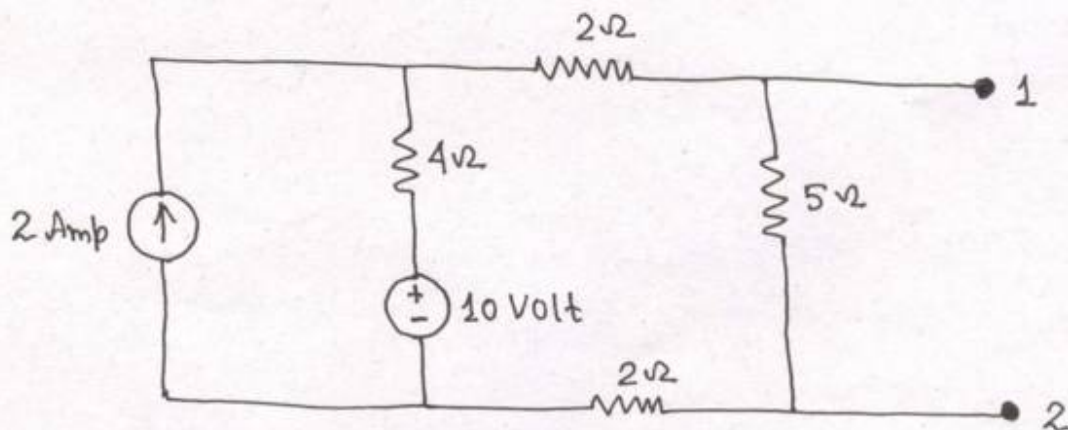



Fig.4.58: Circuit for Ex-4.22.

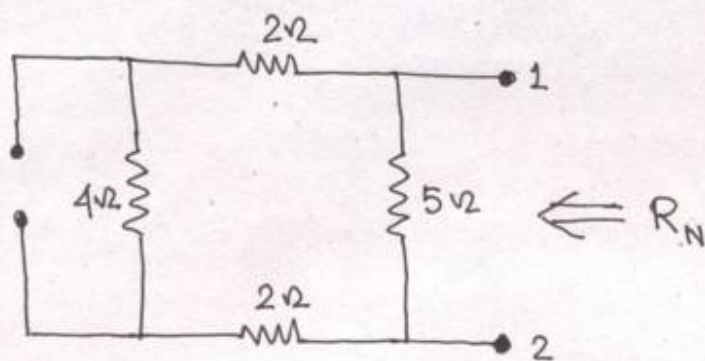

(a)

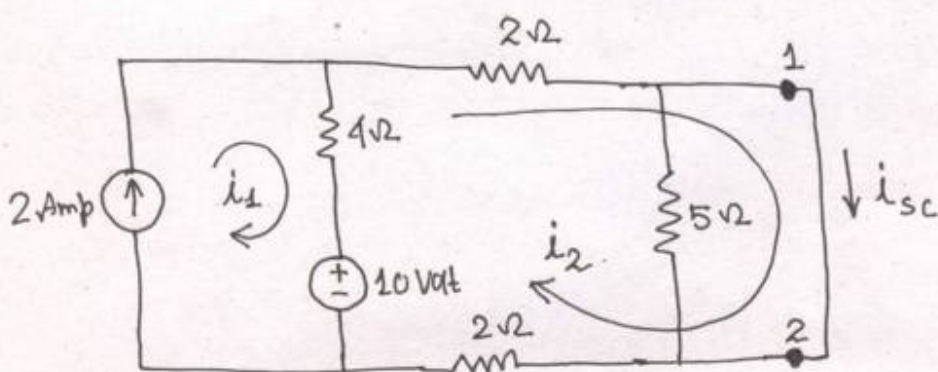

(b)

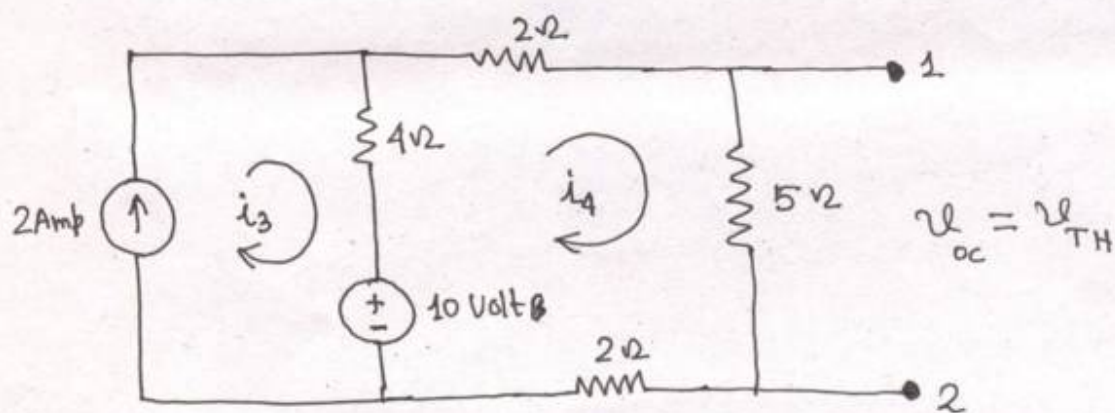

(c)

Fig. 4.59: (a) finding R_N (b) finding $i_N = i_{sc}$

(c) finding $V_{oc} = V_{TH}$

We determine R_N in the same way we find R_{TH} in the Thevenin equivalent circuit. All the independent sources are turned off and this leads to the circuit in Fig. 4.59(a). Thus

$$R_N = \frac{5 \times (2 + 4 + 2)}{5 + (2 + 4 + 2)} = 3.077\Omega = R_{TH}$$

To determine i_N , terminals 1 and 2 are short circuited - as shown in Fig. 4.59(b). $5\ \Omega$ resistor is ignored because it has been short circuited.

Applying mesh analysis, we get,

$$i_1 = 2\text{ Amp and } 8i_2 - 4i_1 = 10$$

$$\therefore 8i_2 = 4 \times 2 + 10 \quad \therefore i_2 = 2.25\text{ Amp.}$$

$$\therefore i_{sc} = i_2 = 2.25\text{ Amp.}$$

Alternatively, we can determine $i_N = \mathcal{V}_{TH} / R_{TH}$.

We obtain \mathcal{V}_{TH} as the open circuit voltage across terminals 1 and 2 in Fig. 4.59(c). Using mesh analysis, we obtain,

$$i_3 = 2\text{ Amp;}$$

$$13i_4 - 4i_3 = 10 \quad \therefore 13i_4 = 4 \times 2 + 10$$

$$\therefore i_4 = 1.384\text{ Amp.}$$

$$\therefore \mathcal{V}_{TH} = \mathcal{V}_{oc} = 5i_4 = 5 \times 1.384 = 6.923\text{ Volt.}$$

Hence,

$$i_N = \frac{\mathcal{V}_{TH}}{R_{TH}} = \frac{6.923}{3.077} = 2.25\text{ Amp.}$$

as obtained previously.

This also serves to confirm eqn (4.14), that

$$R_{TH} = R_N = \frac{\mathcal{V}_{oc}}{i_{sc}} = \frac{6.923}{2.25} = 3.077\ \Omega.$$

Thevenin and Norton equivalent circuits are shown in Fig. 4.60(a) and Fig. 4.60(b) respectively.

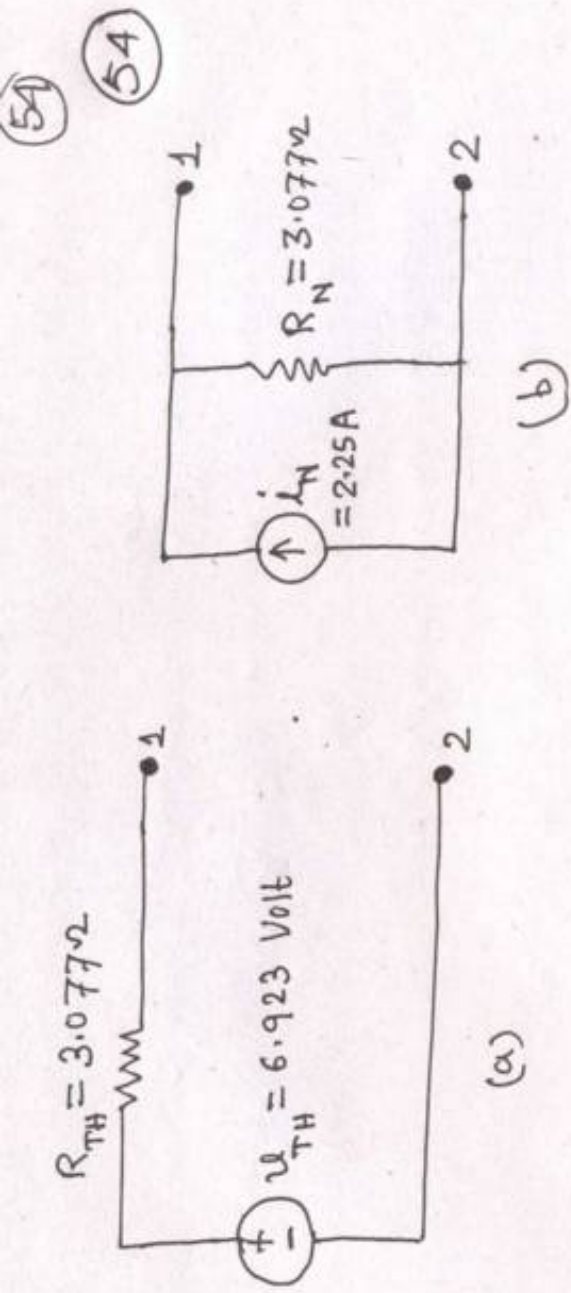


Fig. 4.60: (a) Thevenin equivalent circuit
(b) Norton equivalent circuit.

EX-4.23: Using Norton's theorem, determine R_N and I_N of the circuit shown in Fig. 4.61.

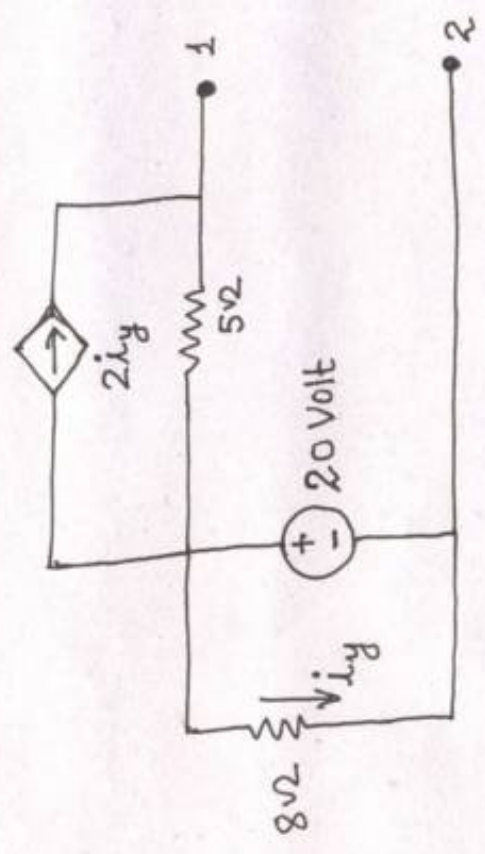


Fig. 4.61: Circuit for EX-4.23

Soln.

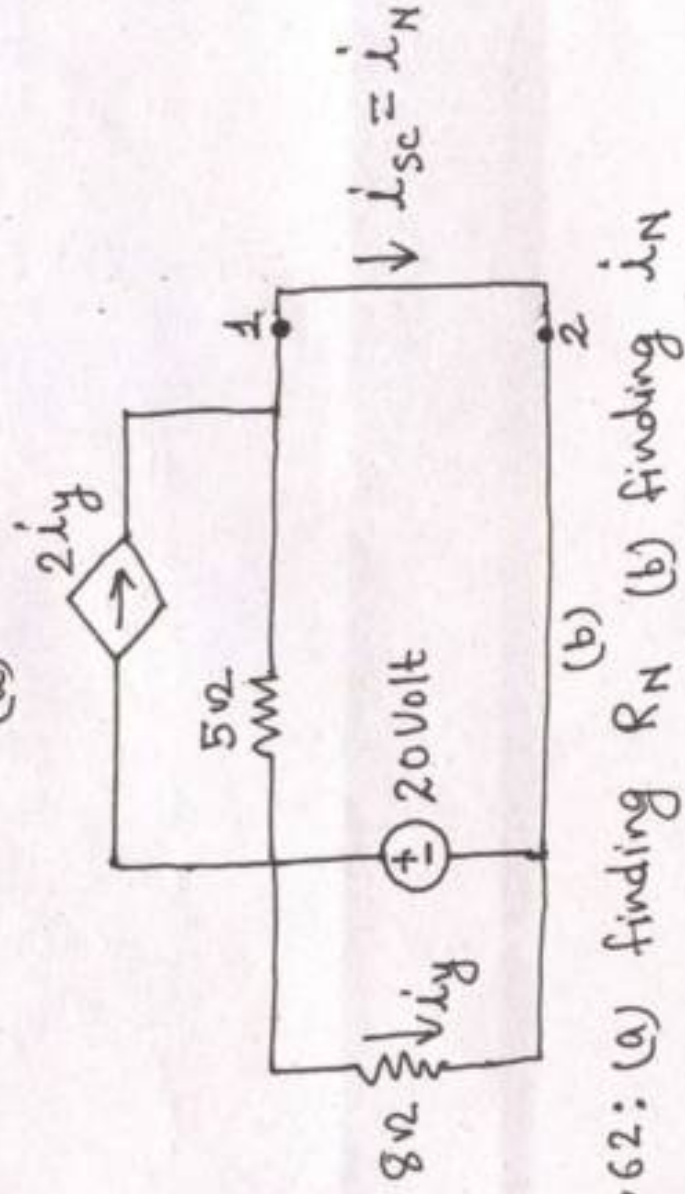
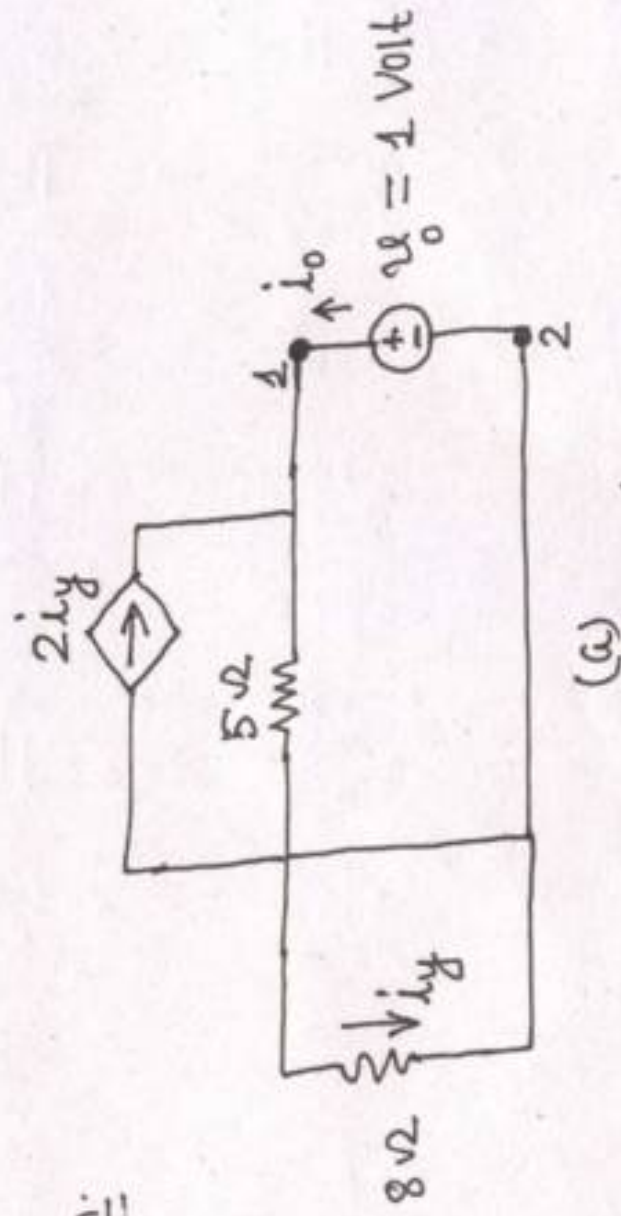


Fig. 4.62: (a) finding R_N (b) finding i_N

To find R_N , we turned off the independent voltage source and connected a voltage source of $v_o = 1$ Volt to the terminals 1 and 2 and resulting circuit is shown in Fig. 4.62(a). We ignore the 8Ω resistance of Fig. 4.62(a) because it is short circuited. Also due to the short circuit, the dependent current source, 5Ω resistor and independent voltage source are in parallel.

Hence, $i_y = 0.0$. ~~At node 1,~~ $i_o = \frac{v_o}{5}$

At node 1,

$$i_o = \frac{v_o}{5} = \frac{1}{5} \text{ Amp.}$$

and

$$R_N = \frac{v_o}{i_o} = \frac{1}{(1/5)} = 5\Omega.$$

To determine i_N , terminals 1 and 2 are short circuited and the resulting circuit is shown in Fig. 4.62(b). In Fig. 4.62(b), dependent current source, 5Ω resistor, 20 Volt and 8Ω resistor all are in parallel. Hence,

$$i_y = \frac{20}{8} = 2.5 \text{ Amp;}$$

At node 1, KCL gives

$$i_{sc} = \frac{20}{5} + 2i_y = 4 + 2 \times 2.5 = 9 \text{ Amp.}$$

Thus,

$$i_N = i_{sc} = 9 \text{ Amp.}$$

Ex-4.24: Determine the current in 10Ω resistor of the circuit shown in Fig. 4.63 by Norton's theorem.



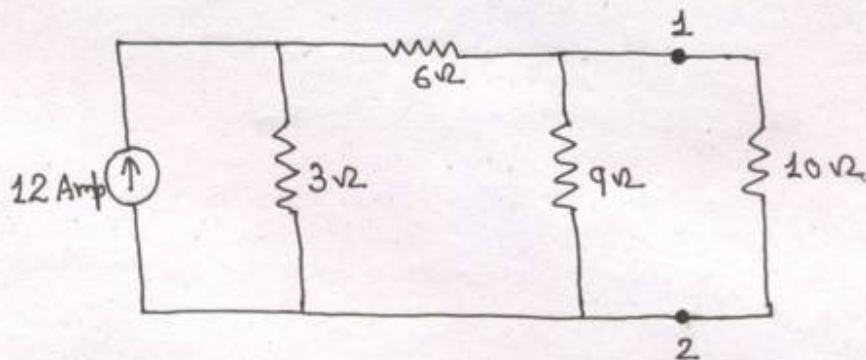


Fig. 4.63: Circuit for Ex-4.24

Soln.

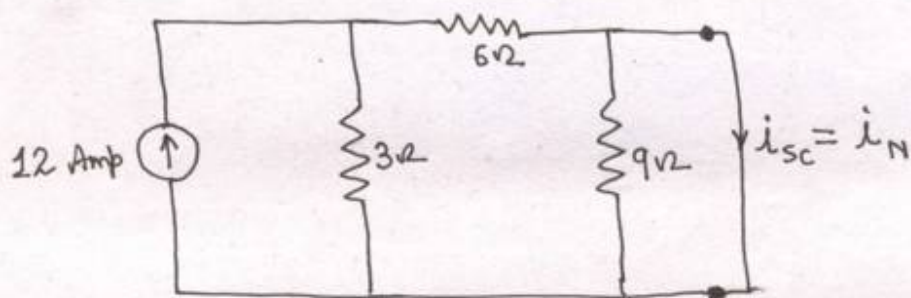

(a)

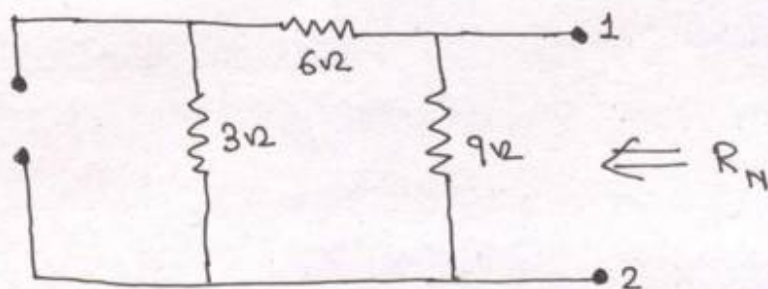

(b)

Fig. 4.64: (a) finding i_N (b) finding R_N

In Fig. 4.64(a), 9Ω resistor is short circuited.

Hence,

$$i_N = \frac{3}{(3+6)} \times 12 = 4 \text{ Amp}$$

From Fig. 4.64(b),

$$R_N = \frac{9 \times (6+3)}{9 + (6+3)} = 4.5\Omega$$

Fig. 4.65 shows Norton equivalent circuit.

(57)

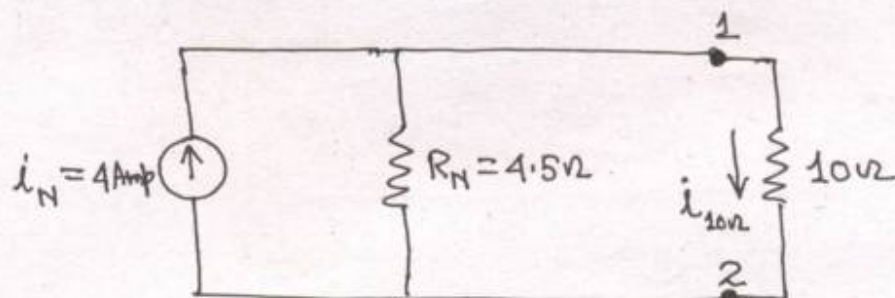


Fig. 4.65: Norton Equivalent circuit for Ex-4.24.

Current through 10 ohm resistor is given by

$$i_{10\Omega} = \frac{4.5}{(4.5 + 10)} \times 4 = 1.241 \text{ Amp.}$$

EX-4.25: Obtain the Norton equivalent circuit for the circuit shown in Fig. 4.66 to determine the current in the 50 ohm resistor.



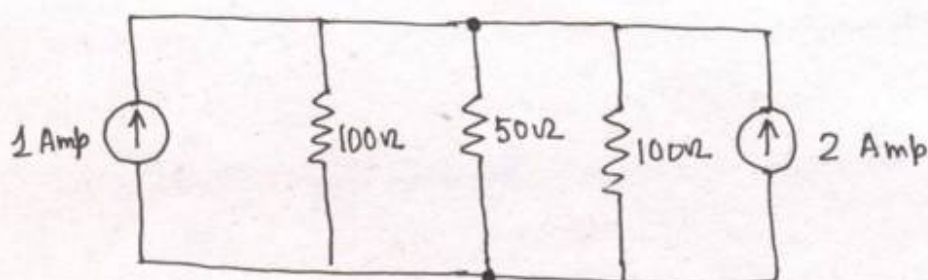


Fig. 4.66: Circuit for Ex-4.25

Soln.

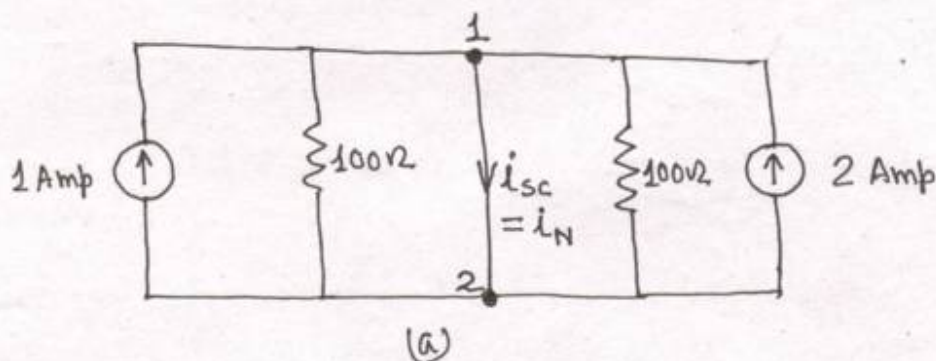

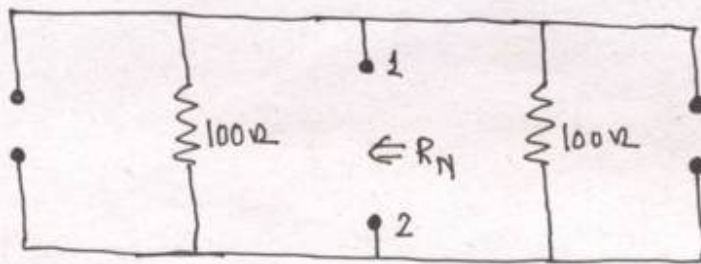

(b)

Fig. 4.67: (a) finding i_N (b) finding R_N

In Fig. 4.67(a), both 100Ω resistors are short circuited. Hence,

$$i_{sc} = i_N = 1 + 2 = 3 \text{ Amp}$$

In Fig. 4.67(b), Both 100Ω resistors are in parallel, hence,

$$R_N = \frac{100 \times 100}{100 + 100} = 50\Omega$$

Norton equivalent circuit is given in Fig. 4.68

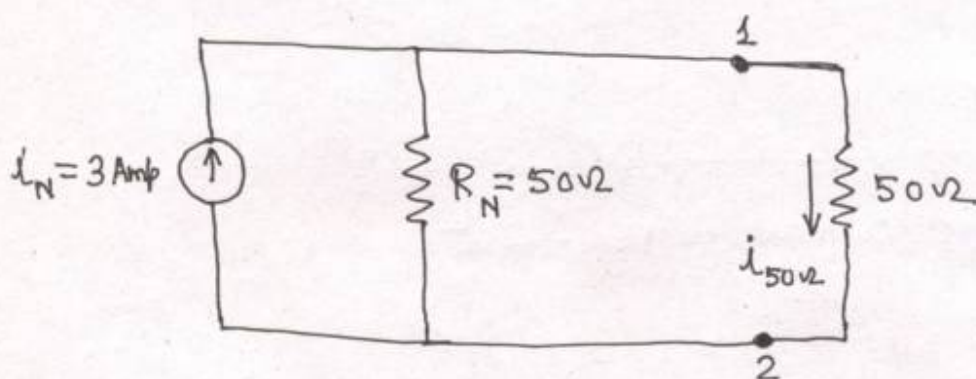


Fig. 4.68: Norton equivalent circuit for EX-4.25

$$\therefore i_{50\Omega} = 3 \times \frac{50}{50+50} = 1.5 \text{ Amp.}$$

EX-4.26: Obtain Norton equivalent circuit of the circuit shown in Fig. 4.69.



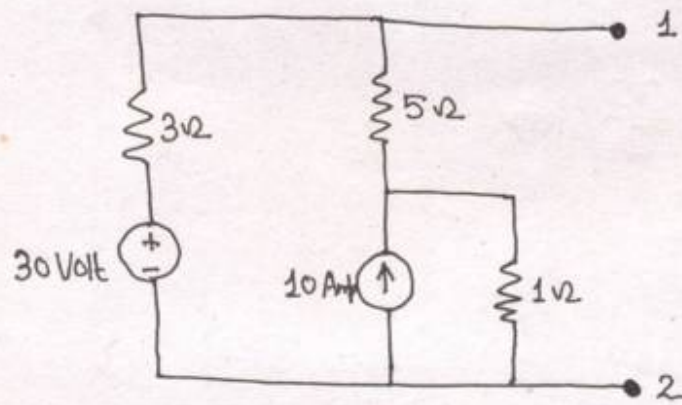


Fig. 4.69: Circuit for Ex-4.26

Soln.

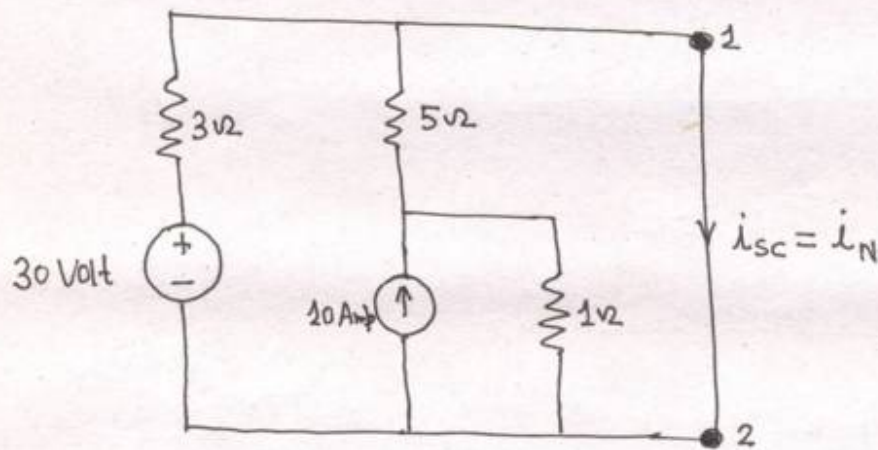

(a)

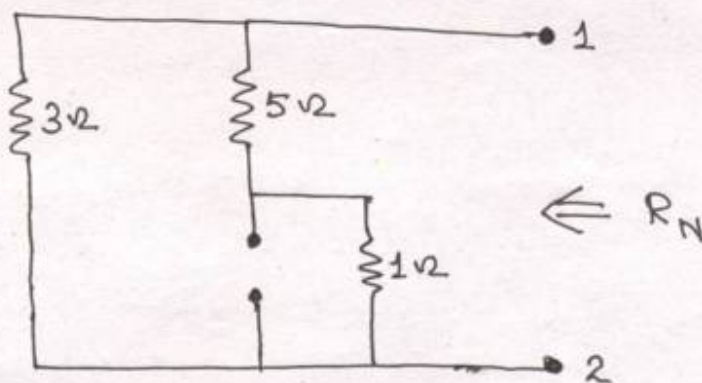

(b)

Fig. 4.70: (a) finding i_N (b) finding R_N

In Fig. 4.70(a), Short circuit current is given by

$$i_{sc} = \left(\frac{30}{3}\right) + \frac{1}{(5+1)} \times 10$$

(60)

$$\therefore i_{sc} = 10 + \frac{5}{3} = \frac{35}{3} \text{ Amp}$$

$$\therefore i_N = i_{sc} = \frac{35}{3} \text{ Amp.}$$

From Fig. 4.70(b),

$$R_N = \frac{3 \times (5+1)}{3 + (5+1)} = 2\Omega$$

Norton equivalent circuit is given in Fig. 4.71,

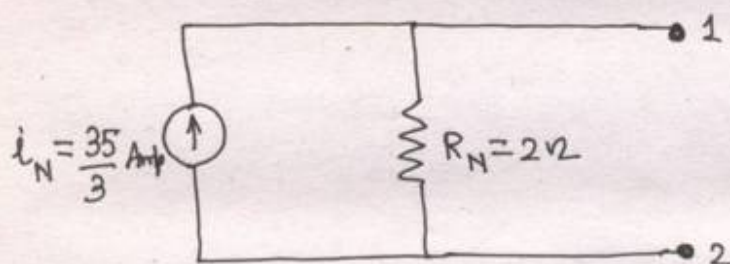


Fig. 4.71: Norton equivalent circuit for Ex-4.26

EX-4.27: Determine R_N of the circuit shown in Fig. 4.72 using $R_N = v_{oc}/i_{sc}$.

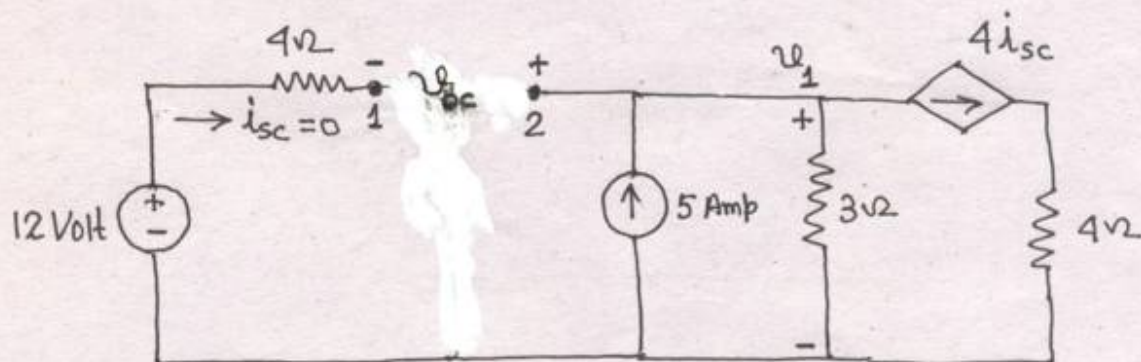


Fig. 4.72: Circuit for Ex-4.27.

Soln.

In the circuit of Fig. 4.72, $i_{sc} = 0$, hence,
 $v_1 = 5 \times 3 = 15 \text{ Volt.}$

Thus,

$$v_1 - 12 - v_{oc} = 0$$

$$\therefore v_{oc} = 15 - 12 = 3 \text{ Volt.}$$

To determine i_{sc} , terminals 1 and 2 are short circuited and the resulting circuit is shown in Fig. 4.73.

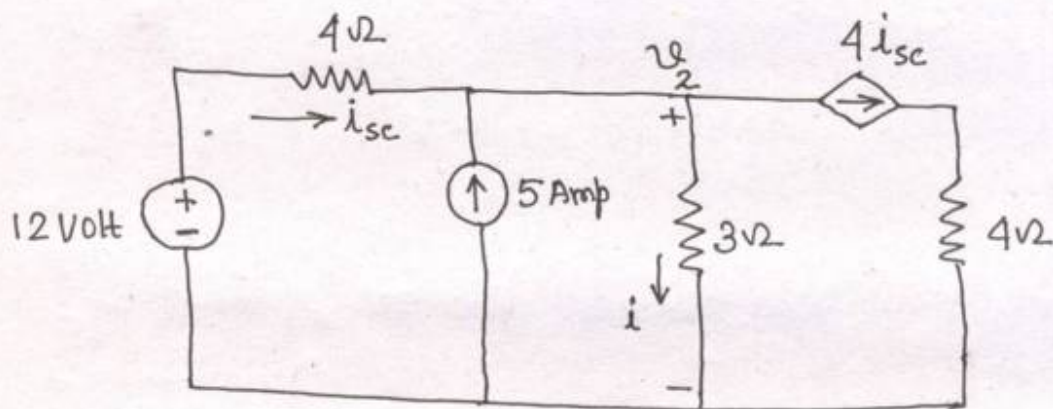


Fig. 4.73: finding i_{sc} for Ex-4.27

$$i_{sc} = \frac{12 - v_2}{4}, \quad i = \frac{v_2}{3}$$

Applying nodal analysis

$$\frac{12 - v_2}{4} + 5 = \frac{v_2}{3} + 4 \cdot \left(\frac{12 - v_2}{4} \right)$$

$$\therefore v_2 = 9.6 \text{ Volt.}$$

$$\therefore i_{sc} = \frac{12 - v_2}{4} = \frac{12 - 9.6}{4} = 0.6 \text{ Amp.}$$

$$\therefore R_N = \frac{v_{oc}}{i_{sc}} = \frac{3}{0.6} = 5 \Omega$$

Ex-4.28:

Obtain the Thevenin equivalent circuit at the terminals 1-2 of the circuit shown in Fig. 4.74

(62)

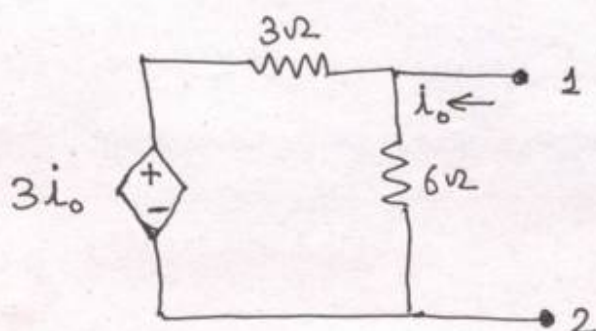
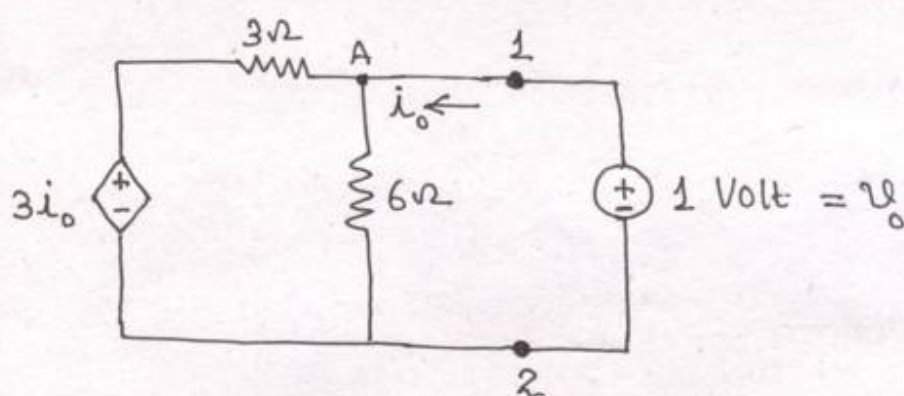


Fig. 4.74: Circuit for Ex-4.28

Soln.

Note that the circuit does not contain any independent source. To obtain the Thevenin equivalent, a voltage source of 1 Volt is applied across the terminals 1-2 and the resulting circuit is shown in Fig. 4.75.

Fig. 4.75: finding R_{TH} .

Using nodal analysis (At node A)

$$i_o = \frac{1}{6} + \frac{1-3i_o}{3} \quad \therefore i_o = \frac{1}{4} \text{ Amp}$$

$$\therefore R_{TH} = \frac{v_o}{i_o} = \frac{1}{1/4} = 4 \Omega$$

Note that there is no independent source in Fig. 4.74, hence, $v_{TH} = 0$. The Thevenin equivalent circuit is shown in Fig. 4.76. (63)

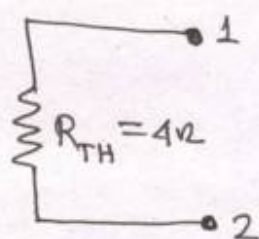


Fig. 4.76: Thevenin equivalent circuit for Ex-4.28

4.6: MAXIMUM POWER TRANSFER

In many practical cases, a circuit is designed to provide power to a load. There are applications in many areas where it is desirable to maximize the power delivered to the load.

The Thevenin equivalent is useful in finding the maximum power, a linear circuit can deliver to a load. We assume that load resistance R_L is adjustable. If the entire circuit is replaced by its Thevenin equivalent except for the adjustable load resistance as shown in Fig. 4.77, the power delivered to the load is

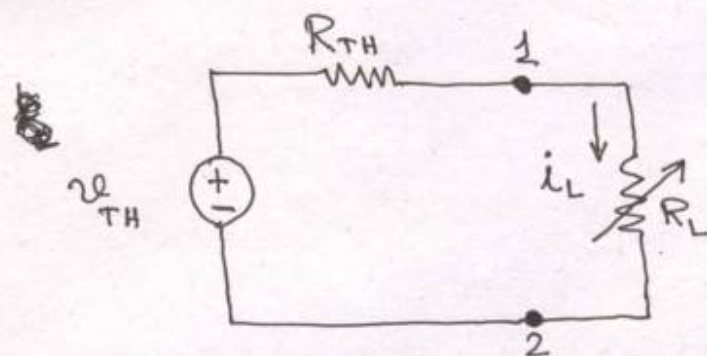


Fig. 4.77: The circuit used for maximum power transfer.

$$P_L = i_L^2 R_L = \left(\frac{V_{TH}}{R_{TH} + R_L} \right)^2 R_L \quad \dots (4.15)$$

(64)

For a given circuit, V_{TH} and R_{TH} are fixed.

By varying R_L , the power delivered to the load can be varied and it is sketched in Fig. 4.78

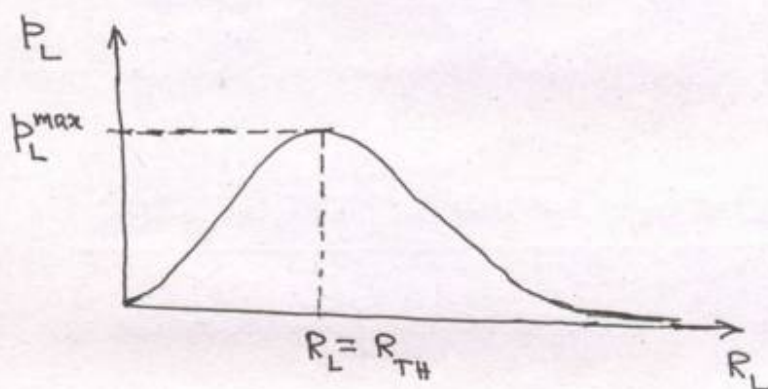


Fig. 4.78: P_L as a function of R_L

From Fig. 4.78, we notice that P_L is small for small or large value of R_L but maximum for some value R_L between 0 and ∞ .

To determine the condition for maximum power transfer, we set,

$$\frac{dP_L}{dR_L} = 0 \quad \dots (4.16)$$

$$\therefore V_{TH}^2 \left[\frac{(R_{TH} + R_L)^2 - 2R_L(R_{TH} + R_L)}{(R_{TH} + R_L)^4} \right] = 0$$

$$\therefore R_{TH} + R_L - 2R_L = 0$$

$$\therefore R_L = R_{TH} \quad \dots (4.17)$$

Therefore, maximum power occurs when $R_L = R_{TH}$. This is known as maximum power theorem.

Substituting $R_L = R_{TH}$, in eqn.(4.15), we get, (65)

$$P_L^{\max} = \frac{V_{TH}^2}{4R_{TH}} \quad \text{----- (4.18)}$$

Ex-4.29: Determine the value of R_L for maximum power transfer in the circuit shown in Fig.4.79. Also find the maximum power.

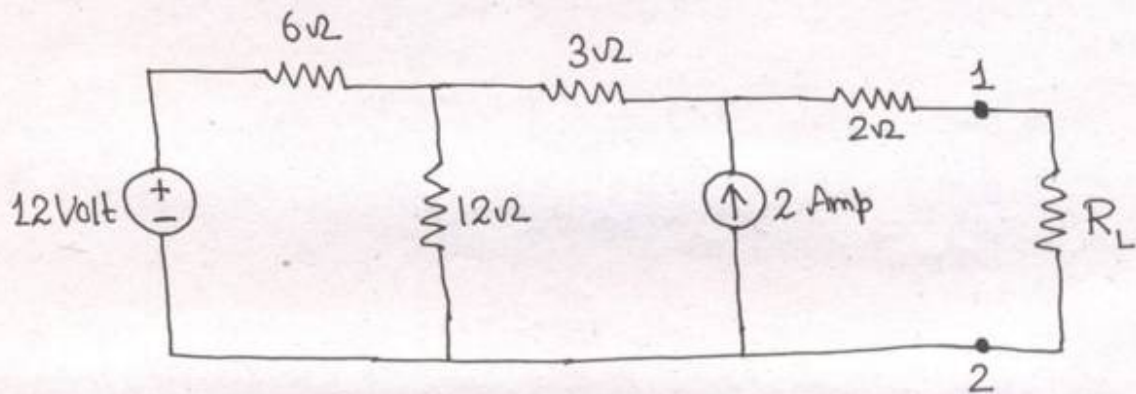


Fig.4.79: Circuit for Ex-4.29

Soln.

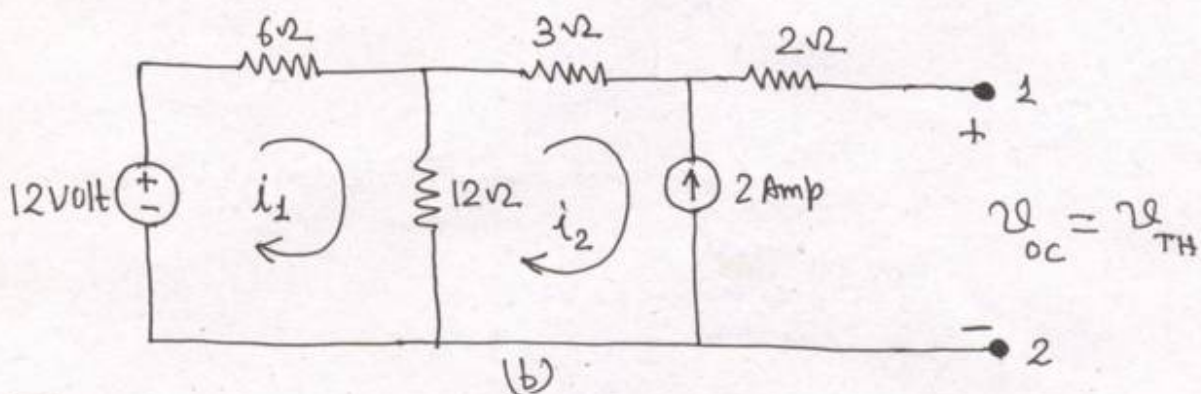
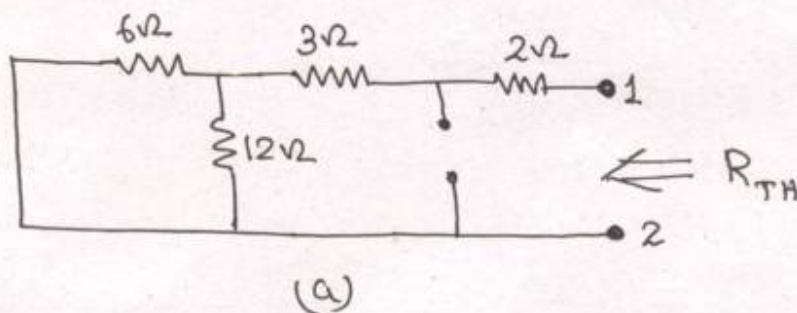


Fig.4.80: (a) finding R_{TH} (b) finding V_{TH} .

We need to determine R_{TH} and V_{TH} . From Fig. 4.80(a), (66)

$$R_{TH} = (2+3) + \frac{6 \times 12}{6+12} = 9 \Omega$$

From Fig. 4.80(b), we obtain by mesh analysis,

$$i_2 = -2 \text{ Amp}$$

and

$$18i_1 = 12 + 12i_2 = 12 + 12(-2) = -12$$

$$\therefore i_1 = -\frac{2}{3} \text{ Amp.}$$

Thus

$$3i_2 + V_{TH} + 12(i_2 - i_1) = 0$$

$$\therefore V_{TH} = -3i_2 - 12(i_2 - i_1)$$

$$\therefore V_{TH} = -3(-2) - 12(-2 + \frac{2}{3})$$

$$\therefore V_{TH} = 22 \text{ Volt}$$

For maximum power transfer,

$$R_L = R_{TH} = 9 \Omega$$

and the maximum power is,

$$P_L^{\max} = \frac{V_{TH}^2}{4R_L} = \frac{(22)^2}{4 \times 9} = 13.44 \text{ Watt.}$$

Ex-4.30: In the circuit of Fig. 4.81, what resistor R_L will absorb maximum power and what is this power?


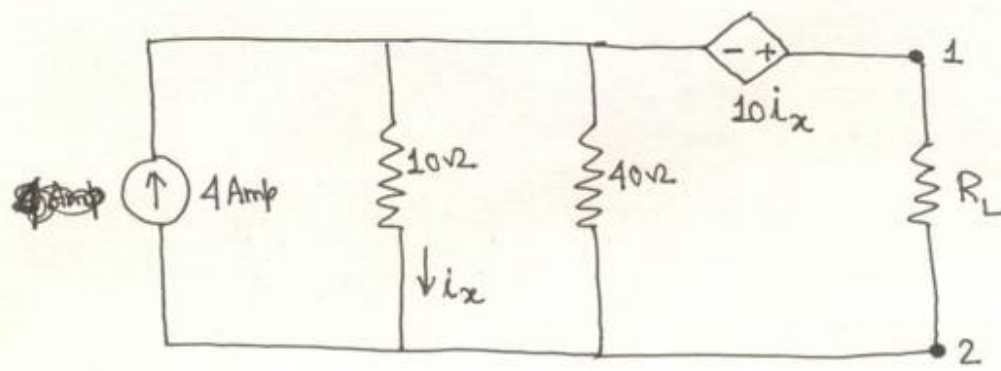



Fig. 4.81: Circuit for Ex- 4.30

Soln.

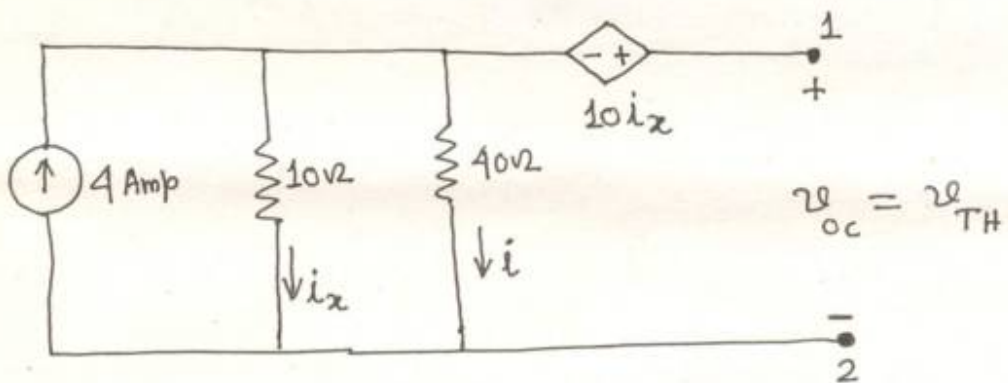For maximum power transfer,
 $R_L = R_{TH}$ and $P_L^{max} = \frac{v_{TH}^2}{4R_{TH}}$



(a)

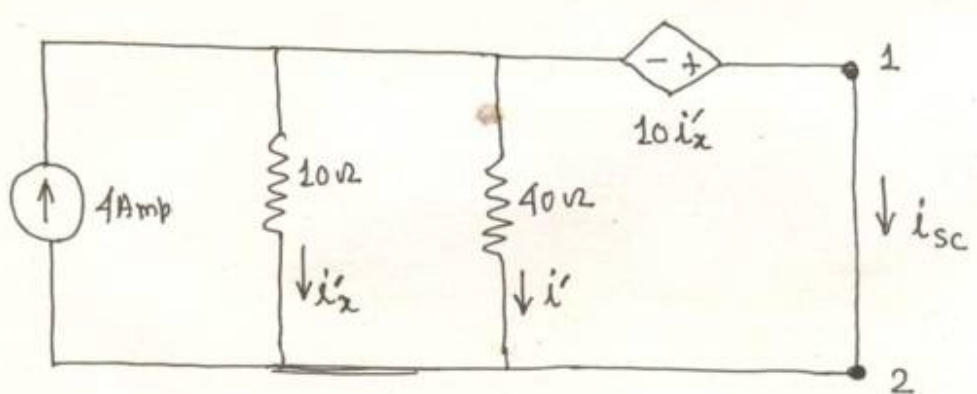

(b)

Fig. 4.82: (a) finding v_{TH} (b) finding i_{sc}

In Fig. 4.82(a),

$$i_x = \frac{40}{(40+10)} \times 4 = 3.2 \text{ Amp}$$

$$\therefore i = 4 - 3.2 = 0.8 \text{ Amp}$$

Thus

$$10i_x + 40i - v_{TH} = 0$$

$$\therefore v_{TH} = 40 \times 0.8 + 10 \times 3.2 = 64 \text{ Volt.}$$

It is convenient to use the short circuit current approach to determine R_{TH} . In Fig. 4.82(b), terminals 1-2 are short circuited. Hence ~~40V~~ 40V and 10V resistors are short circuited. ~~and~~ No current will be flowing through 10V and 40V resistors. Thus $i'_x = 0.0$ and $i' = 0.0$. Therefore all 4 Amp current will flow through the short circuit.

$$\therefore i_{sc} = 4 \text{ Amp.}$$

$$\therefore R_{TH} = \frac{v_{TH}}{i_{sc}} = \frac{64}{4} = 16 \Omega$$

$$\text{Thus, } R_L = R_{TH} = 16 \Omega$$

$$\therefore p_L^{\max} = \frac{v_{TH}^2}{4R_{TH}} = \frac{(64)^2}{4 \times 16} = 64 \text{ Watt.}$$

Ex-4.31: In the circuit of Fig.4.83, find R_L for maximum power transfer and also determine p_L^{\max} .

(69)

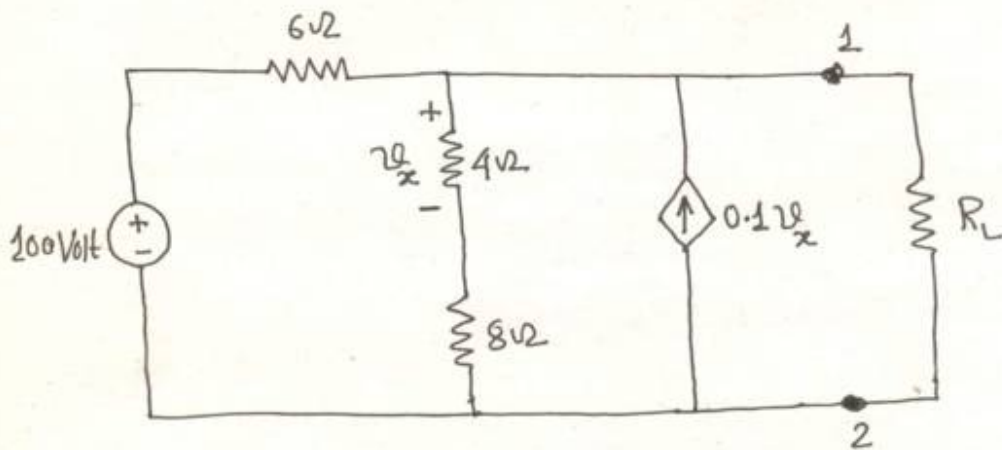


Fig. 4.82: Circuit for Ex-4.31

Soln.

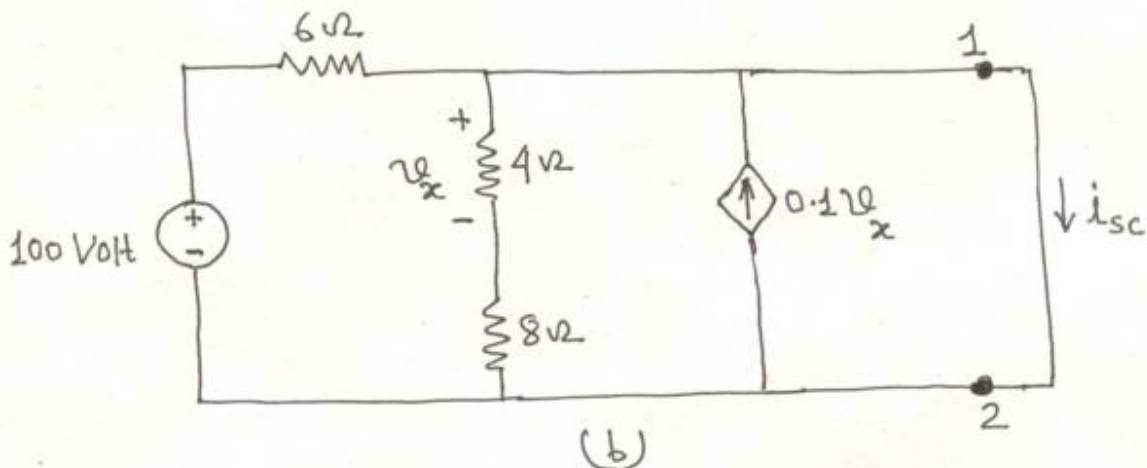
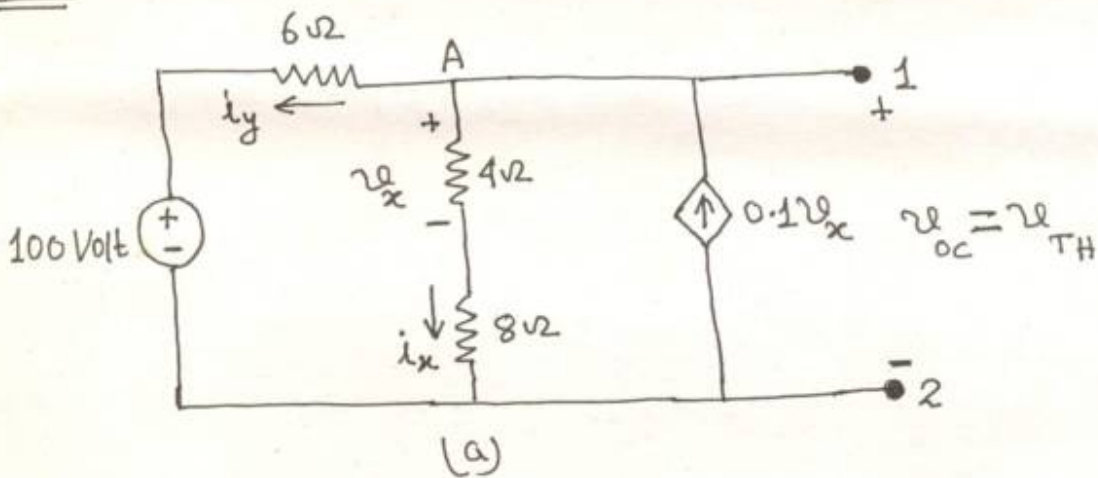


Fig. 4.83: (a) finding v_{TH} (b) finding i_{sc}

In Fig. 4.83(a), load resistance R_L is removed and $V_{oc} = V_{TH}$. Now 4Ω resistor is in series with 8Ω resistor. Voltage across 4Ω resistor is V_x ,

$$\therefore V_x = 4i_x \quad \dots (i)$$

Applying KVL, we get,

$$V_{TH} = 4i_x + 8i_x = ~~12i_x~~$$

$$\therefore V_{TH} = 12i_x \quad \dots (ii)$$

From eqns. (i) and (ii), we have

$$V_{TH} = 3V_x \quad \dots (iii)$$

At node A,

$$\frac{3V_x - 100}{6} + \frac{V_x}{4} - 0.1V_x = 0$$

$$\therefore \frac{V_x}{2} + \frac{V_x}{4} - 0.1V_x = \frac{100}{6}$$

$$\therefore V_x = 25.64 \text{ Volt}$$

$$\therefore V_{TH} = 3V_x = 3 \times 25.64 = 76.92 \text{ Volt}$$

$$\therefore i_y = \frac{3V_x - 100}{6} = \frac{3 \times 25.64 - 100}{6} = -3.846 \text{ Amp}$$

$$i_x = \frac{V_x}{4} = \frac{25.64}{4} = 6.41 \text{ Amp}$$

In Fig. 4.83(b), terminals 1-2 are short circuited to determine i_{sc} and hence R_{TH} . As the terminals 1-2 are short circuited, $V_x = 0.0$, this means

(71)

$(4+12) \Omega = 12 \Omega$ resistor is short circuited. (71)

Thus

$$i_{sc} = \frac{100}{6} = \frac{50}{3} \text{ Amp}$$

$$\therefore R_{TH} = \frac{V_{TH}}{i_{sc}} = \frac{76.92}{(50/3)} = 4.615 \Omega$$


For maximum power transfer,

$$R_L = R_{TH} = 4.615 \Omega$$

$$\therefore P_L^{\max} = \frac{V_{TH}^2}{4R_{TH}} = \frac{(76.92)^2}{4 \times 4.615} = 320.51 \text{ Watt.}$$

EXERCISE-4

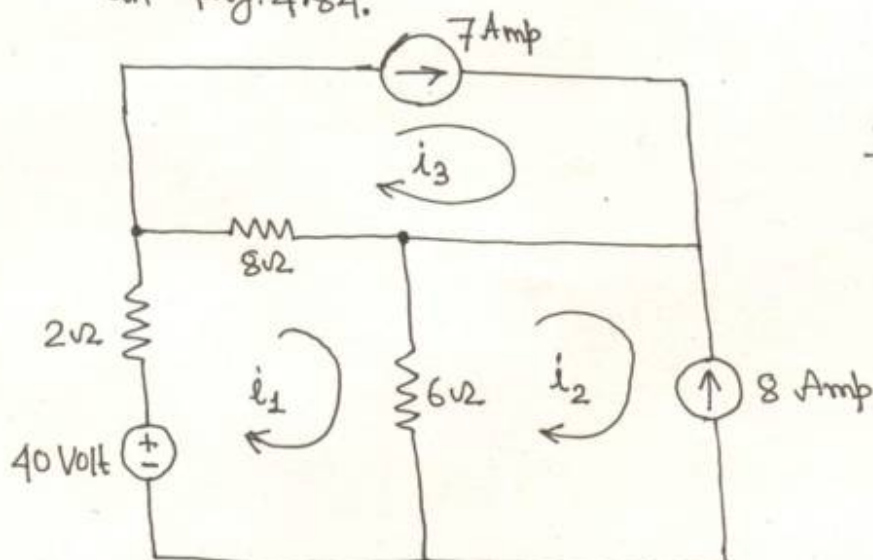4.1: Determine i_1 , i_2 and i_3 for the circuit shown in Fig. 4.84.




Ans: $i_1 = 3 \text{ Amp}$
 $i_2 = -8 \text{ Amp}$
 $i_3 = 7 \text{ Amp.}$

Fig. 4.84: Circuit for Problem 4.1

4.2: Determine current through 2Ω resistor of the circuit shown in Fig. 4.85 by using superposition.


(72)

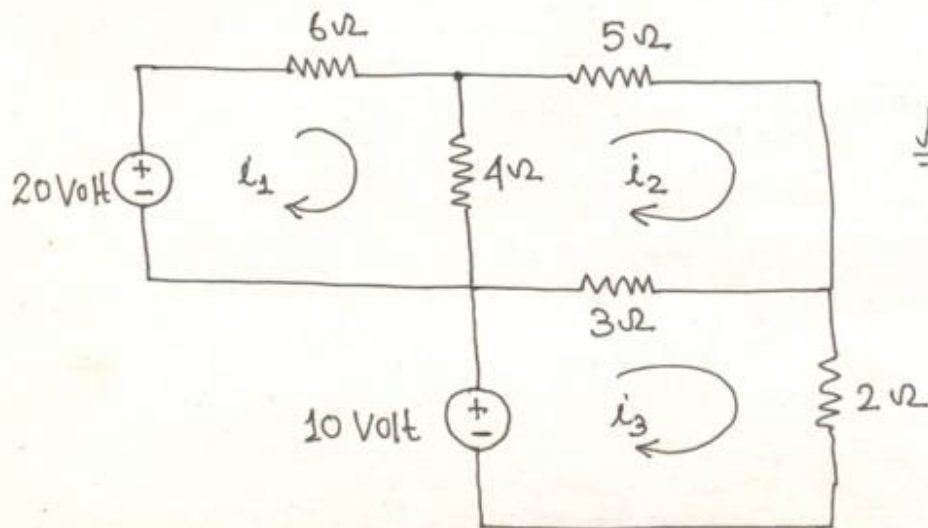

Ans: $i_3 = 2.98 \text{ Amp}$

Fig. 4.85: Circuit for Problem 4.2

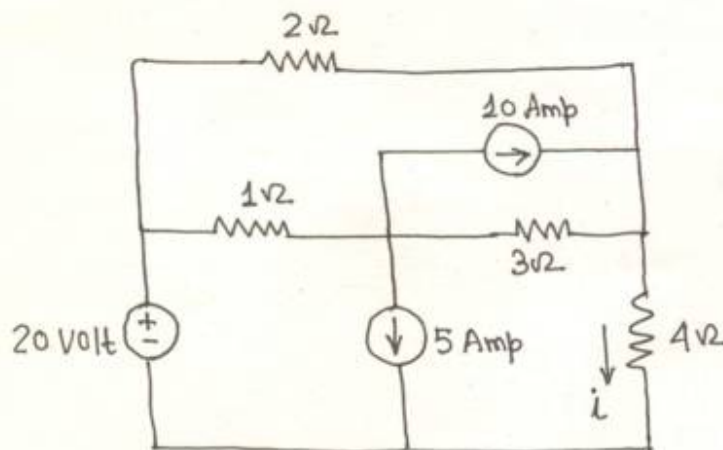4.3: Calculate the current through 4Ω resistor of the circuit shown in Fig. 4.86 by superposition.



Ans: $i = 5.31 \text{ Amp}$

Fig. 4.86: Circuit for Problem 4.3

4.4: Determine v_x and i_x of the circuit shown in Fig. 4.87 by applying source transformation.

(73)

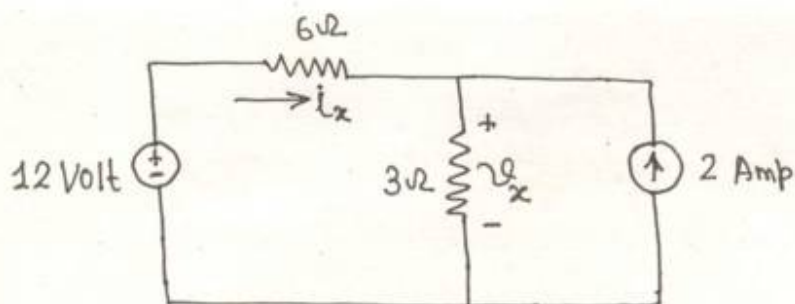


Fig. 4.87: Circuit for Problem 4.4

Ans: $v_x = 8 \text{ Volt}$

$i_x = 0.67 \text{ Amp}$

4.5: Using source transformation determine current and power in 8Ω resistor of the circuit shown in Fig. 4.88

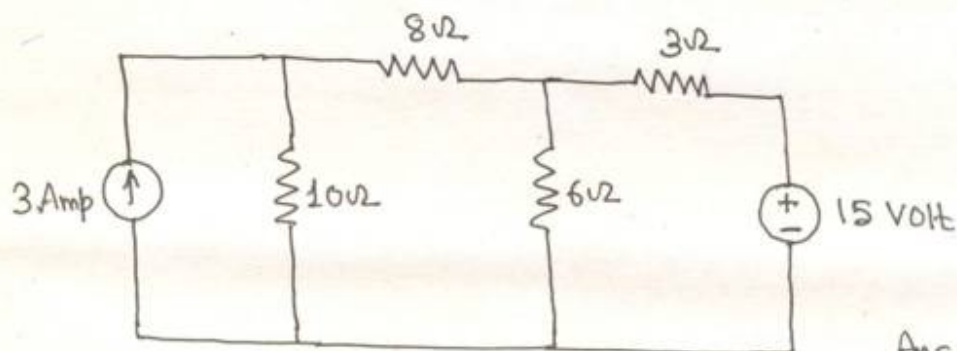


Fig. 4.88: Circuit for Problem 4.5

Ans: 1 Amp

8 Watt.

4.6: In the circuit of Fig. 4.89, determine v_o using source transformation.

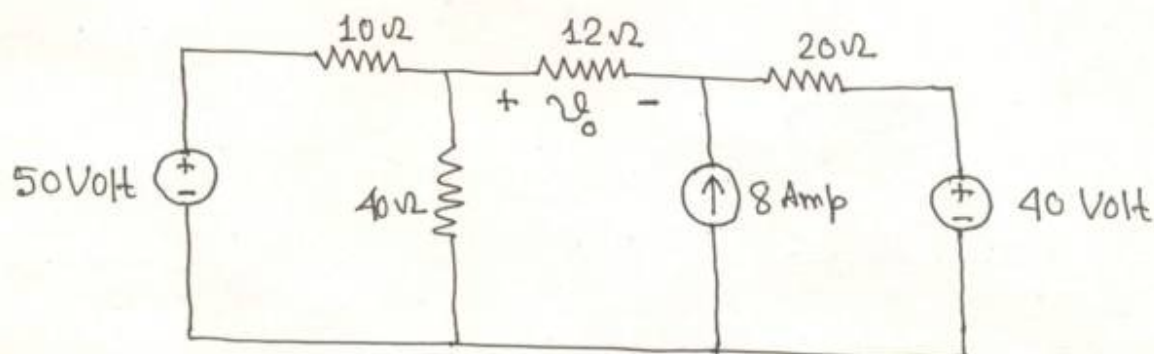


Fig. 4.89: Circuit for Problem 4.6

Ans: $v_o = -48 \text{ Volt.}$

4.7: Determine the current i_x in the circuit of Fig. 4.90 by making a succession of appropriate source transformations. Also find the power developed by the 75 Volt source.

(74)
(74)

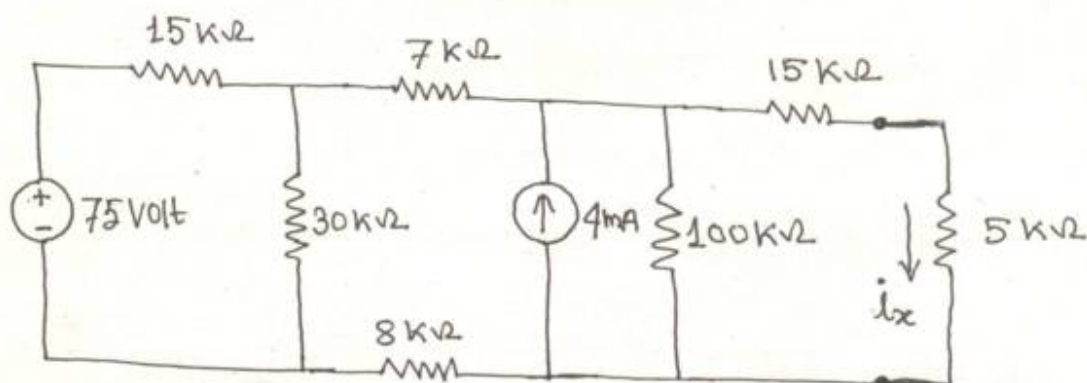


Fig. 4.90: Circuit for ~~Fig.~~ Problem 4.7

Ans: 3 mAmp
0.105 Watt

4.8: Find v_o of the circuit of Fig. 4.91 by using source transformations. Also find (a) the power developed by the 300 Volt source (b) the power developed by 10 Amp current source (c) verify that the total power developed equals to the total power dissipated.


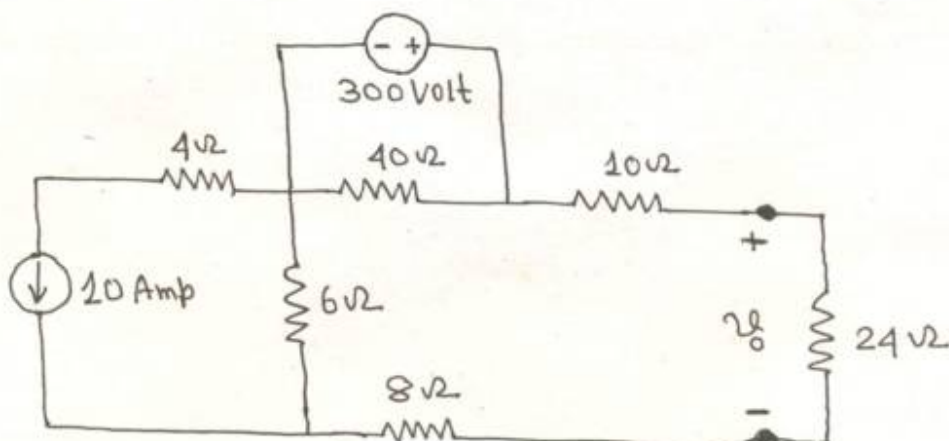


Fig. 4.91: Circuit for Problem 4.8

Ans: $v_o = 120$ Volt
(a) 3750 Watt
(b) 1300 Watt
(c) 5050 Watt

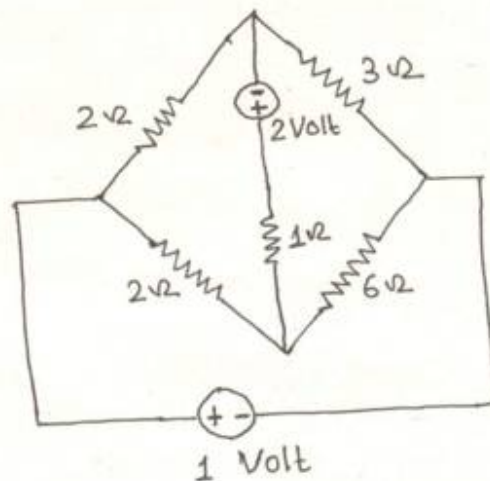
4.9: Determine the current through $3\ \Omega$ resistor of the circuit shown in Fig. 4.92 by using superposition.



Ans: 0.0 Amp

Fig. 4.92: Circuit for Problem 4.9

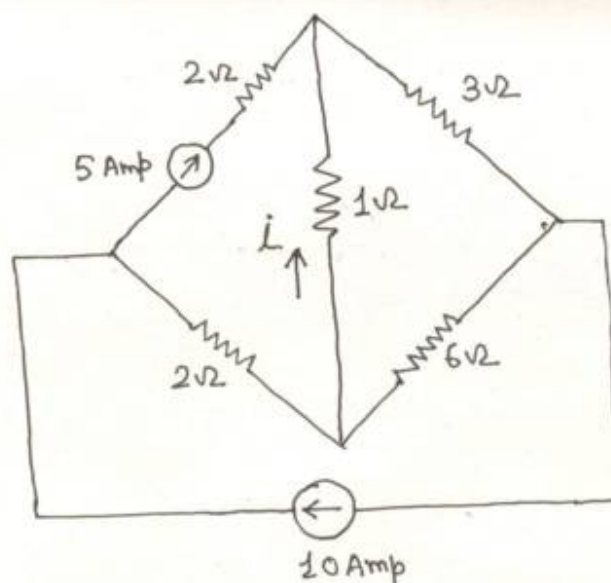4.10: Determine the current through $1\ \Omega$ resistor of the circuit shown in Fig. 4.93 by using superposition.



Ans: $i = 1.5$ Amp

Fig. 4.93: Circuit for Problem 4.10

4.11: Determine v_x of the circuit shown in Fig. 4.93 by using superposition.

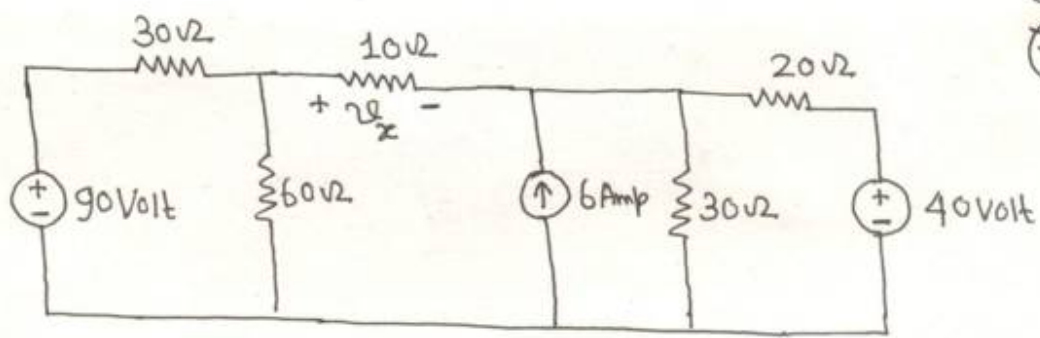


Fig. 4.93: Circuit for Problem 4.11.

Ans: $v_x = -8.57 \text{ Volt}$

4.12: Determine v_o of the circuit shown in Fig. 4.94 by using source transformation

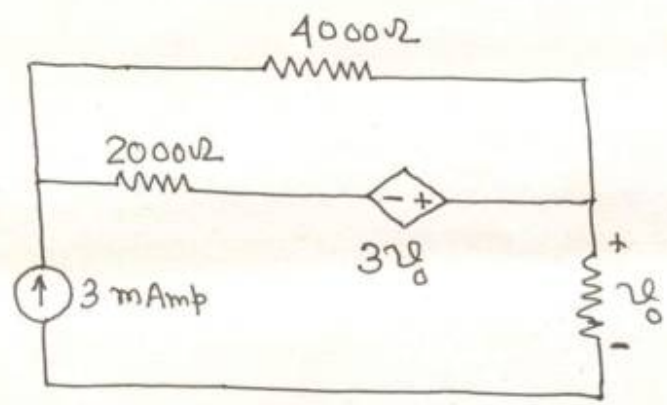


Fig. 4.94: Circuit for Problem 4.12

Ans: $v_o = 3 \text{ Volt}$

4.13: Determine the Thevenin equivalent circuit of which hold for the terminal pair 1-2 in the circuit of Fig. 4.95


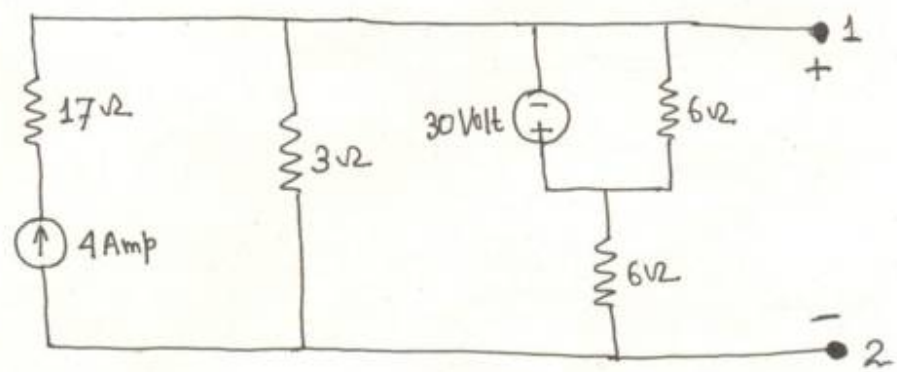


Fig. 4.95: Circuit for Problem 4.13

Ans: $v_{TH} = -2 \text{ Volts}$
 $R_{TH} = 2 \Omega$

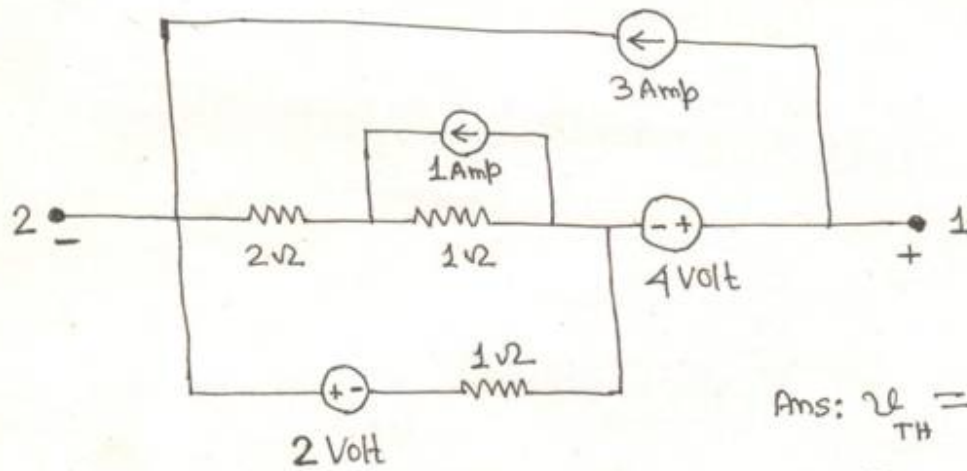4.14: Determine the Thevenin equivalent circuit for the network shown in Fig. 4.96 at the terminals 1-2



Ans: $V_{TH} = 0.0 \text{ Volt}$

$R_{TH} = 0.75 \Omega$

Fig. 4.96: Circuit for Problem 4.14

4.15: Determine the Thevenin equivalent circuit of the network shown in Fig. 4.97 at the terminals 1-2.

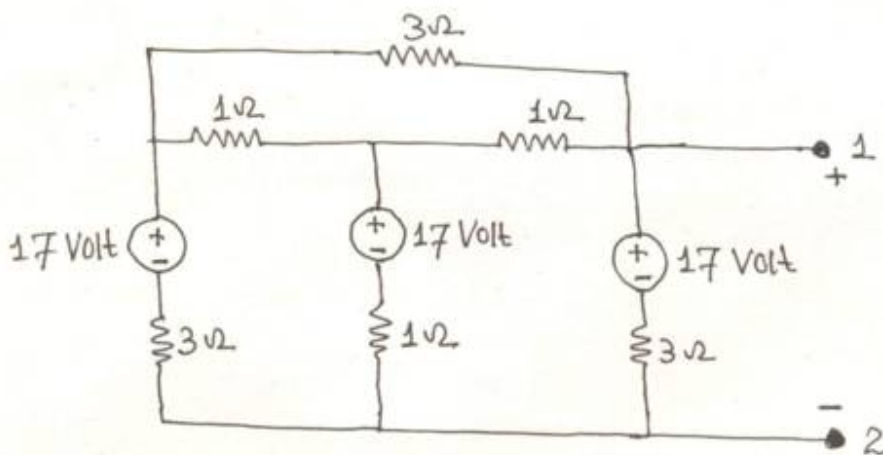


Fig. 4.97: Circuit for Problem 4.15

Ans: $V_{TH} = 17 \text{ Volts}$

$R_{TH} = 1 \Omega$

4.16: Determine the Thevenin equivalent circuit of the network shown in Fig. 4.98 at the terminals 1-2.

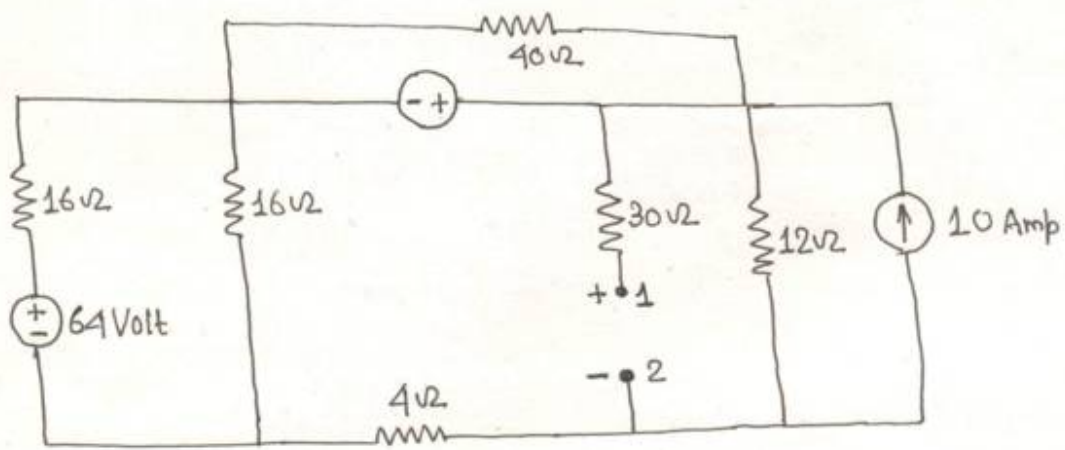


Fig. 4.98: Circuit for Problem 4.16

Ans: $V_{TH} = 88 \text{ Volts}$

$R_{TH} = 36\Omega$

4.17: Determine the Norton equivalent circuit for the network shown in Fig. 4.99.


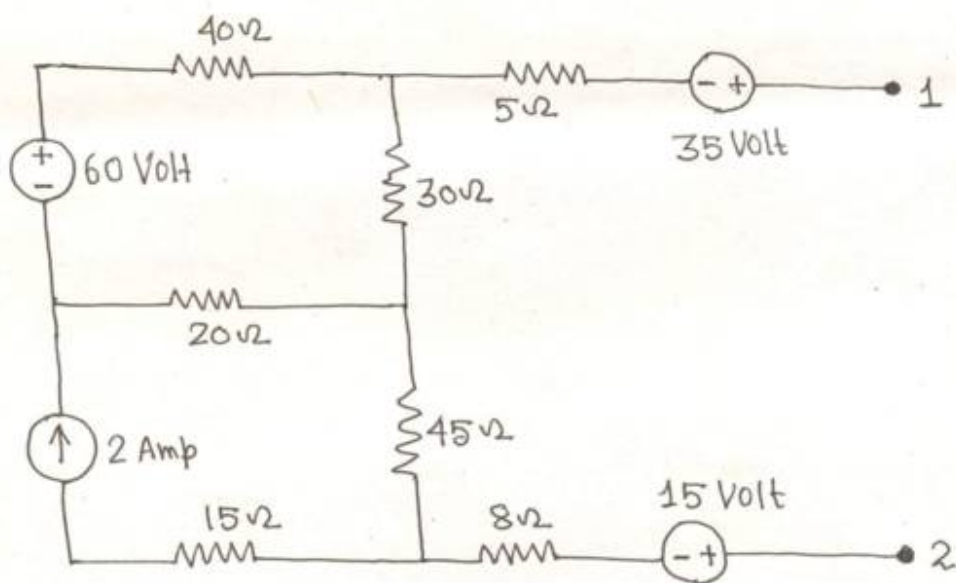


Fig. 4.99: Circuit for Problem 4.17

Ans: $I_N = 1.84 \text{ Amp}$

$R_N = 78\Omega$

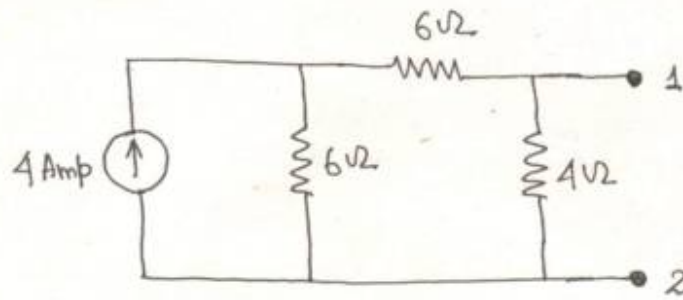4.18: Determine Norton equivalent of the circuit in Fig. 4.100 at the terminals 1-2.



Ans: $i_N = 2 \text{ Amp}$

$R_N = 3 \Omega$

Fig. 4.100: circuit for Problem 4.18

4.19: Determine Norton equivalent of the circuit shown in Fig. 4.101 at the terminals 1-2.


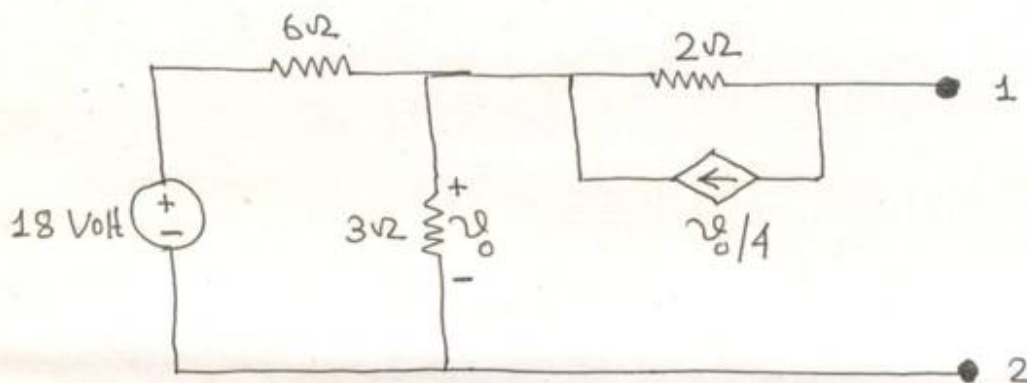


Fig. 4.101: circuit for Problem 4.19

Ans: $i_N = 1 \text{ Amp}$

$R_N = 3 \Omega$

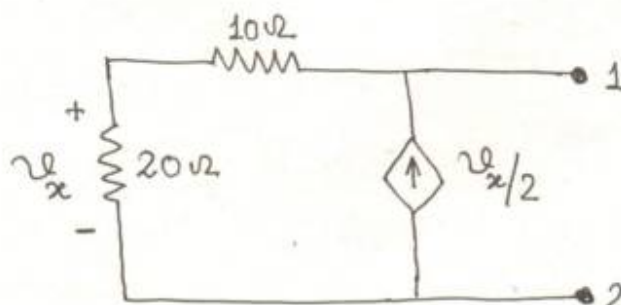4.20: Determine the Norton equivalent for the circuit shown in Fig. 4.102



Ans: $i_N = 0.0 \text{ Amp}$

$R_N = -\frac{1}{3} \Omega$

Fig. 4.102: Circuit for Problem 4.20

- 4.21: Determine the value of R_L for which it draws maximum power in the circuit of Fig. 103. Also determine P_L^{\max} .

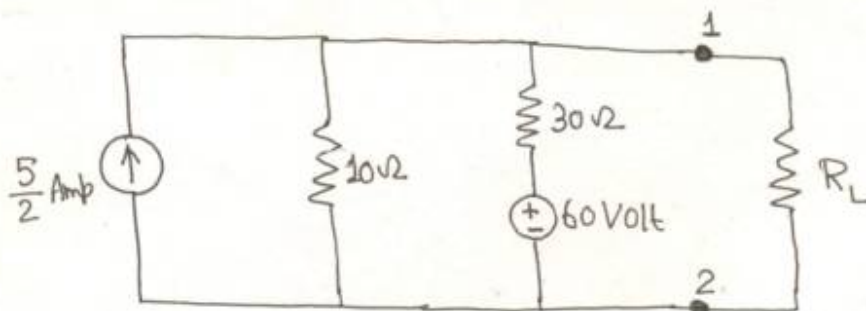


Fig. 4.203: Circuit for Problem 4.21

Ans: $R_L = 2\Omega$

$P_L^{\max} = 4.5 \text{ Watt.}$

- 4.22: Determine the value of R_L for which it absorbs maximum power in the circuit of Fig. 4.104 and also determine P_L^{\max} .



Ans: $R_L = 7.5\Omega$

$P_L^{\max} = 38 \text{ Watt.}$

Fig. 4.104: Circuit for Problem 4.22.

- 4.23: The variable resistor R_L in the circuit in Fig. 4.105 is adjusted until the power dissipated in the resistor is 250 Watt. Determine the values of R_L that satisfy the condition.

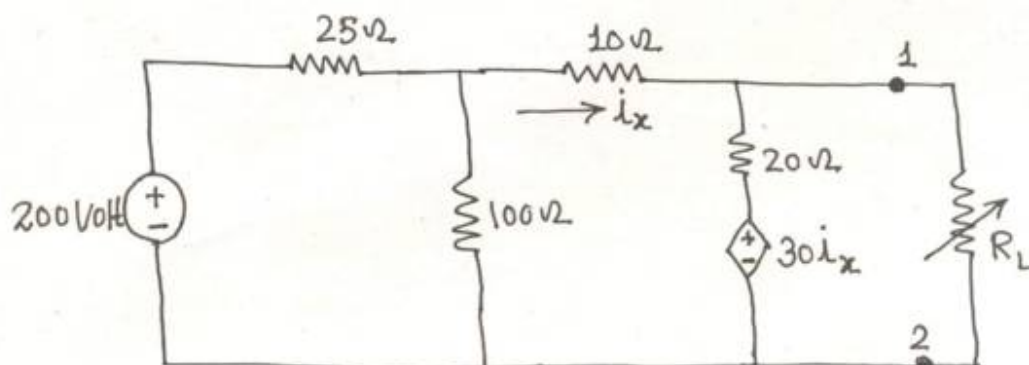


Fig. 4.105: Circuit for Problem 4.23

Ans: $R_L = 2.5\Omega$

OR

$R_L = 22.5\Omega$

4.24 : Determine the value of R_L that enables the circuit shown in Fig. 4.106 to deliver maximum power to the terminals 1, 2. Find the maximum power delivered to R_L

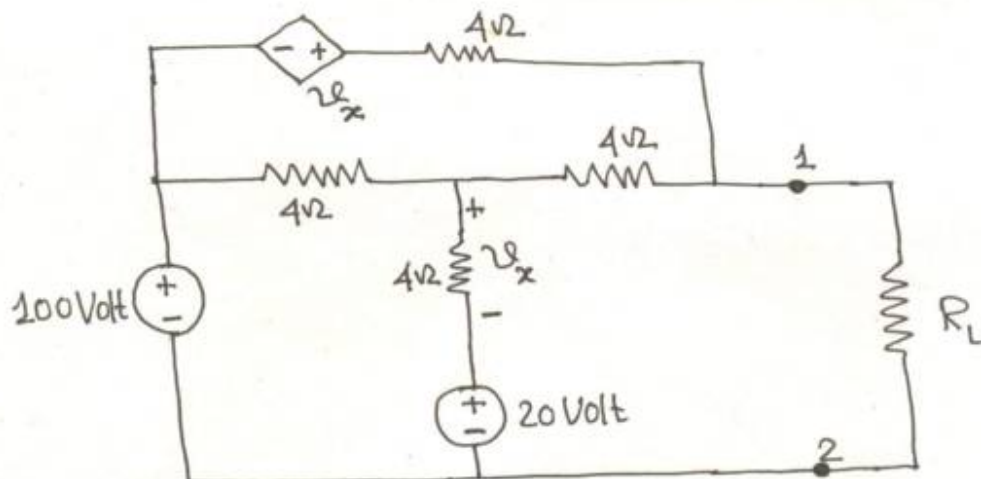


Fig. 4.106: Circuit for Problem 4.24.

Ans: $R_L = 3\Omega$

$P_L^{\max} = 1200 \text{ Watt.}$

4.25: For the circuit shown in Fig. 4.107, determine the relationship between v_o and i_o .

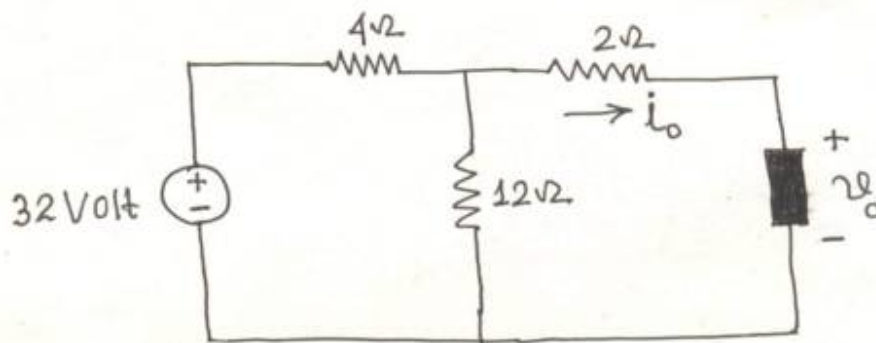


Fig. 4.107: Circuit for Problem 4.25

Ans: $v_o = 24 - 5i_o$