

WK	M	T	W	T	F	S	S
05			1	2	3	4	
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				



Wk 01 • 003 Day

WEDNESDAY

03

METHODS OF ANALYSIS

- Current flows from a higher potential to a lower potential in a resistor.
- Mesh-analysis is also known as loop analysis or the mesh-current method.
- a) Mesh is a loop which does not contain any other loops within it.
- b) A supermesh results when two meshes have a (dependent or independent) current source in common. (similarly supernode)
 - ↳ for them a single equation is better.
- In nodal analysis, assign node voltages, and use KCL.
- "Node" refers to any point on a circuit where two or more branches meet.
- A "branch" represents a single element such as a voltage source or a resistor.
- A "junction" is any point where conductors are joined electrically.
- A "loop" is any closed path in a circuit.


Wk	M	T	W	T	F	S	S
05			1	2	3	4	
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

DC Network Theorems

Wk 01 • 005 Day

① Linear Systems

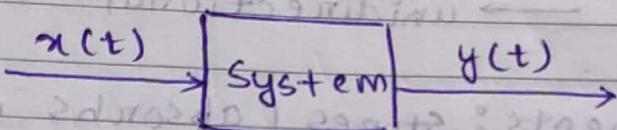- A system is said to be linear if it satisfies the following:
 - Additive property (or superposition theorem)
 - Homogeneity property



- Additive property $x_1(t) \rightarrow y_1(t)$

$$x_2(t) \rightarrow y_2(t)$$

$$\Rightarrow x_1(t) + x_2(t) \rightarrow y_1(t) + y_2(t)$$

- Homogeneity property $\alpha x(t) \rightarrow \alpha y(t)$


(any scalar)

Together; $\alpha_1 x_1(t) + \alpha_2 x_2(t) \rightarrow \alpha_1 y_1(t) + \alpha_2 y_2(t)$

Ex : I) Resistor ($V = IR$)

II) Inductor ($V_L = L \frac{di_L}{dt}$)

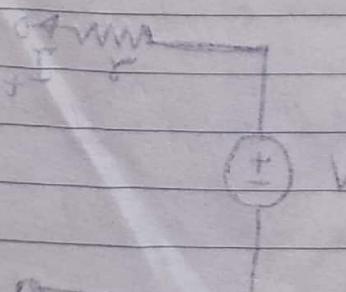III) Capacitor ($I_C = C \frac{dv_C}{dt}$)



'18 JANUARY

06

Wk 01 • 006 Day

SATURDAY

DC Network Analysis

Wk	M	T	W	T	F	S	S
01	1	2	3	4	5	6	7
02	8	9	10	11	12	13	14
03	15	16	17	18	19	20	21
04	22	23	24	25	26	27	28
05	29	30	31				

 02
Wk M
05
06
07
08
09
12
19
26

④

② Bidirectional, passive and active elements

→ Current can flow in both direction, and then bidirectional element

R, L, C → bidirectional
diodes → unidirectional


→ Passive elements: stores / absorbs energy
R, L, C

→ Active elements: generates / amplifies power, voltage, current.


→ generators, current and voltage sources.

③ Ideal voltage source

07 Sunday

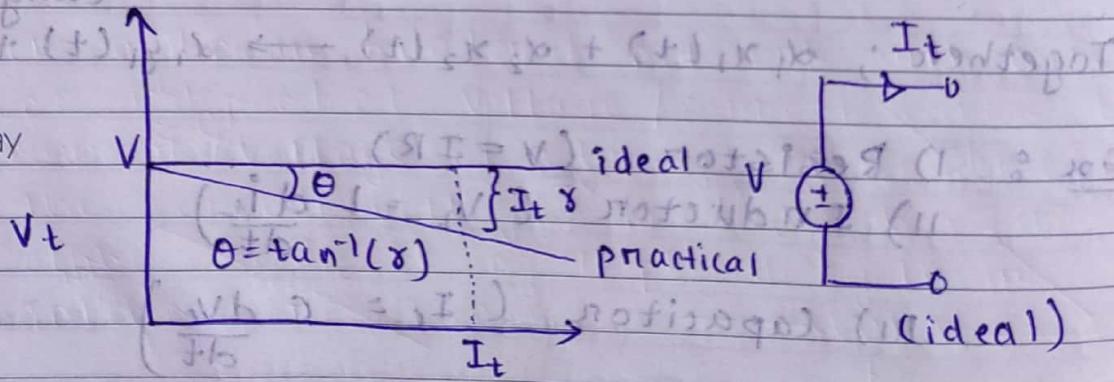

(load/terminal current)


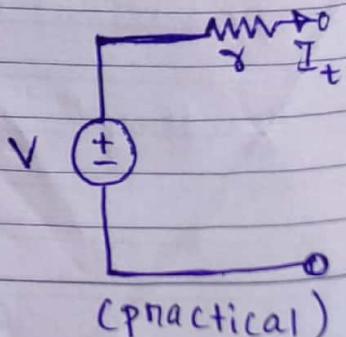


(practical)


Wk	M	T	W	T	F	S	S
05			1	2	3	4	
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

Wk 02 • 008 Day
MONDAY

(4) Ideal current source

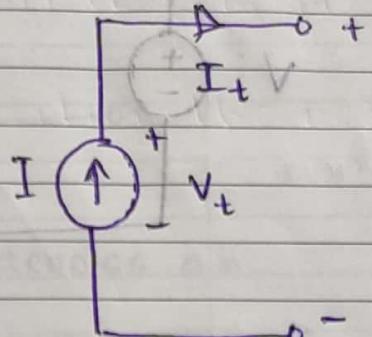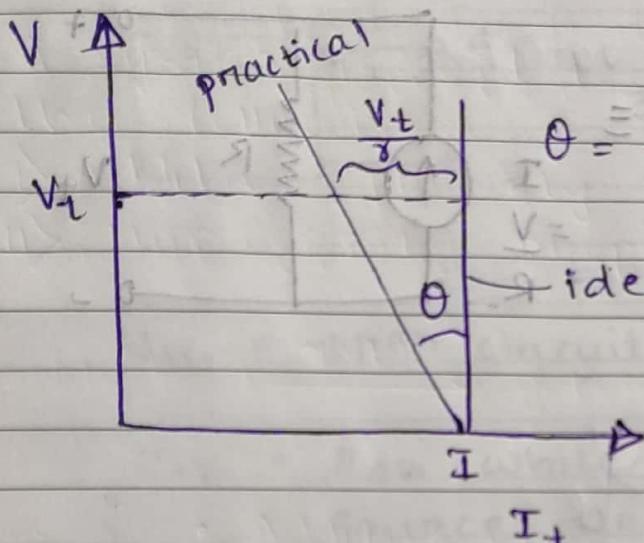


(Ideal)

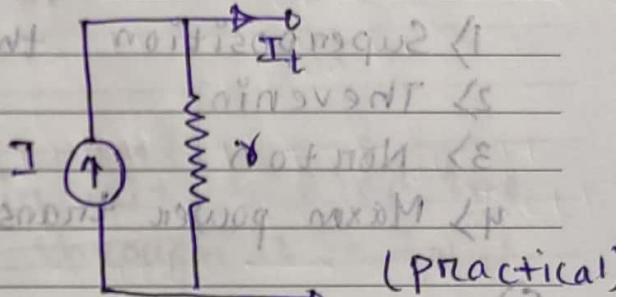

(Practical)

→ [check the resistor colour code]


(5) Source transformation

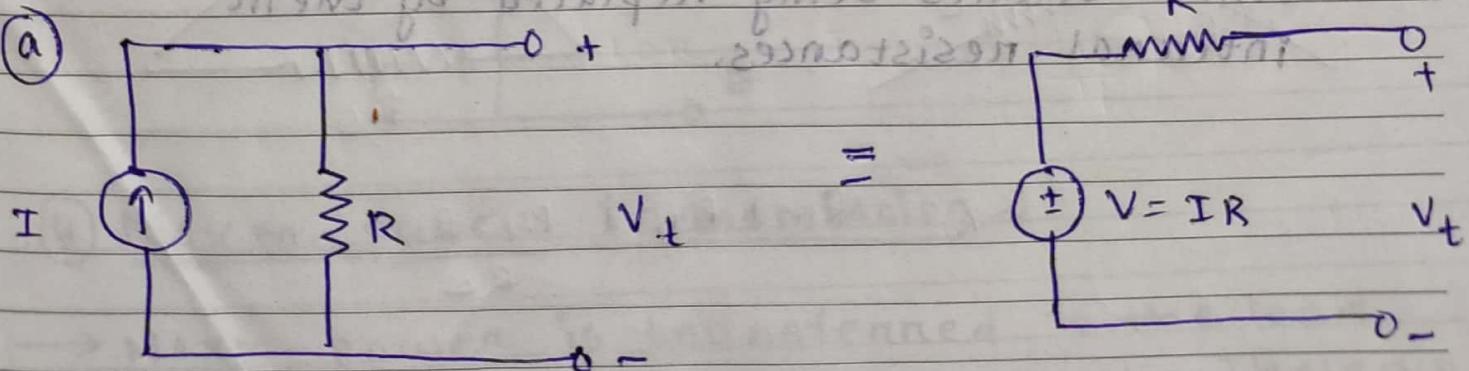


09

 Wk 02 • 009 Day
TUESDAY

(b)

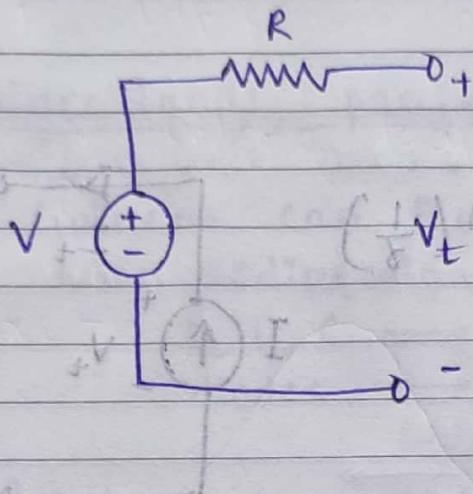

09/01/2018 Tuesday 10:30 AM (b)

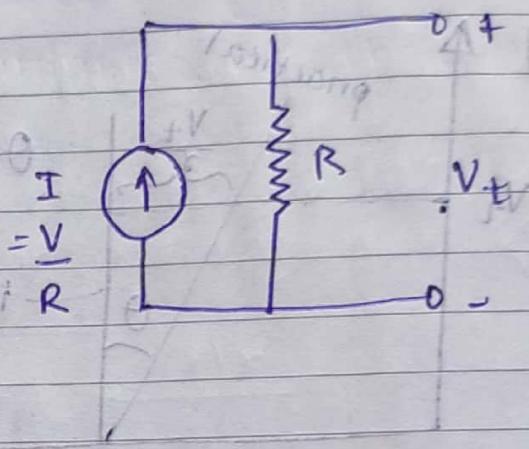


* Network Theorems

- 1) Superposition theorem
- 2) Thevenin "
- 3) Norton "
- 4) Maxm power transmission "

} Assumption :
The circuit is
linear & bilateral

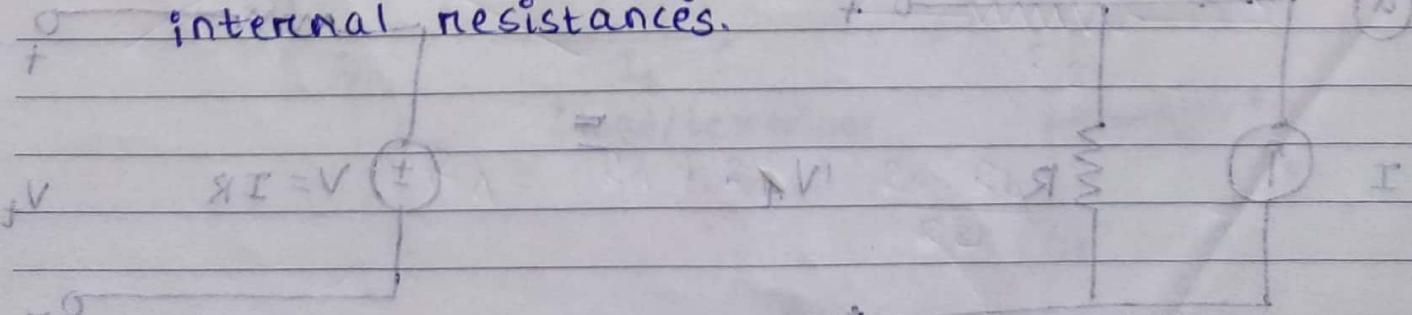(1) Superposition theorem


For a linear, bilateral network with more than one independent voltage / current sources, the current / voltage of a branch / node is equal to the current / voltage due to each sources with other sources being replaced by their internal resistances.



Wk	M	T	W	T	F	S	S
05			1	2	3	4	
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

Wk 02 • 010 Day


WEDNESDAY

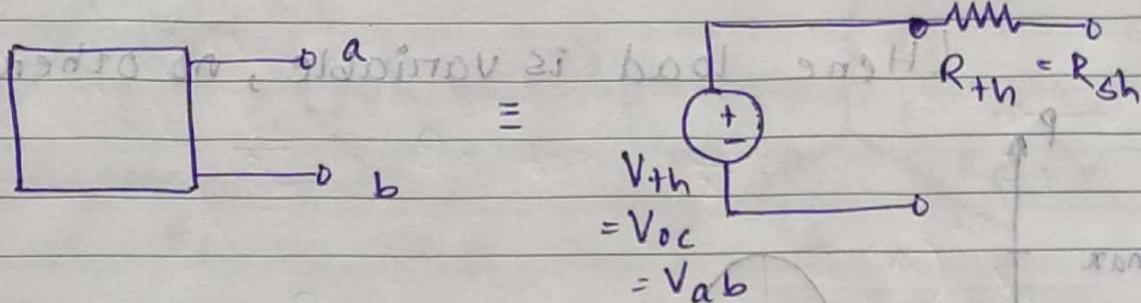(2) Thevenin V_{th} = open circuit voltage across ab R_{th} = R_{ab} while voltage and current sources are replaced by internal resistance(3) Norton

$$I_N = \frac{V_{th}}{R_{th}}$$

(Short circuit to find the current through it = I_N)

$$R_{th} = R_{Norton} = R_N$$

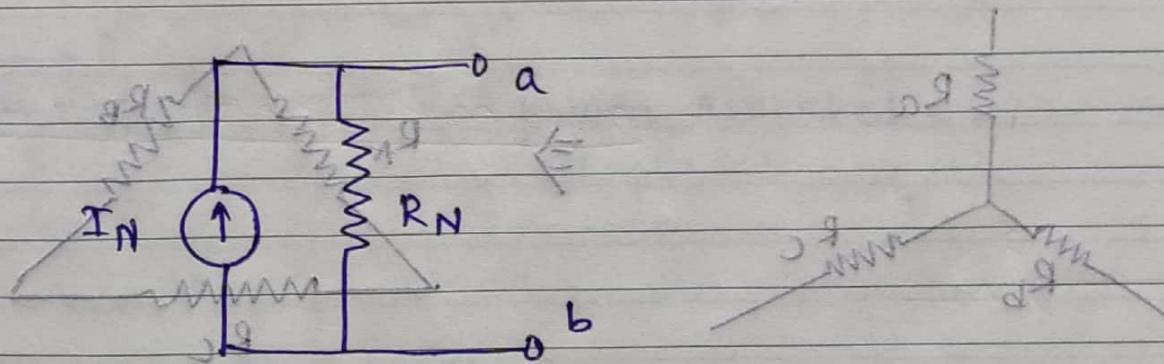(4) Maxm. power transmission

→ Maxm. power is transferred to the load when the load resistance equals the Thevenin


11

Wk 02 • 011 Day

THURSDAY

Wk	M	T	W	T	F	S	S
01	1	2	3	4	5	6	7
02	8	9	10	11	12	13	14
03	15	16	17	18	19	20	21
04	22	23	24	25	26	27	28
05	29	30	31				

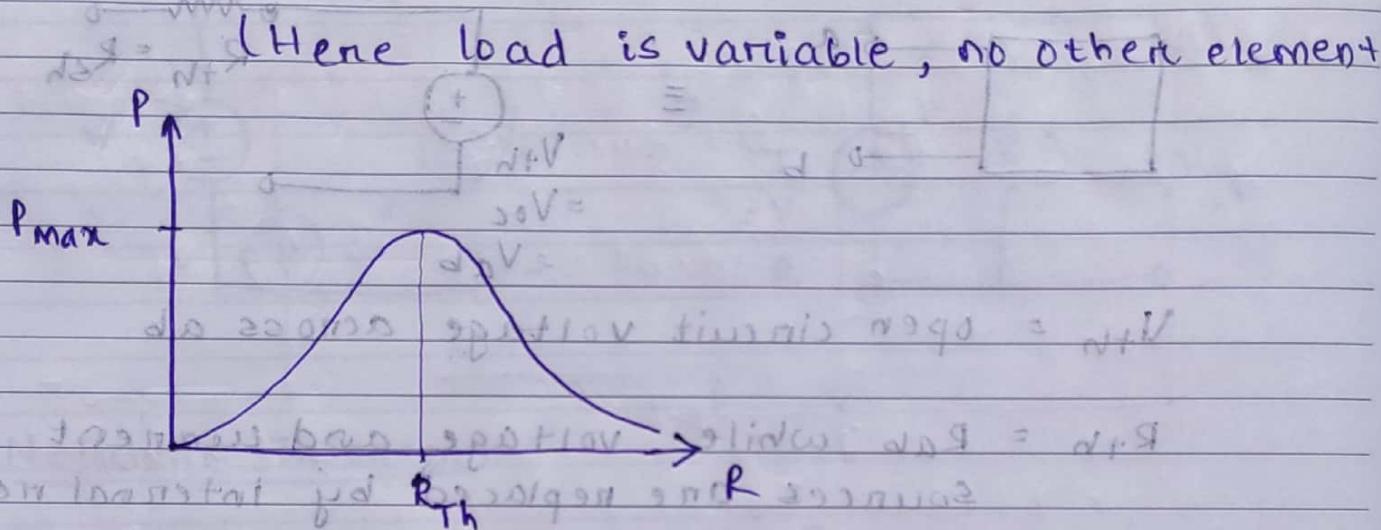
Resistance as seen from the load ($R_L = R_{Th}$)



$$P_{Max.} = \frac{V_{Th}^2}{4R_{Th}}$$

Notation

* Star \leftrightarrow Delta

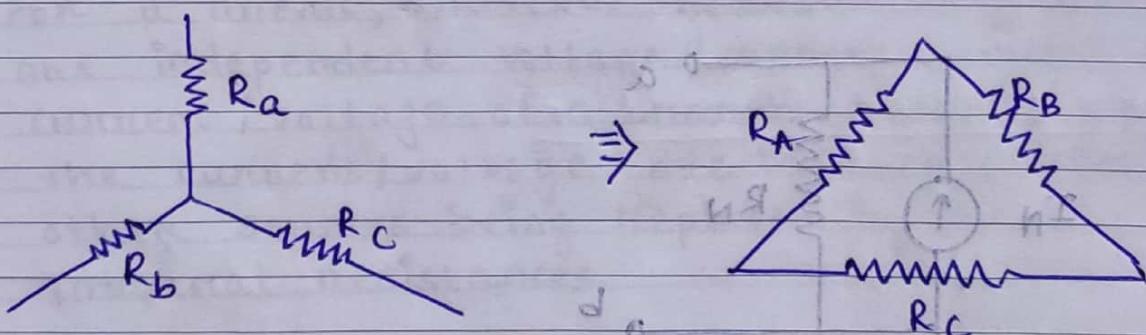


$$R_\Delta = R_A + R_B + \frac{R_A \cdot R_B}{R_C}$$

Result of transformation is giving max \leftrightarrow minimum and always transform load and





Wk	M	T	W	T	F	S	S
05				1	2	3	4
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

Wk 02 • 012 Day
FRIDAY

12

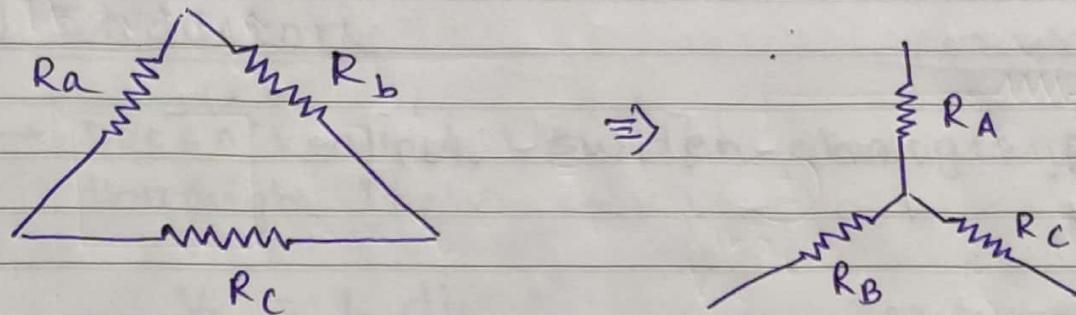
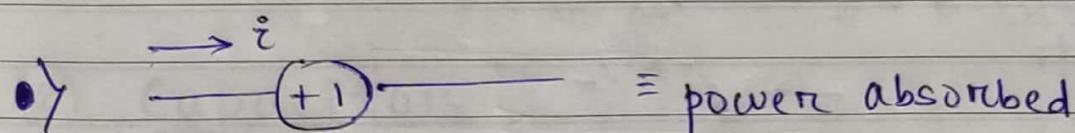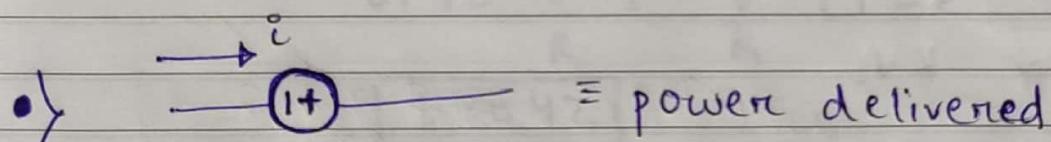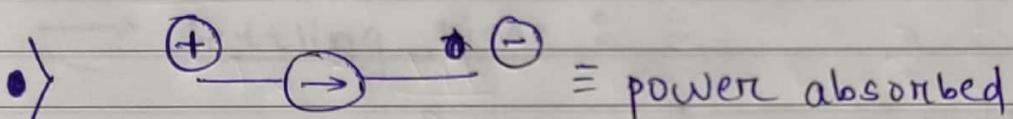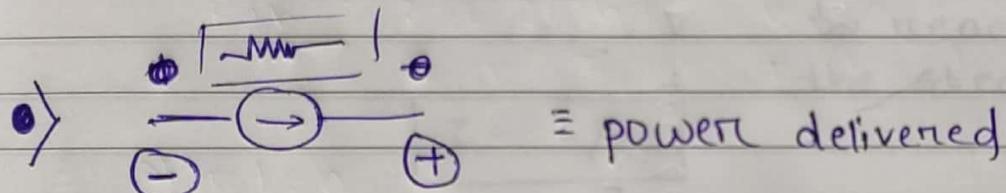
$$R_A = \frac{R_a \cdot R_b}{R_a + R_b + R_c}$$



Wk	M	T	W	T	F	S	S
05			1	2	3	4	
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

Wk 03 • 015 Day
MONDAY

DC TRANSIENTS

① Inductor

→ Doesn't allow sudden changes of current through it.

$$V_L = L \frac{di_L}{dt}$$

transient A ①

→ Time constant : It is the time required to reach the 63.2% of the steady state value

$$\tau = L/R$$

→ Settling time :

$$0.98 \frac{V}{R} = \frac{V}{R} (1 - e^{-t/\tau})$$

$$t \approx 4\tau$$

② Capacitor

→ Doesn't allow sudden changes of voltage across it.

$$(negative nature) C \frac{dV_C}{dt}$$

→ Time constant :

~~$\tau = \frac{1}{RC}$~~

$$\tau = RC$$

01	1	2	3	4	5	6
02	8	9	10	11	12	13
03	15	16	17	18	19	20
04	22	23	24	25	26	27
05	29	30	31			

'18 JANUARY

16

 Wk 03 • 016 Day
TUESDAY

DC TRANSIENTS


 ③ Transients

$$\checkmark i_L = i(\infty) - [i(\infty) - i(0)] e^{-t/\tau}$$

$$\checkmark v_C = v(\infty) - [v(\infty) - v(0)] e^{-t/\tau}$$

 ④ AC transient

$$i_L(t) = \frac{V}{R}$$

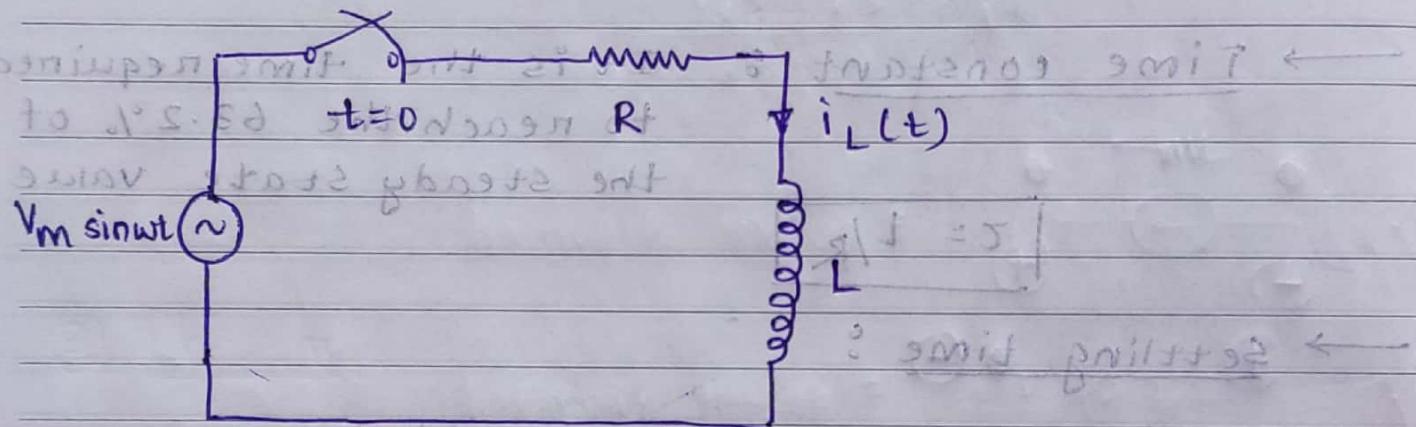

$$\text{Using KVL, } \frac{V}{R} + \frac{L di_L}{dt} = V_m \sin \omega t$$

$$L \frac{di_L}{dt} + R i_L = V_m \sin \omega t \quad (1)$$

$$i_L(t) = C.F. + P.I.$$

Complementary Function
(Transient)

Particular Integral
(Steady-state)

For P.I.

Let $i_L = I_1 \sin \omega t + I_2 \cos \omega t$,
put in eqn (1) and solve.

02 February 2018

WK	M	T	W	T	F	S	S
05				1	2	3	4
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

Wk 03 • 017 Day

WEDNESDAY

17

Further $i(0) = 0$; find A

$$\Rightarrow i_L(t) = \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \left[\sin \phi e^{-\frac{Rt}{L}} + \sin(\omega t - \phi) \right]$$

Wk	M	T	W	T	F	S	S
05				1	2	3	4
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				


AC CIRCUITS

Wk 03 • 019 Day
FRIDAY

19

* 1-Φ AC voltage generation

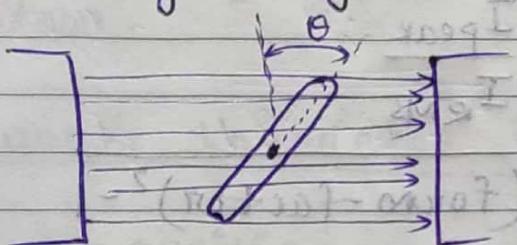(Fleming's right hand rule) generating principle



$$E = (2\pi n) BA N \sin \theta$$

$f = \frac{N \theta}{60}$ = No. of cycles per second $\times \frac{\text{revolution}}{\text{second}}$ $\times \text{No. of revolution per second}$

$$= 1 \times n = n \text{ (1-pole pair)}$$

$$= p \times n = np \text{ (p-pole pair)}$$

$$\boxed{f = p \times n} \quad (p = \text{pole pairs}; n = \text{rev/s})$$

$$f = p \times \left(\frac{N \theta}{60} \right) \rightarrow \delta f \text{ pm}$$

$$\text{no. of rev} = \frac{P}{2} \cdot \frac{N \theta}{60}$$

$$\Rightarrow \boxed{f = \frac{N \theta \cdot P}{120}}$$

* RMS and AVG. value

$$\rightarrow I_{\text{RMS}}^2 = \frac{1}{T} \int_0^{T/2} i^2(t) dt \quad (\text{consider full wave-form})$$

$$\rightarrow I_{\text{AVG.}} = \frac{1}{(T/2)} \int_0^{T/2} i(t) dt \quad (\text{consider half wave-form for symmetrical})$$

→ For unsymmetrical; consider full wave form

20

 Wk 03 • 020 Day
SATURDAY

AC CIRCUITS

	Jan	Feb	Mar	Apr	May	Jun	Jul	Aug	Sep	Oct	Nov	Dec
Wk	1	2	3	4	5	6	7	8	9	10	11	12
01	1											
02	8	9	10	11	12	13	14					
03	15	16	17	18	19	20	21					
04	22	23	24	25	26	27	28					
05	29	30	31									

(a) Form factor = $\frac{I_{RMS}}{I_{AVG}}$ (> 1 , so that AC component is there)

(b) Peak factor = $\frac{I_{peak}}{I_{RMS}}$

(c) Ripple-factor = $\sqrt{(form\text{-factor})^2 - 1}$

$$\therefore V_{AC} = \sqrt{V_{RMS}^2 - V_{avg}^2}$$

and ripple factor = $\frac{V_{AC}}{V_{avg}}$

(3) Phasor (steady-state analysis)
not transients.

$V_m \sin(\omega t + \phi)$ \equiv $\underline{V_m} / \phi = \underline{V}$
(Time-domain representation)

21 Sunday $\frac{q}{R_i} \leftrightarrow \frac{s}{R}$ (Freq.-domain representation)

$\underline{X_L} \rightarrow j\omega L$

$\underline{X_C} \rightarrow \frac{1}{j\omega C}$ $= \frac{1}{j\omega C} I \leftarrow$

$\underline{I} = \frac{1}{j\omega C} I \leftarrow$

Scanned by CamScanner

Wk	M	T	W	T	F	S	S
05			1	2	3	4	
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				




22

→ While drawing phasor diagram, it is easier to take loop current when series else node voltage when parallel as reference phasor.

Network theorems in AC

- i) Superposition
- ii) Thevenin
- iii) Norton
- iv) Maxm. power transfer theorem

} directly applicable

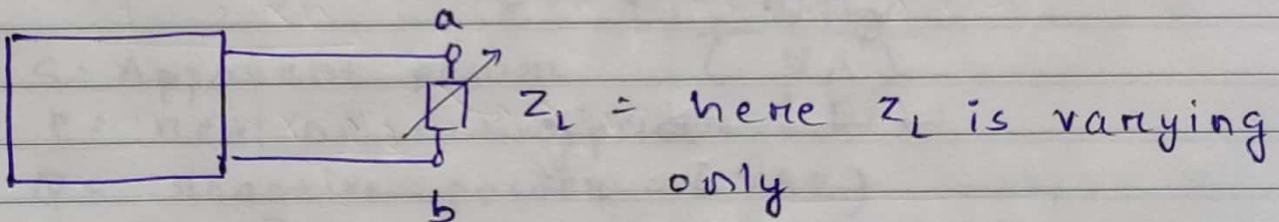

$$\boxed{z_L = z_{Th}^*}$$

$$R_L = R_{Th} \text{ and } X_L = -X_{Th}$$

$$\text{Power transferred} = \frac{V_{Th}^2}{4 R_{Th}}$$

If Z_L is purely resistive ; $R_L = 1z_{Th}$ and P_{max} has to be calculated from basics

Wk	M	T	W	T	F	S	S
05			1	2	3	4	
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

Wk 04 • 024 Day
WEDNESDAY

24

AC Power Analysis

$$\textcircled{1} \quad P(t) = V(t) i(t)$$

→ The instantaneous power (in watts) is the power at any instant of time.

→ The average power, in watts, is the average of the instantaneous power over one period.

$$(i > v) \text{ real power} = \frac{1}{2} \operatorname{Re}[V I^*] = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

→ A resistive load (R) absorbs power at all times, while a reactive load (L or C) absorbs zero power.

2) Apparent Power and power-factor

Units:

S = Apparent power (VA)

P = real or active power (W)

Q = reactive power (VAR)

$$\boxed{S = P + jQ}$$

$$\text{power factor} = (\text{pf}) = \frac{P}{\sqrt{S^2 - Q^2}} = \frac{P}{\sqrt{S^2 - Q^2}} = \cos(\theta_v - \theta_i)$$

$$\frac{S}{V} = \beta \Delta$$

$$\frac{P}{V} = \cos \theta_v$$

$$\frac{Q}{V} = \sin \theta_v$$

(leading)

(lagging)

$$\boxed{\frac{P}{V} = \beta \Delta}$$

$$\boxed{\frac{Q}{V} = \alpha \Delta}$$

	1	2	3	4	5	6	7
02	8	9	10	11	12	13	14
03	15	16	17	18	19	20	21
04	22	23	24	25	26	27	28
05	29	30	31				

'18 JANUARY


25

Wk 04 • 025 Day

THURSDAY

25 JANUARY 2023

$$(+i)(+v) = (+q) \quad (1)$$

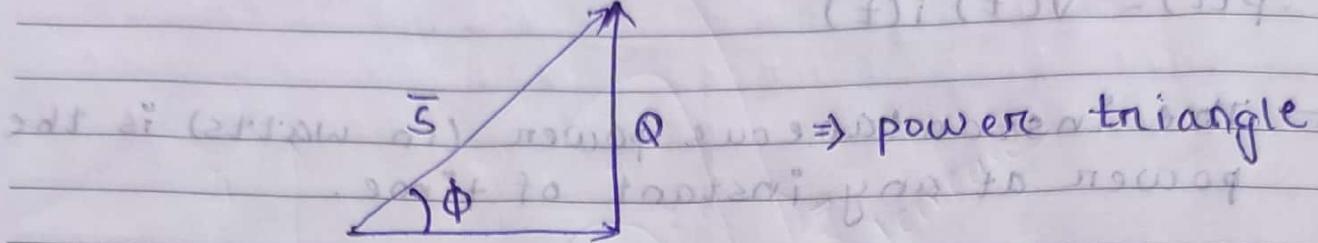

$Q = 0 \rightarrow$ pure resistive circuit


$Q < 0 \rightarrow$ capacitive circuit ($\theta_v < \theta_i$)

$Q > 0 \rightarrow$ inductive circuit ($\theta_v > \theta_i$)

While improvement of power factor,

P is to remain constant

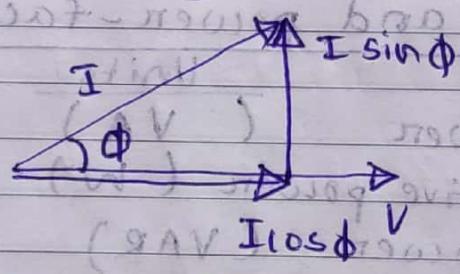Also $(I \cos\phi)$ and V should be constant



capacitor \rightarrow VAR generator (connected in parallel)
Inductor \rightarrow VAR absorber

$$\Delta Q = \frac{V_c^2}{X_C} \quad \text{or} \quad \Delta Q = \frac{V_L^2}{X_L}$$

$$\Delta Q = \omega C V_c^2$$

$$\Delta Q = \frac{V_L^2}{\omega L}$$

$$\left(\frac{\Delta Q}{\omega V_c^2} \right)$$

$$\left[L = \frac{V_L^2}{\omega \Delta Q} \right]$$

Wk	M	T	W	T	F	S	S
05				1	2	3	4
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				



Wk 04 • 026 Day
FRIDAY

26

* Conservation of AC Power

→ The complex, real, and reactive powers of the sources equal the respective sums of the complex, real, and reactive powers of the individual load.

(write S in a complex form)


→ Motor on half-load = apparent power is halved
 Motor on full-load = apparent power is complete or not changed.

Lagging : Current lags voltage
 (Inductive)

Yabru282

'18 JANUARY


27

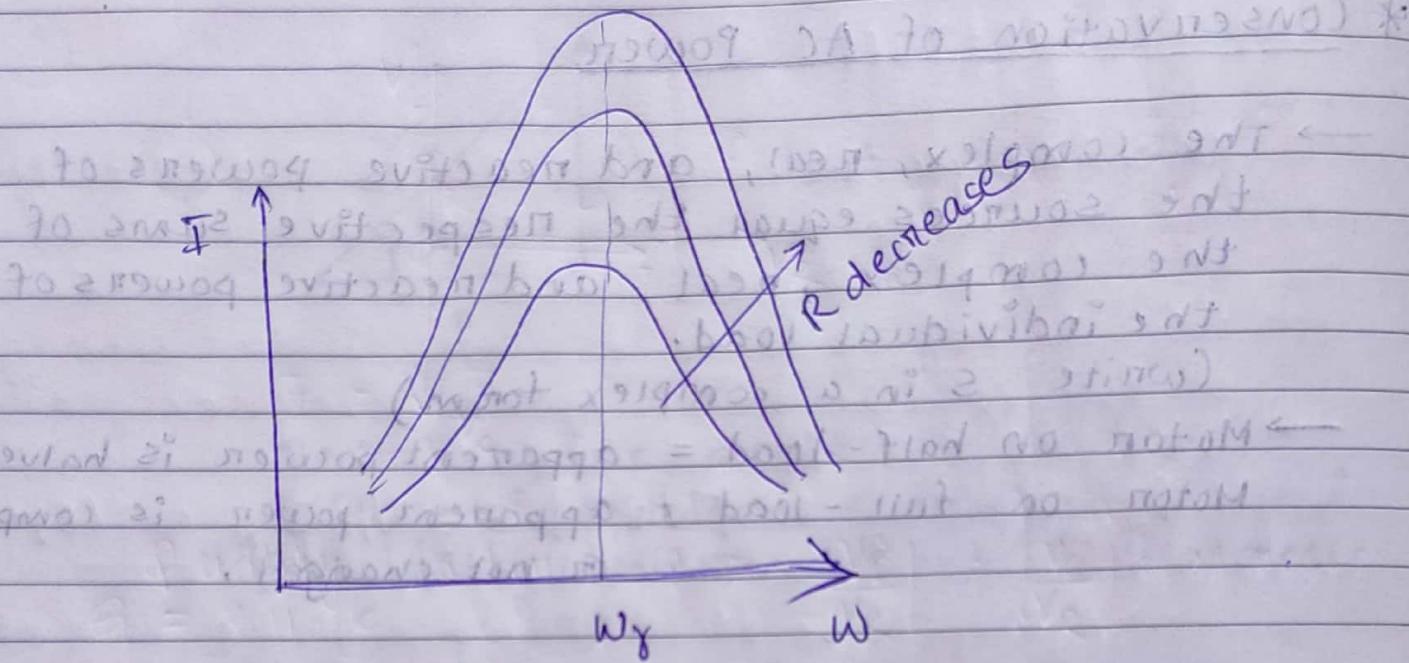 Wk 04 • 027 Day
SATURDAY

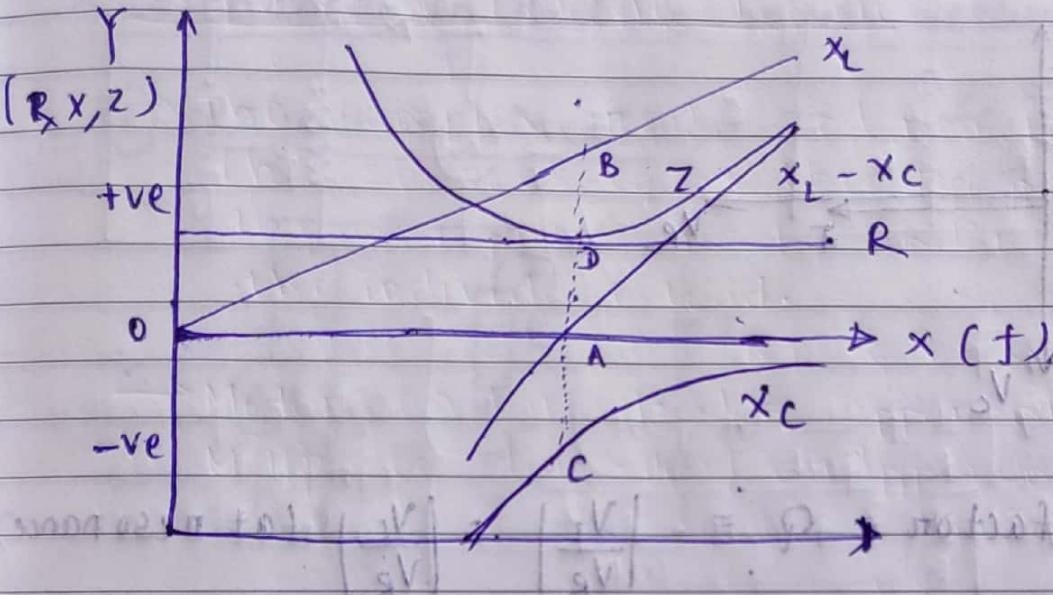
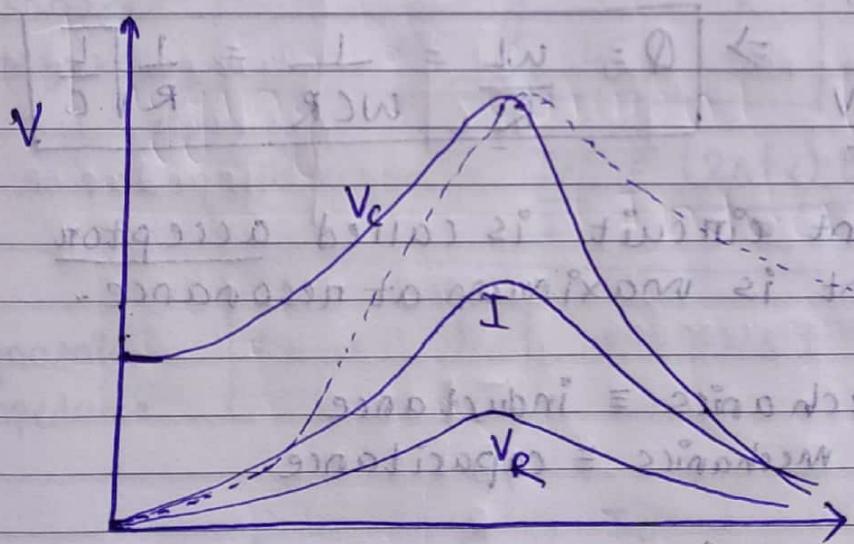
28 Sunday

Wk	M	T	W	T	F	S	S
05			1	2	3	4	
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

29

Wk 05 • 029 Day
MONDAYRESONANCE

Occurs when the peak energies stored by the inductor and the capacitor are equal and hence occurs resonance.



$$|V_C(f=0)| = |V_L(f=\infty)|$$

For R-L-C series resonance,

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$


01	1	2	3	4	5	6
02	8	9	10	11	12	13
03	15	16	17	18	19	20
04	22	23	24	25	26	27
05	29	30	31			

'18 JANUARY

30

 Wk 05 • 030 Day
TUESDAY

RESONANCE

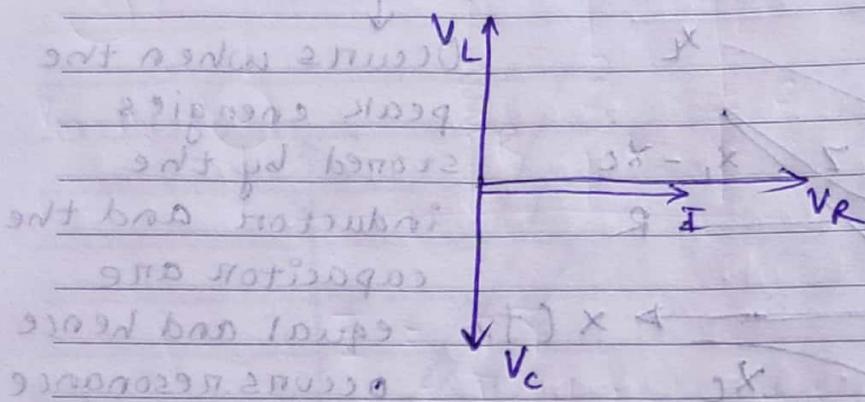

Quality factor $\Rightarrow Q = \frac{|V_L|}{|V_R|} = \frac{|V_C|}{|V_R|}$ (at resonance)

$Q = \text{Voltage magnification}$

Magnified voltage $= Q \times V$

$$\Rightarrow Q = \frac{\omega L}{R} = \frac{1}{WCR} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

- Series resonant circuit is called acceptor since current is maximum at resonance.
- Inertia in mechanics \equiv inductance elasticity in mechanics \equiv capacitance.



→ Natural frequency in an LC circuit $= 2\pi \frac{1}{\sqrt{LC}}$

In a LC circuit, the power taken from supply is simply that required to move this energy backwards and forwards between L and C through the resistance of the circuit.

Wk	M	T	W	T	F	S	S
05				1	2	3	4
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

* Resonance in RLC parallel networks

① Rejection circuit

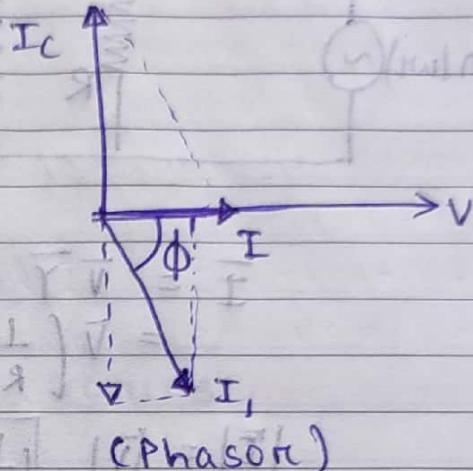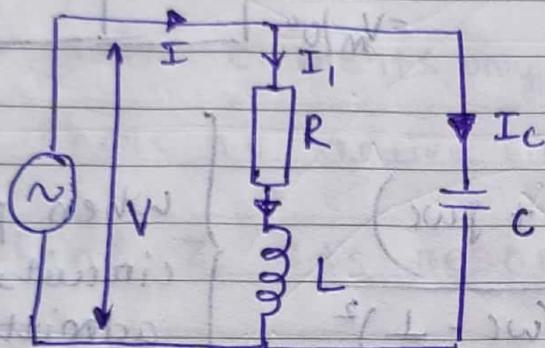




resonance frequency

$$f_{rc} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Ω -factor = $\frac{I_C}{I} = \frac{(2\pi f_\delta) L}{R}$

dynamic impedance

$$Z_n = \frac{L}{CR}$$

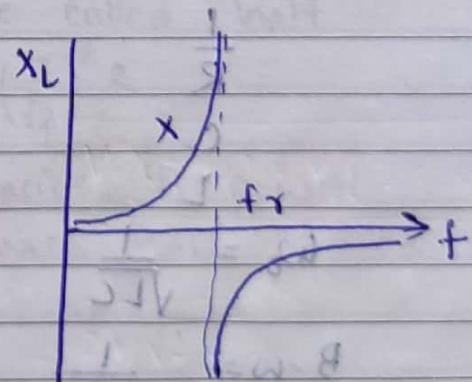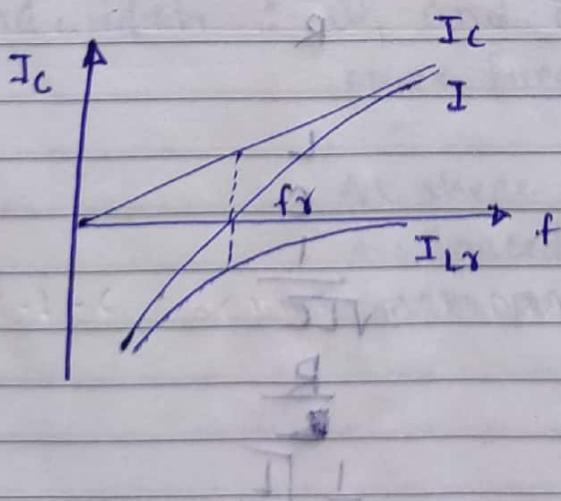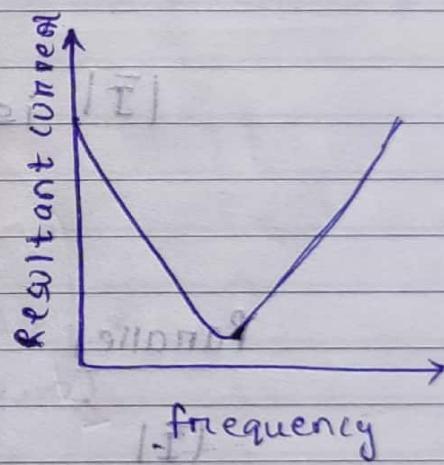


01

Wk 05 • 032 Day

THURSDAY

	1	2	3	4
W	5	6	7	8
05	12	13	14	15
06	19	20	21	22
07	26	27	28	

(2)

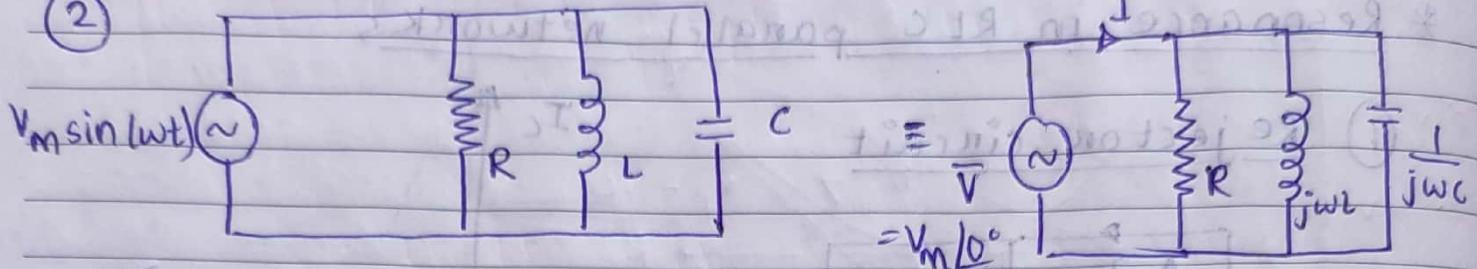

$$\bar{I} = \bar{V} \bar{Y}$$

$$= \bar{V} \left(\frac{1}{R} + \frac{1}{j\omega L} + j\omega C \right)$$

$$|\bar{I}| = |\bar{V}| \sqrt{\left(\frac{1}{R}\right)^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}$$

when parallel circuit, use admittance

$$|\bar{I}|$$

is minm.

$$\omega = \frac{1}{\sqrt{LC}}$$

When series circuit, use impedance

Parallel
replacement
Series

$$(\bar{I})$$

$$|\bar{V}|$$

$$\frac{1}{R}$$

$$C$$

$$L$$

$$|\bar{V}|$$

$$|\bar{I}|$$

$$R$$

$$L$$

$$C$$

$$\frac{1}{\sqrt{LC}}$$

$$\frac{1}{R}$$


$$\frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$B - w = \frac{1}{RC}$$


$$Q = R \sqrt{\frac{C}{L}}$$

W	K	M	T	W	T	F	S	S
09				1	2	3	4	
10	5	6	7	8	9	10	11	
11	12	13	14	15	16	17	18	
12	19	20	21	22	23	24	25	
13	26	27	28	29	30	31		

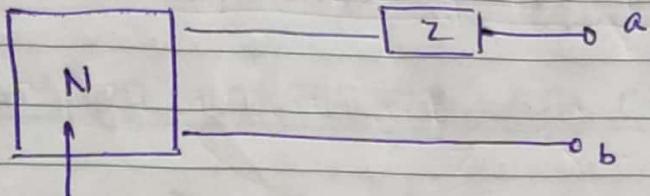

passive elements only
(hence no active elements)

→ Find Z s.t. resonance occurs.

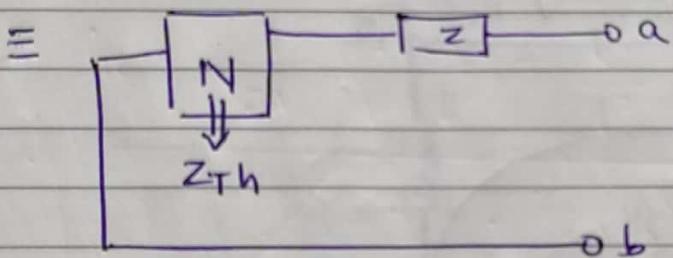

$$Z_{Th} = R_{Th} + j X_{Th} \quad ; \quad Z = R + j X$$

For $X_{Th} = -X \quad ; \quad R \in [0, \infty)$

→ Bandwidth : ω_1 and ω_2 are called half power frequencies $\left(\frac{I}{\sqrt{2}}\right)^2 R$

At these frequencies, the power dissipated becomes half of the max. power.

Wk 06 • 036 Day
MONDAY


05

THREE PHASE

CIRCUITS

* Advantage of 3- ϕ AC circuit

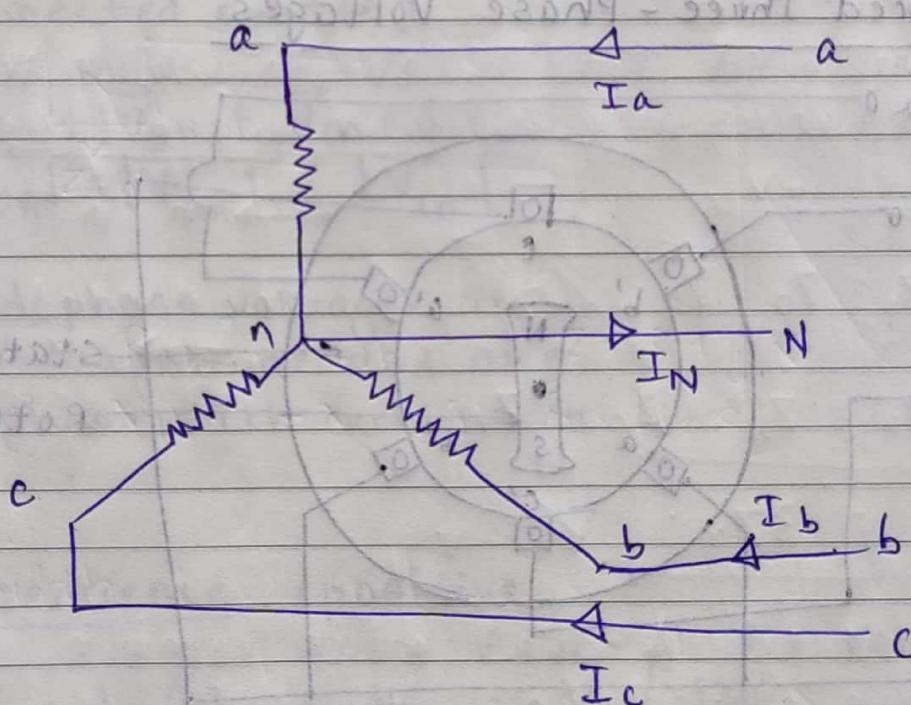- Bulk amount of power can be transmitted with reduced cost.
- Instantaneous power in a three-phase system can be constant.
- All the industrial heavy drives are of 3- ϕ in nature.



- | | | |
|---|----------------------------------|--------------|
| ① | V_{an} = Line to phase voltage | w.r.t supply |
| ② | V_{ab} = Line to line voltage | |
| ③ | V_{an} = Phase voltage | |
| ④ | I_{an} = Line current | |
| ⑤ | I_{an} = Phase current | |

Trick:

$$P = \frac{L}{\sqrt{3}} \quad \checkmark$$


THREE PHASE

05	6	7	8	1	2	3
06	5	6	7	8	9	10
07	12	13	14	15	16	17
08	19	20	21	22	23	24
09	26	27	28			

- Household : a single-phase three-wire system
- Polyphase : circuits or systems in which the ac sources operate at the same frequency but different phases.

In three phase system, it is produced by a generator consisting of three sources having the same amplitude and frequency but out of phase with each other by 120° .

* Balanced Three-Phase Voltages

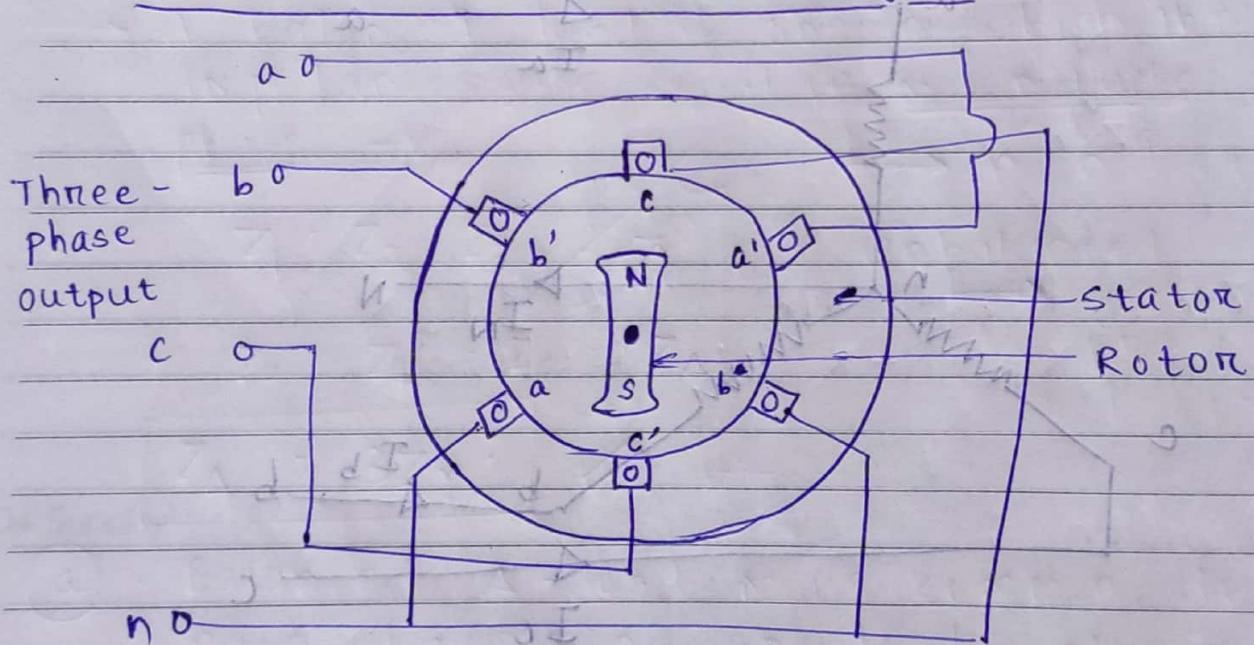


Three phase ac generator (alternator)

A typical three-phase system consists of three voltage sources connected to loads by three or four wires - the voltage sources can be either wye-connected or delta-connected.


Wk	M	T	W	T	F	S	S
09				1	2	3	4
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	

Wk 06 • 038 Day

WEDNESDAY

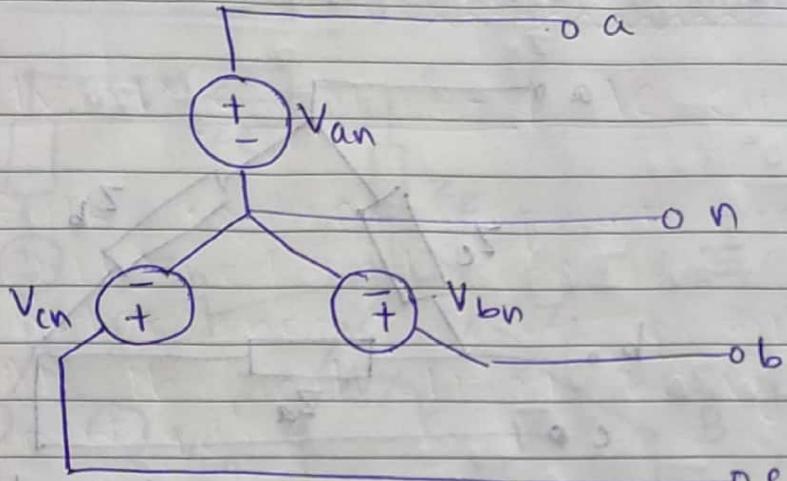

(Y-connected source)

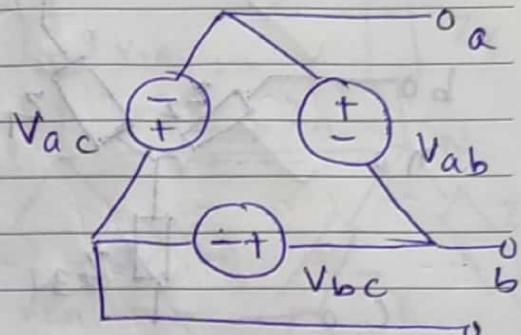

(\Delta-connected source)

phase voltage

$$\vec{V}_{an} + \vec{V}_{bn} + \vec{V}_{cn} = 0$$

$$|V_{an}| = |V_{bn}| = |V_{cn}|$$

→ Balanced phase voltages are equal in magnitude and are out of phase with each other by 120° .

(A) abc sequence / positive

$$V_{an} = V_p [0^\circ] \quad V_{bn} = V_p [-120^\circ]$$

$$V_{cn} = V_p [-240^\circ] = V_p [120^\circ]$$

(B) acb sequence / negative

$$V_{an} = V_p [0^\circ] \quad V_{bn} = V_p [120^\circ]$$


$$V_{cn} = V_p [120^\circ]$$

08


Wk 06 • 039 Day

THURSDAY

Loads

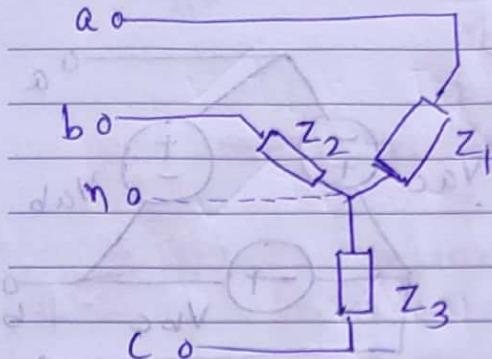 a₀


(Y-connected load)

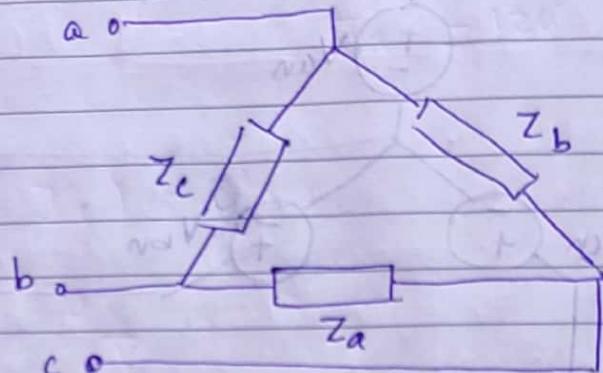 a₀


(Δ-connected load)

→ A balanced load is one in which the phase impedances are equal in magnitude and in phase.

↳ in induction motor

$$Z_1 = Z_2 = Z_3 = Z_Y$$

unbalanced

$$Z_a = Z_b = Z_c \neq Z_\Delta$$

↳ generally
practical
purposes

$$\boxed{Z_\Delta = 3Z_Y} \quad \checkmark$$

(a)

Balanced Δ-load more common, due to ease of replacing any load, also in wye-load, neutral may not be accessible.

(b)


Δ-connected sources are not common in practice because of the circulating current that will result in delta-mesh if voltages are slightly unbalanced.

Wk	M	T	W	T	F	S	S
09			1	2	3	4	
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	

Wk 06 • 040 Day
FRIDAY

09

* Balanced Wye-Wye Connection

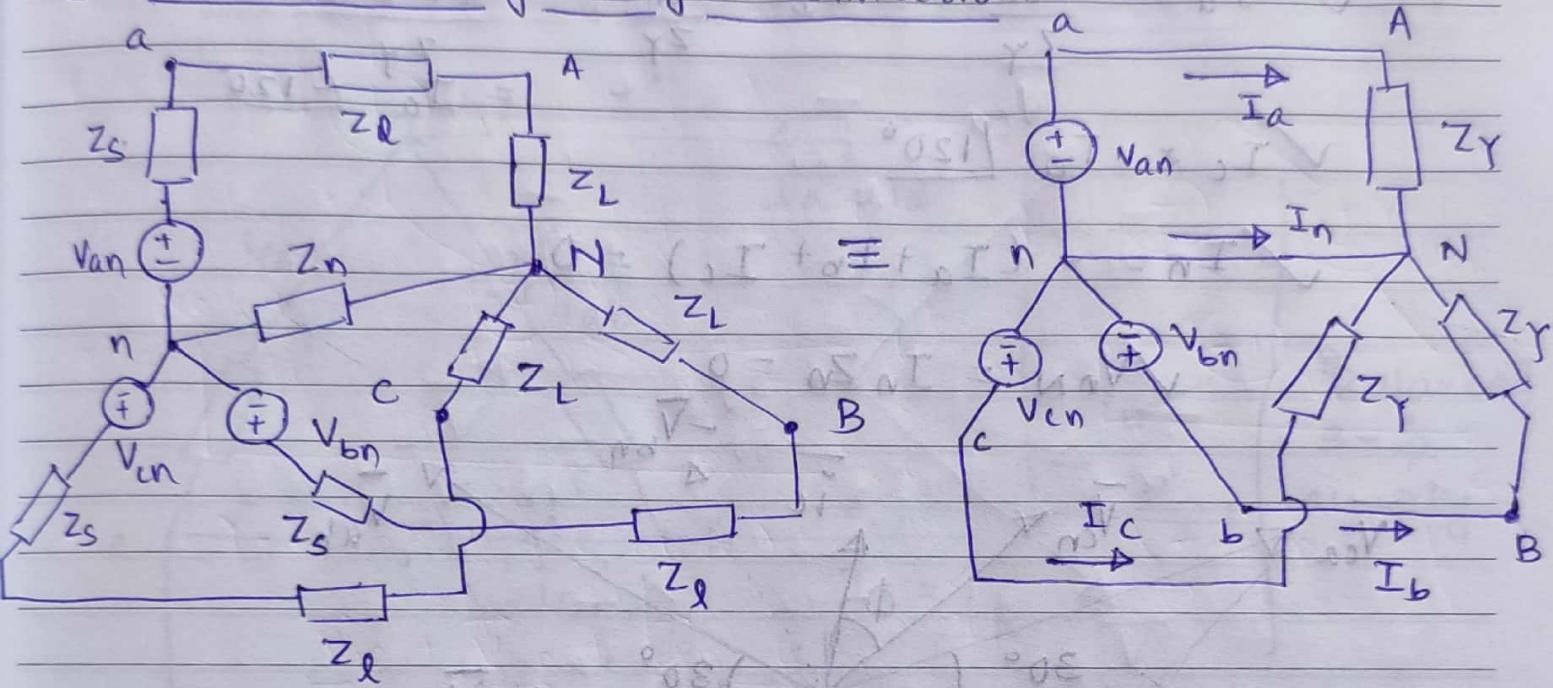

Phase voltages: $V_{An} = V_p \angle 0^\circ$; $V_{bn} = V_p \angle -120^\circ$; $V_{cn} = V_p \angle 120^\circ$

The line to line voltages or simply line voltages

$$V_{ab} = V_{An} - V_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ$$

$$V_{bc} = \sqrt{3} V_p \angle 30^\circ$$

$$V_{ca} = \sqrt{3} V_p \angle -210^\circ$$

$$\boxed{\frac{V_L}{\sqrt{3}} = V_p}$$

$$\text{and } \boxed{|I_L| = |I_p|}$$

Wk	M	T	W	T	F	S	S
05				1	2	3	4
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

'18 FEBRUARY

10

Wk 06 • 041 Day


SATURDAY

$$\checkmark I_a = \frac{V_{an}}{Z_Y} \quad \checkmark I_b = \frac{V_{bn}}{Z_Y} = \frac{V_{an} \angle 120^\circ}{Z_Y} \\ = I_a \angle 120^\circ$$

$$\checkmark I_c = I_a \angle 120^\circ$$

$$\checkmark I_n = -(I_a + I_b + I_c) = 0.$$

$$\checkmark V_{nN} = I_n Z_n = 0$$

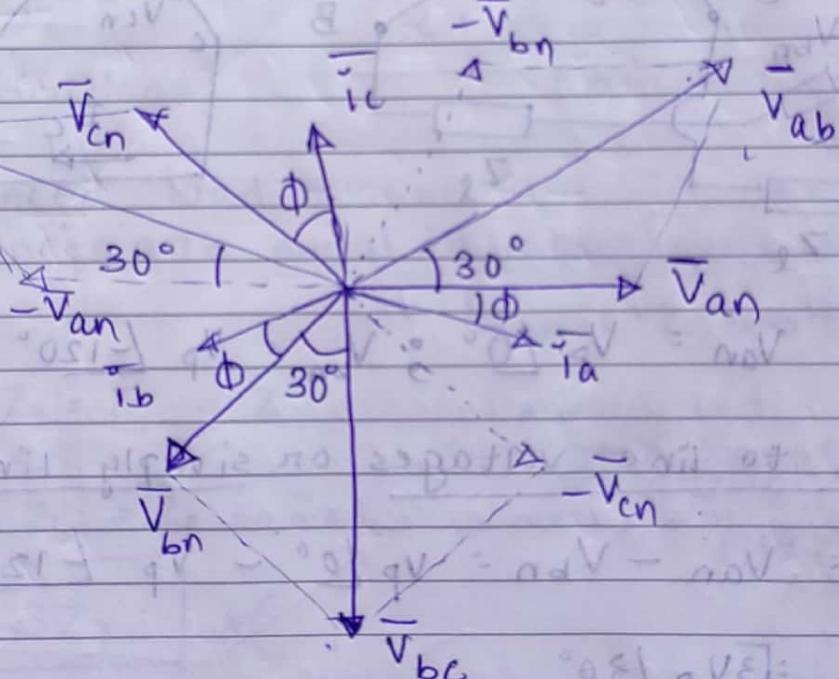

11 Sunday

$$qT = \sqrt{T^2 - b^2}$$


$$qV = \sqrt{V^2 - E^2}$$

Wk/M	T	W	T	F	S	S
09			1	2	3	4
10	5	6	7	8	9	10
11	12	13	14	15	16	17
12	19	20	21	22	23	24
13	26	27	28	29	30	31

 Wk 07 • 043 Day
MONDAY

12

* Balanced Wye - Delta Connection

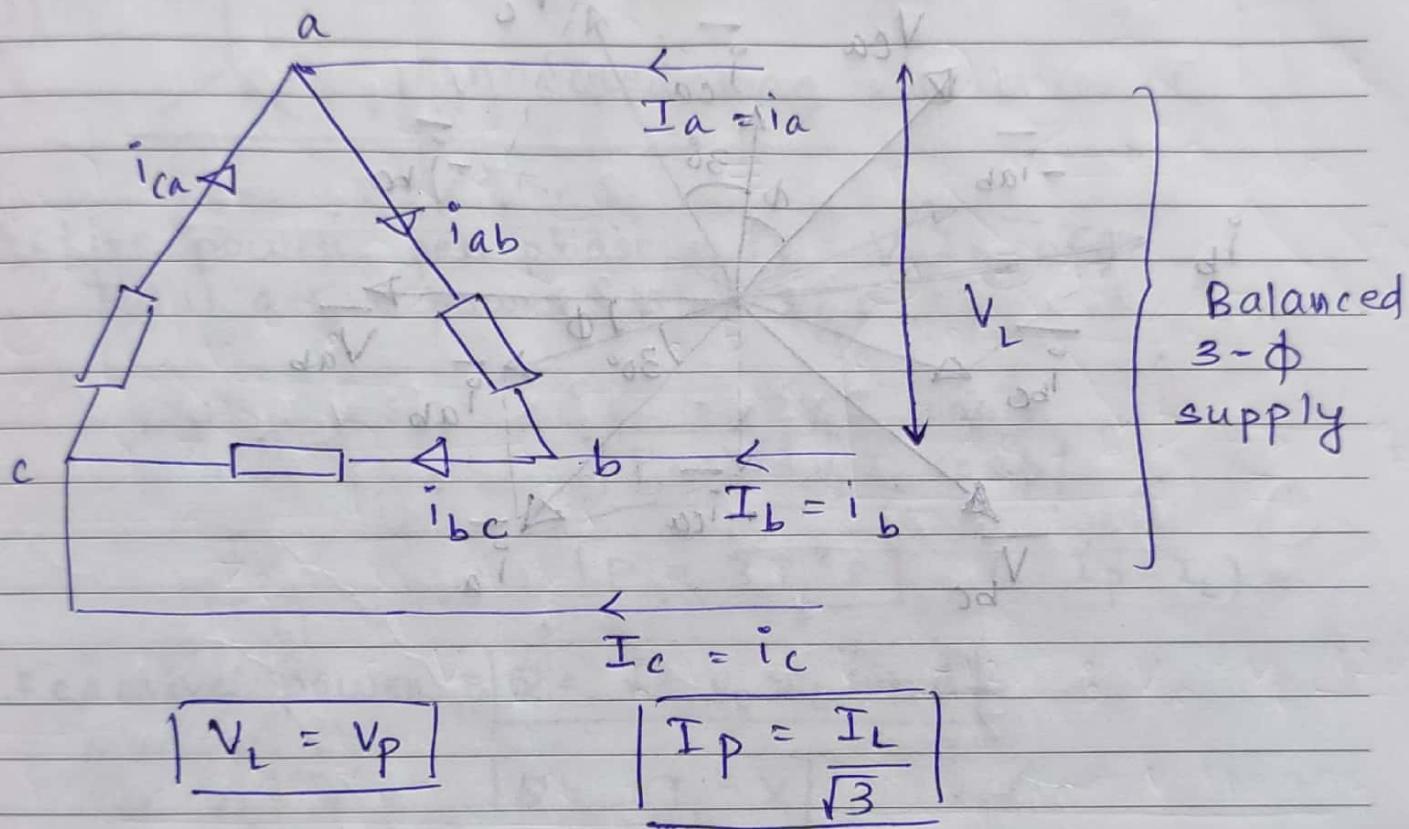

$$\bar{i}_a = \bar{i}_{ab} - \bar{i}_{ca} = \sqrt{3} |I_p| \angle (30 + \phi)$$


$$\bar{i}_b = \sqrt{3} |I_p| \angle (-150 + \phi)$$

$$\bar{i}_c = \sqrt{3} |I_p| \angle 90 - \phi$$

Wk	M	T	W	F	S
05				1	2 3 4
06	5	6	7	8 9 10 11	
07	12	13	14	15 16 17 18	
08	19	20	21	22 23 24 25	
09	26	27	28		

'18 FEBRUARY

13

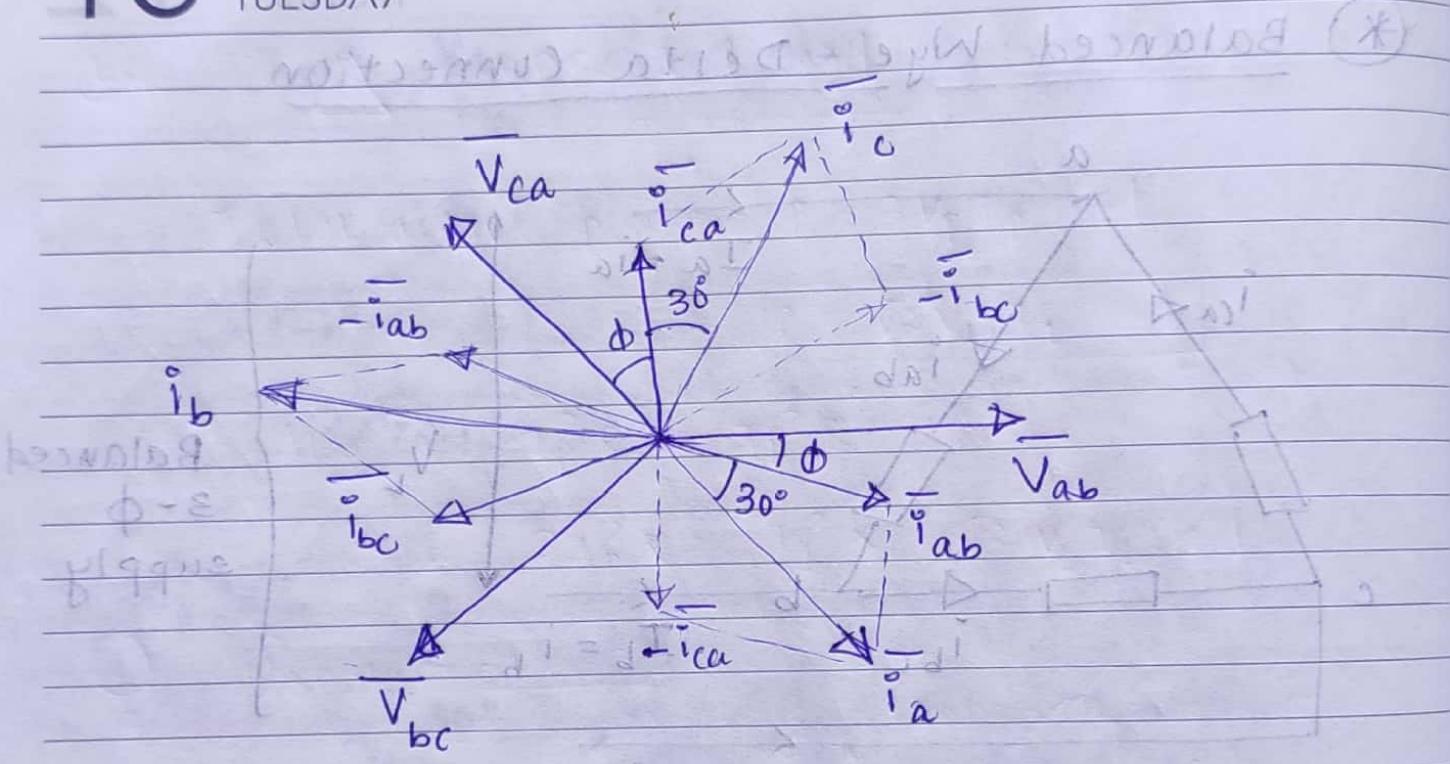 Wk 07 • 044 Day
TUESDAY


$$\left[\frac{\sqrt{3}I}{\sqrt{3}} = qI \right] \quad \left[qV = \sqrt{3}V \right]$$

$$(\phi + 30^\circ) \rightarrow |qI| \sqrt{3}V = \sqrt{3}I = \sqrt{3}I$$

$$(\phi + 30^\circ) \rightarrow |qI| \sqrt{3}V = \sqrt{3}I$$

$$\phi - 30^\circ \rightarrow |qI| \sqrt{3}V = \sqrt{3}I$$


Wk/M	T	W	T	F	S	S
09			1	2	3	4
10	5	6	7	8	9	10
11	12	13	14	15	16	17
12	19	20	21	22	23	24
13	26	27	28	29	30	31

Wk 07 • 045 Day
WEDNESDAY

14

* 3 - φ power

(a)

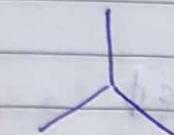

- connected load

Active power per phase = $P_p = V_p I_p \cos \phi$ Total active power $P = 3 P_p$

$$\boxed{P = \sqrt{3} V_L I_L \cos \phi}$$

$$\boxed{P = 3 I_L^2 R} \quad (\because I_p = I_L)$$

Reactive power = $\boxed{Q = \sqrt{3} V_L I_L \sin \phi}$

$$\boxed{Q = 3 I_L^2 X}$$

Using complex power concept -

$$\overline{S}_p = \overline{V}_p \cdot \overline{I}_p^*$$

$$\overline{V}_p = |V_p| \angle 0$$

$$\overline{I}_p^* = |I_p| \angle \phi \Rightarrow \overline{S}_p = |V_p| |I_p| \angle \phi$$

$$\boxed{\overline{S}_p = \overline{P}_p + j \overline{Q}_p}$$

W	K	M	T	W	T	F	S	S
05					1	2	3	4
06	5	6	7	8	9	10	11	12
07	12	13	14	15	16	17	18	19
08	19	20	21	22	23	24	25	26
09	26	27	28					

'18 FEBRUARY

15

Wk 07 • 046 Day

THURSDAY

(b)


 Δ - connected load


 Total active power $P = 3V_p I_p \cos\phi$

$$P = \sqrt{3} V_L I_L \cos\phi$$

$$\text{Also } P = 3I_p^2 R = I_L^2 R$$

$$Q = 3I_p^2 X = I_L^2 X = \sqrt{3} V_L I_L \sin\phi$$

(c)

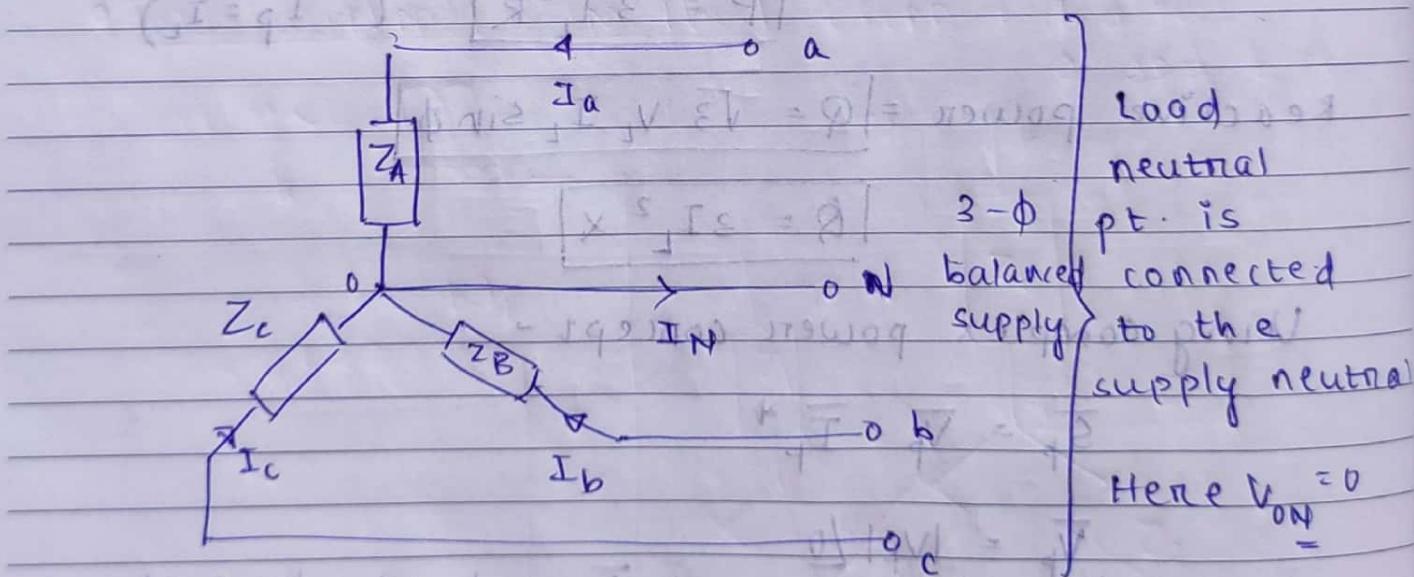Unbalanced case


→ neutral wire is connected, because across Z_A only voltage is V_{AN} .

→ test $V_{ON} \neq 0$, and p.d. b/w supply 3-φ and 3-φ load.

Wk	M	T	W	T	F	S	S
09			1	2	3	4	
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	

 Wk 07 • 047 Day
FRIDAY

16

$$I_a = \frac{(\bar{V}_{AN})}{Z_A}, \quad \bar{I}_b = \frac{\bar{V}_{BN}}{Z_B}, \quad \bar{I}_c = \frac{\bar{V}_{CN}}{Z_C}$$

$$P = |V_{AN}| |I_a| \cos \phi_a + |V_{BN}| |I_b| \cos \phi_b + |V_{CN}| |I_c| \cos \phi_c$$



$$\boxed{\bar{I}_N = \bar{I}_a + \bar{I}_b + \bar{I}_c}$$

If neutral point is not connected -

$$\bar{I}_a + \bar{I}_b + \bar{I}_c = 0$$

$$\Rightarrow (\bar{V}_{AN} - \bar{V}_{ON}) \cdot \bar{Y}_a + (\bar{V}_{BN} - \bar{V}_{ON}) \cdot \bar{Y}_b + (\bar{V}_{CN} - \bar{V}_{ON}) \cdot \bar{Y}_c = 0$$

$$\Rightarrow \bar{V}_{ON} = \frac{\bar{V}_{AN} \cdot \bar{Y}_a + \bar{V}_{BN} \cdot \bar{Y}_b + \bar{V}_{CN} \cdot \bar{Y}_c}{\bar{Y}_a + \bar{Y}_b + \bar{Y}_c}$$

$$\Rightarrow \boxed{\bar{V}_{ON} = \frac{\sum \bar{V}_p \cdot \bar{Y}_p}{\sum \bar{Y}_p}}$$

W	K	M	T	W	T	F	S
05				1	2	3	4
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

'18 FEBRUARY

17

WK 07 • 048 Day


SATURDAY



Three phase power measurements using two wattmeter

- The wye-source : used for long distance transmission of electric power. ($I^2 R$) = Resistive losses are minimum, since phase voltage and line voltage are higher, and so I is higher.
- The delta-source : when single-phase circuits are desired from 3-φ source, especially in residential wiring.

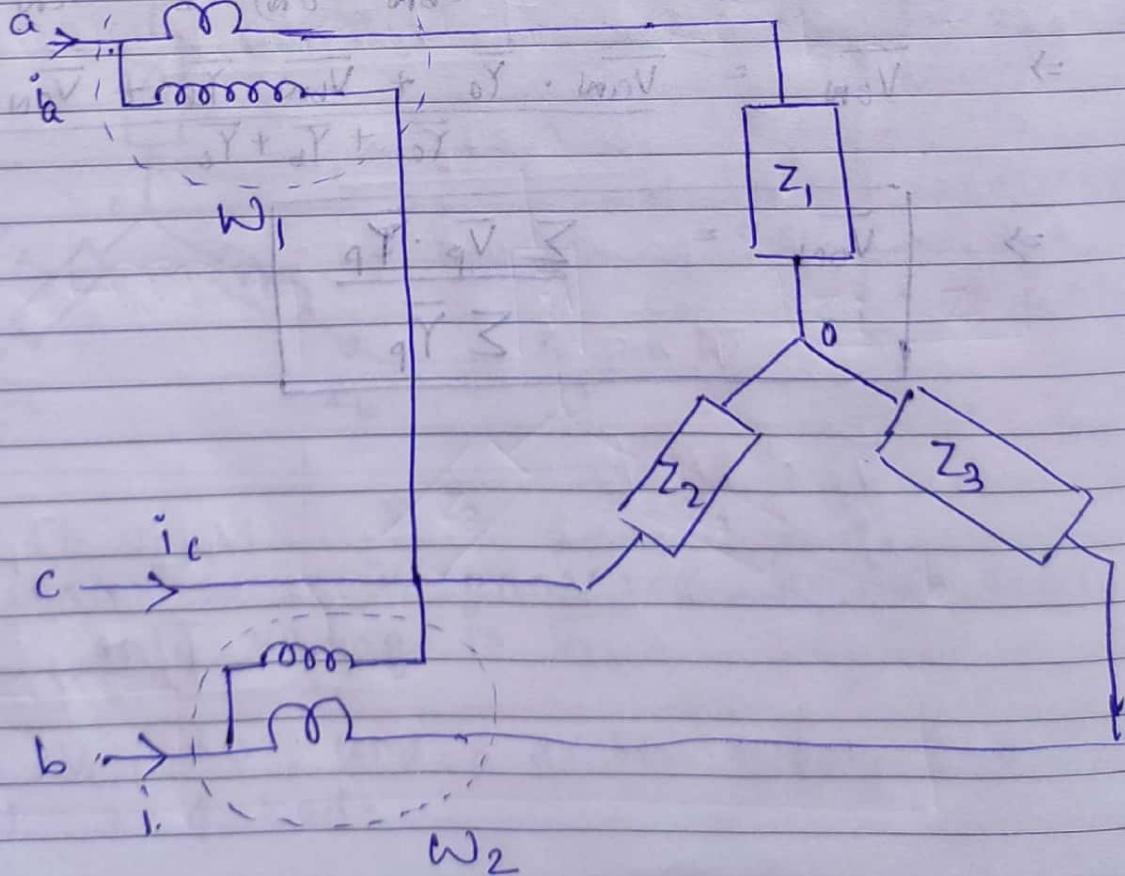- Two wattmeter method (Connected across a and b phases)



18 Sunday

Wk	M	T	W	T	F	S	S
09			1	2	3	4	
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	

FEBRUARY



SSP Notes

19

Wk 08 • 050 Day

MONDAY

instantaneous power -

$$w_1 = V_{ac}(t) \cdot i_a(t)$$

$$w_2 = V_{bc}(t) \cdot i_b(t)$$

Total instantaneous power -

$$W(t) = w_1(t) + w_2(t)$$

$$= V_{ac}(t) \cdot i_a(t) + V_{bc}(t) \cdot i_b(t)$$

$$V_{ac}(t) = V_{ao}(t) - V_{co}(t)$$

$$V_{bc}(t) = V_{bo}(t) - V_{co}(t)$$

$$W(t) = V_{ao}(t) i_a(t) + V_{bo}(t) i_b(t)$$

$$-(i_a + i_b)(t) V_{co}(t)$$

$$\rightarrow W(t) = V_{ao}(t) i_a(t) + V_{bo}(t) i_b(t) + i_c(t) V_{co}(t)$$

(Frequency of power = $\frac{\pi}{\omega}$)Avg. power consumed in load = $w = w_1 + w_2$

$$w_1 = |V_{ac}| |i_a| \cos(30^\circ - \phi)$$

$$w_2 = |V_{bc}| |i_b| \cos(30^\circ + \phi)$$

from phasor diagram

$$\rightarrow w_1 + w_2 = \sqrt{3} V_L I_L \cos \phi = \text{Active power}$$

$$\rightarrow \sqrt{3}(w_1 - w_2) = \sqrt{3}(V_L I_L \sin \phi) = \text{Reactive power}$$

\downarrow

subtract $w_1 - w_2$ or $w_2 - w_1$, so that
 $\sin \phi$ comes in expression


W	K	M	T	W	T	F	S	S
05						1	2	3
06	5	6	7	8	9	10	11	12
07	12	13	14	15	16	17	18	19
08	19	20	21	22	23	24	25	26
09	26	27	28					

$$\tan \phi = \frac{\sqrt{3}(\omega_1 - \omega_2)}{(\omega_1 + \omega_2)}$$

$$\cos \phi = \text{p.f.} = \frac{(\text{t})}{\sqrt{1 + 3(\omega_1 - \omega_2)^2}} = (\text{t}) \cdot \frac{1}{\sqrt{1 + 3(\omega_1 - \omega_2)^2}}$$

→ current wire must be connected along two phases. voltage wire across two phases correspondingly.

Wattmeters connected in a & c phase -

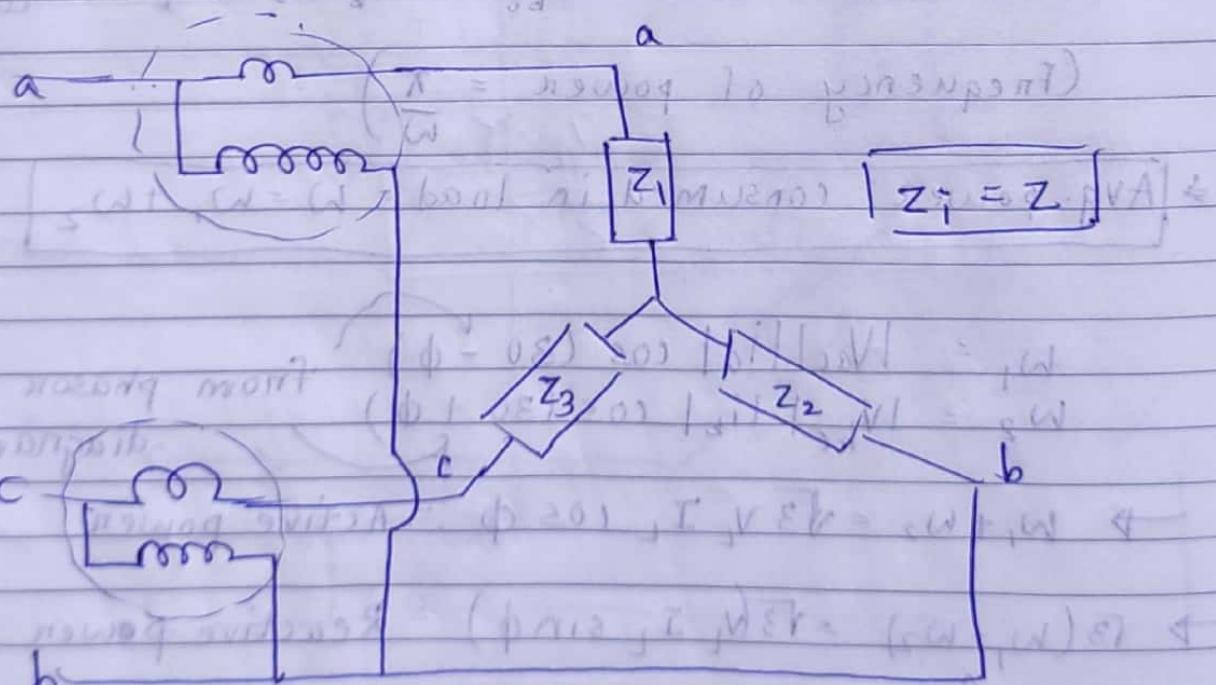

March 2018

03	Wk M	T	W	T	F	S	S
09				1	2	3	4
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	

 Wk 08 • 052 Day
 WEDNESDAY

→ When wattmeter connected to a & b phases -

✓ $\omega_1 = \omega_2 \Rightarrow \cos \phi = 1 \Rightarrow$ resistive pure load

✓ $\omega_1 > \omega_2 \Rightarrow \tan \phi > 0 \Rightarrow$ inductive load

(\therefore reactive power $= \sqrt{3}(\omega_1 - \omega_2)$
 $= (+) \text{ve}$
 \Rightarrow power absorbed (VAR))

✓ $\omega_1 < \omega_2 \Rightarrow \tan \phi < 0 \Rightarrow$ capacitive load

(\therefore reactive power $= \sqrt{3}(\omega_1 - \omega_2)$
 $= (-) \text{ve}$
 \Rightarrow power supplied (VAR))

FEBRUARY

March 2018

Wk	M	T	W	T	F	S	S
09			1	2	3	4	
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	

MAGNETIC CIRCUITS

Wk 08 • 054 Day
FRIDAY

23

- Magnetic field intensity = H
- Magnetic flux density = B

(1) Magneto motive force (mmf)

$$\boxed{mmf = N_i I = H_c l_0}$$

N_i = algebraic sum of the ampere-turns of all the windings.

H_c can be found from the right hand rule, similar to Φ , B .

$$(2) \boxed{B = \mu H} \quad (\mu = \text{permeability})$$

$= \mu_r \mu_0$

μ is property of region in which the field exists.

→ μ_r is assumed constant though it varies appreciably with magnetic flux density.

(3) Magnetic flux

$$\boxed{\Phi = \int_S \vec{B} \cdot d\vec{a}} \quad (in webers)$$

$$\rightarrow \oint \vec{B} \cdot d\vec{a} = 0$$

S	S	S	S	S	S	S	S
05			1	2	3	4	
06	5	6	7	8	9	10	11
07	12	13	14	15	16	17	18
08	19	20	21	22	23	24	25
09	26	27	28				

'18 FEBRUARY

24

Wk 08 • 055 Day

SATURDAY

(4) Reluctance

$$R = \frac{l}{\mu A}$$

$$\rightarrow P = \text{Permeance} = \frac{1}{R} = \frac{\mu A}{l}$$

(*) Maxwell Equation

$$\oint H \cdot dl = \int J \cdot dA \quad \text{for } J = \text{ct. density}$$

 . & Assumption: $\frac{\partial D}{\partial t} \ll J \Rightarrow J + \frac{\partial D}{\partial t} \approx J$

$$\oint B \cdot da = 0$$

$$\frac{\partial D}{\partial t} H \propto = \frac{D}{\partial t} \quad (5)$$

D = electric

displacement

(*) Ohm's Law

$$B = \mu H \quad (1)$$

25 Sunday

$$\Phi = B \cdot A = \mu NI \cdot A$$

$$(encl. area) \quad \frac{l}{l} \quad [ab. S] = \Phi$$

$$NI = (\Phi) \left(\frac{l}{\mu A} \right)$$

$$mmf = \Phi \times R \quad (2)$$

Wk	M	T	W	T	F	S	S
09			1	2	3	4	
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	

Wk 09 • 057 Day
MONDAY


26

$$\rightarrow \text{Flux linkage} = \lambda = N\phi$$


$$\text{Self-inductance } L = \frac{N\phi}{I} = \frac{\mu N^2 A}{l} = \frac{\lambda}{I}$$

$$L = \frac{\mu N^2 A}{l} \quad (3)$$

\rightarrow Ckt. diagram

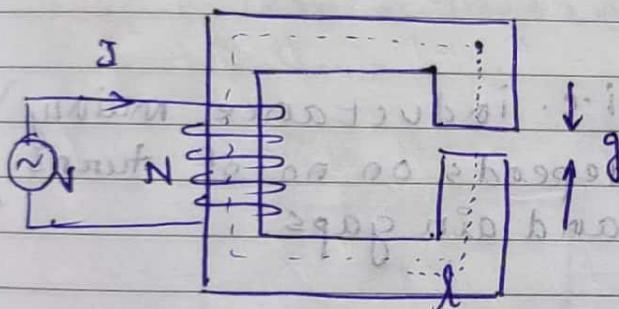

g = length of air gap.

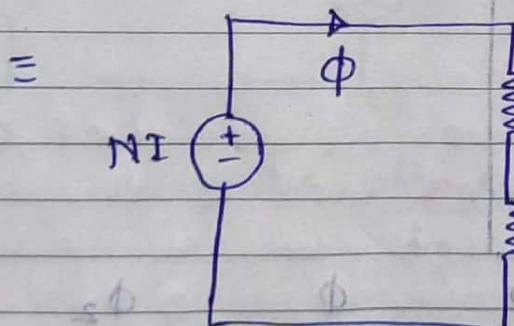

$$R_c = \frac{l}{\mu_c A_c} = \frac{l_c}{\mu_0 \mu_r A_c}$$

$$R_g = \frac{l_g}{\mu_0 A_g} = \frac{l_g}{\mu_0 A_g}$$

$A_g \approx (1.1 + 1.2) \times A_c$
 \rightarrow If no fringing effect,

$$A_c = A_g$$

$$R_c \ll R_g$$

Wk	M	T	W	T	F	S
05				1	2	3
06	5	6	7	8	9	10
07	12	13	14	15	16	17
08	19	20	21	22	23	24
09	26	27	28			

'18 FEBRUARY

27

Wk 09 • 058 Day

TUESDAY




$$\left| \frac{\phi}{I} = \frac{NI}{R_c + R_g} \approx \frac{NI}{R_g} \right| \quad (4)$$

$$L = \frac{N\phi}{I} = \frac{N^2}{R_c + R_g}$$

$$\left| L = \frac{N^2}{R_{total}} \right| \quad (5)$$

$$\approx \frac{N^2}{R_g}$$

(i.e. inductance mainly depends on no. of turns and air gaps)

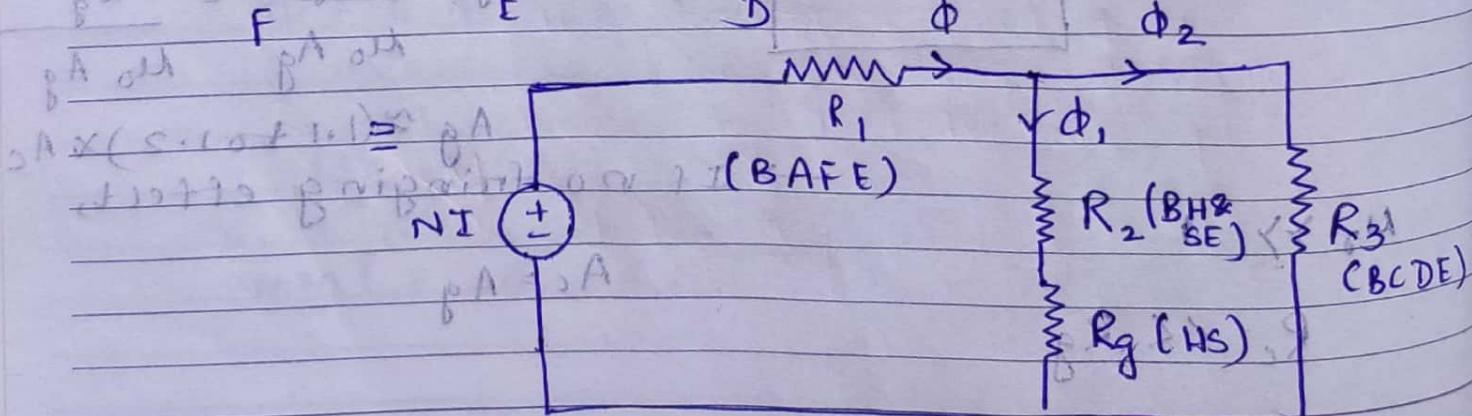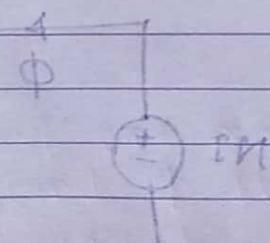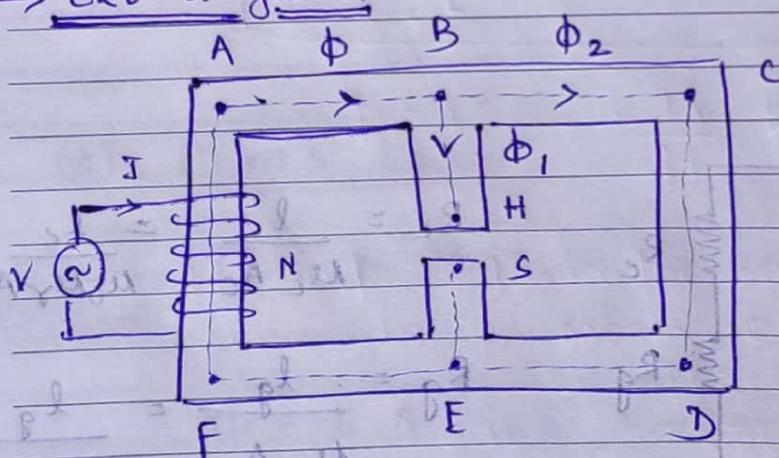→ Ckt. diagram


Wk 09 • 059 Day
 WEDNESDAY

28


March 2018

Wk	M	T	W	T	F	S	S
09			1	2	3	4	
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	




Mutual inductance

$$M_1 \approx \infty$$

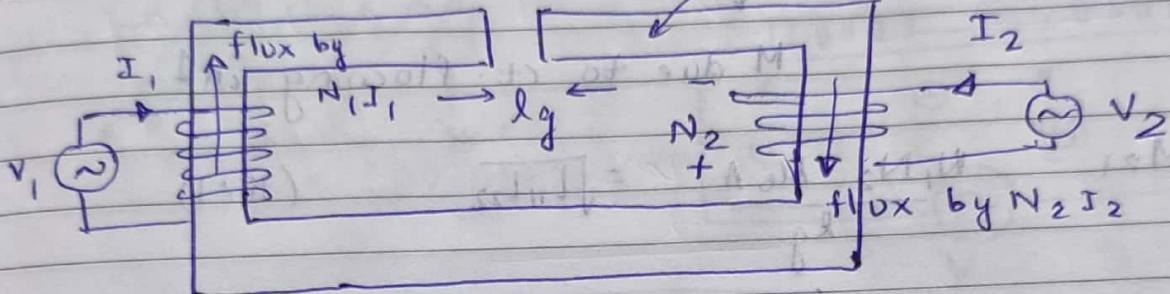

$$\text{mmf} = N_1 I_1 + N_2 I_2$$

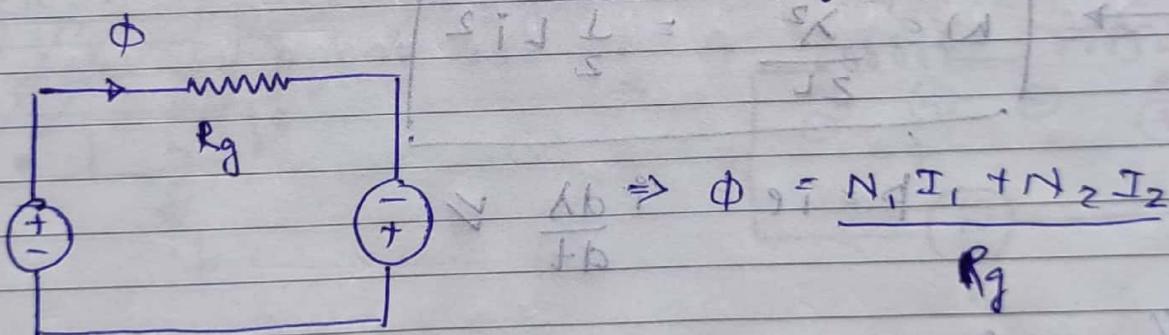~~permeance~~ Total reluctance = $R_c + R_g$
~~B not const~~ $= 0 + \frac{l_g}{\mu_0 A}$



~~total, I mmf has to maintain a unit of~~
~~Heaviside flux units~~ $\phi_{air} = \frac{\mu_0 A}{l_g} (N_1 I_1 + N_2 I_2)$

~~current I1 will result in flux in the core~~
~~current I2 will result in flux in the air gap~~
~~total flux in the core is same as in the air gap~~

Flux linkage in coil 1

of the core, $\propto N_1 \phi$

$$\lambda_1 = \left(\frac{N_1^2 \mu_0 A}{l_g} \right) I_1 + \left(\frac{N_1 N_2 \mu_0 A}{l_g} \right) I_2$$

$$\lambda_1 = L_{11} I_1 + M_{12} I_2 \quad (1)$$

\rightarrow Mutual inductance (due to ct. flowing in coil 2)

W	K	M	T	W	T	F	S	S
09				1	2	3	4	5
10	5	6	7	8	9	10	11	12
11	12	13	14	15	16	17	18	19
12	19	20	21	22	23	24	25	26
13	26	27	28	29	30	31		

'18 MARCH
01

Wk 09 • 060 Day

THURSDAY

$$\lambda_2 = L_{22} I_2 + M_{21} I_1$$

M due to ct. flowing in 1.

$$M_{12} = M_{21} = \frac{N_1 N_2 \mu_0 A}{l g} = \sqrt{L_{11} L_{22}} \quad (K=1)$$

In general $M_{12} = K \sqrt{L_{11} L_{22}}$

 $0 < K < 1$ = coupling factor

$$\rightarrow W = \frac{\lambda^2}{2L} = \frac{1}{2} L i^2$$

$$\text{E.S.H.T., principle} \Rightarrow i \frac{d\lambda}{dt} \rightleftharpoons$$

To find self-inductance of one mmf, short the other mmfs and find ϕ through itself when only it is present and then divide by I , In this situation find ϕ through other source (mmf) and multiply their N and divide by I of the mmf present to find M .

$$I \left(\frac{A \cdot M \cdot H \cdot N}{B} \right) + I \left(\frac{A \cdot M \cdot S \cdot H \cdot N}{B} \right) = IR$$



$$(A \cdot M \cdot H \cdot N) + (A \cdot M \cdot S \cdot H \cdot N) = IR$$

W	K	M	T	W	T	F	S	S
13	30						1	
14	2	3	4	5	6	7	8	
15	9	10	11	12	13	14	15	
16	16	17	18	19	20	21	22	
17	23	24	25	26	27	28	29	

Wk 09 • 061 Day
FRIDAY

02

• Cumulative coupling

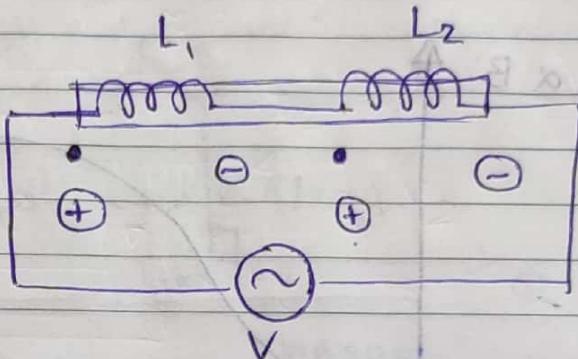
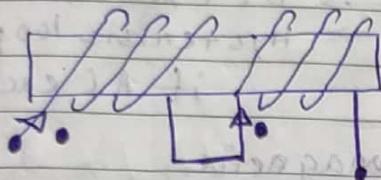


$$V = L_1 \frac{di}{dt} + M \frac{di}{dt} + L_2 \frac{di}{dt} + M \frac{di}{dt}$$

$$(L_1 + L_2 + 2M) \frac{di}{dt}$$

(Leq)

• Differential coupling

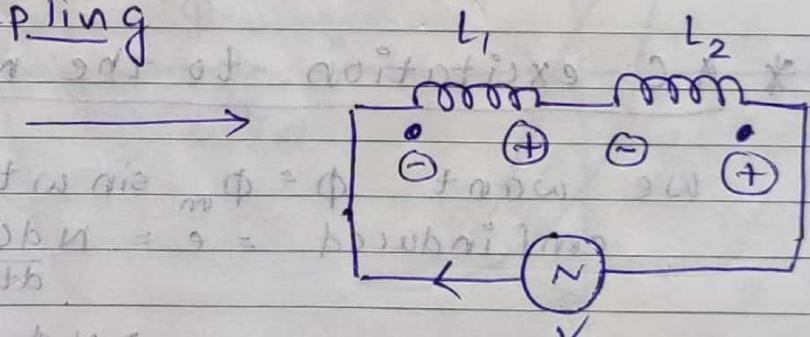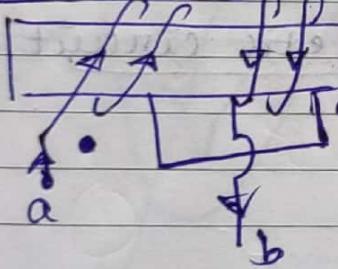

$$V = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} - M \frac{di}{dt} - M \frac{di}{dt}$$

$$(L_1 + L_2 - 2M) \frac{di}{dt}$$

(Leq)

nd multiply by N.


- due to dot, the other dot would be \oplus
- due to non-dot, the non-dot of other would be \oplus .

5	6	7	8	9	10	11	12	13	14	15	16	17
12	13	14	15	16	17	18	19	20	21	22	23	24
26	27	28	29	30	31							

03

 Wk 09 • 062 Day
SATURDAY

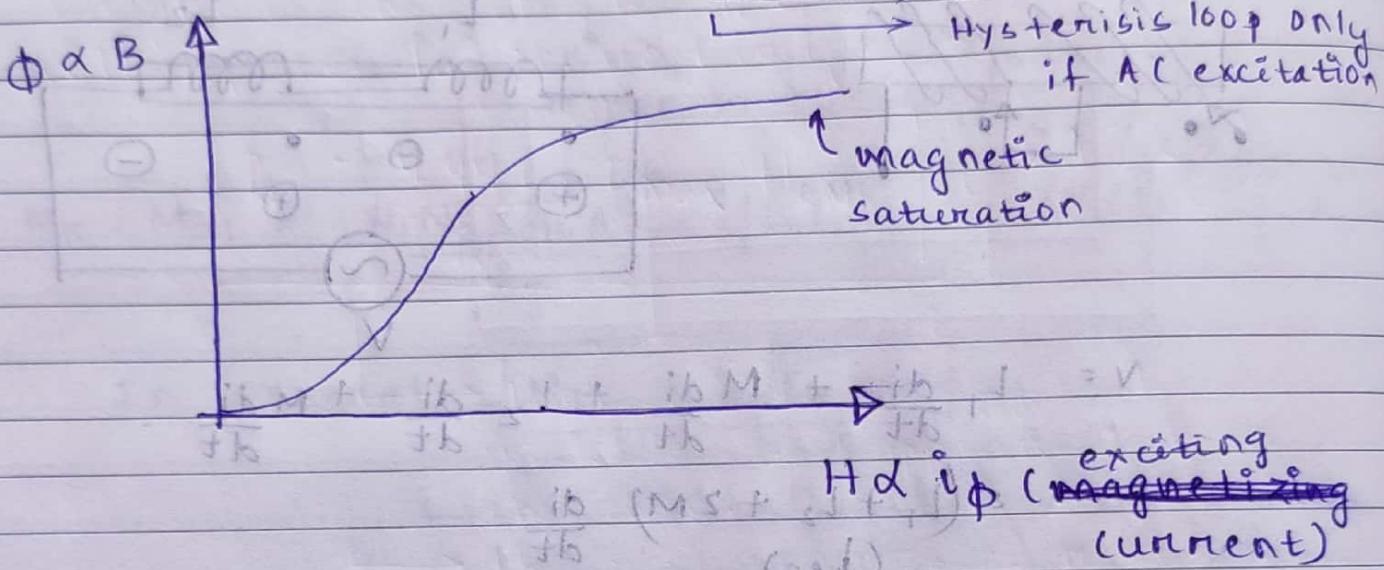* B-H characteristic or (DC) magnetization curve



* AC excitation to the magnetic circuit

$$\text{We want } \Phi = \Phi_m \sin \omega t$$

$$\text{emf induced} = e = N \frac{d\Phi}{dt}$$

$$= N \Phi_m \omega \cos \omega t$$

$$E_{\text{rms}} = \frac{N \Phi_m \omega}{\sqrt{2}}$$

$$E_{\text{rms}} = 4.44 \Phi_m N f$$


$$E_{\text{rms}} = 4.44 B_m A_c N f$$

⇒ e leads Φ by $\frac{\pi}{2}$


Wk	M	T	W	T	F	S	S
13	30					1	
14	2	3	4	5	6	7	8
15	9	10	11	12	13	14	15
16	16	17	18	19	20	21	22
17	23	24	25	26	27	28	29

Wk 10 • 064 Day
MONDAY

05

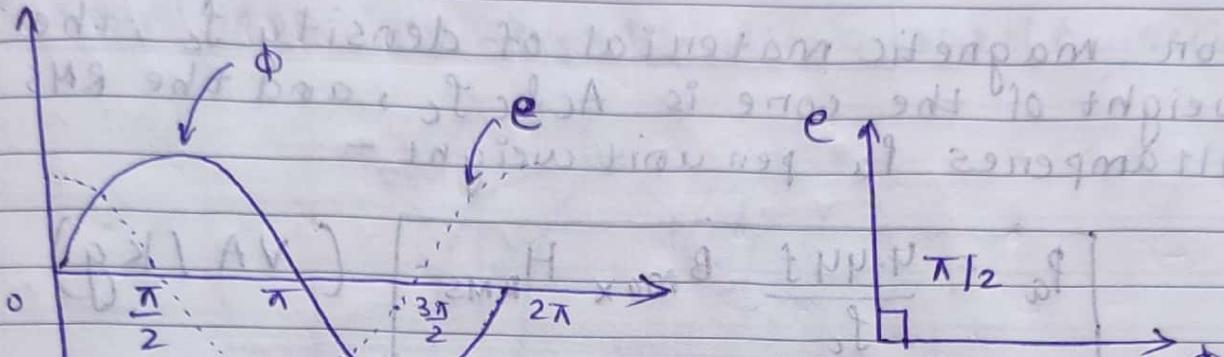

Phason

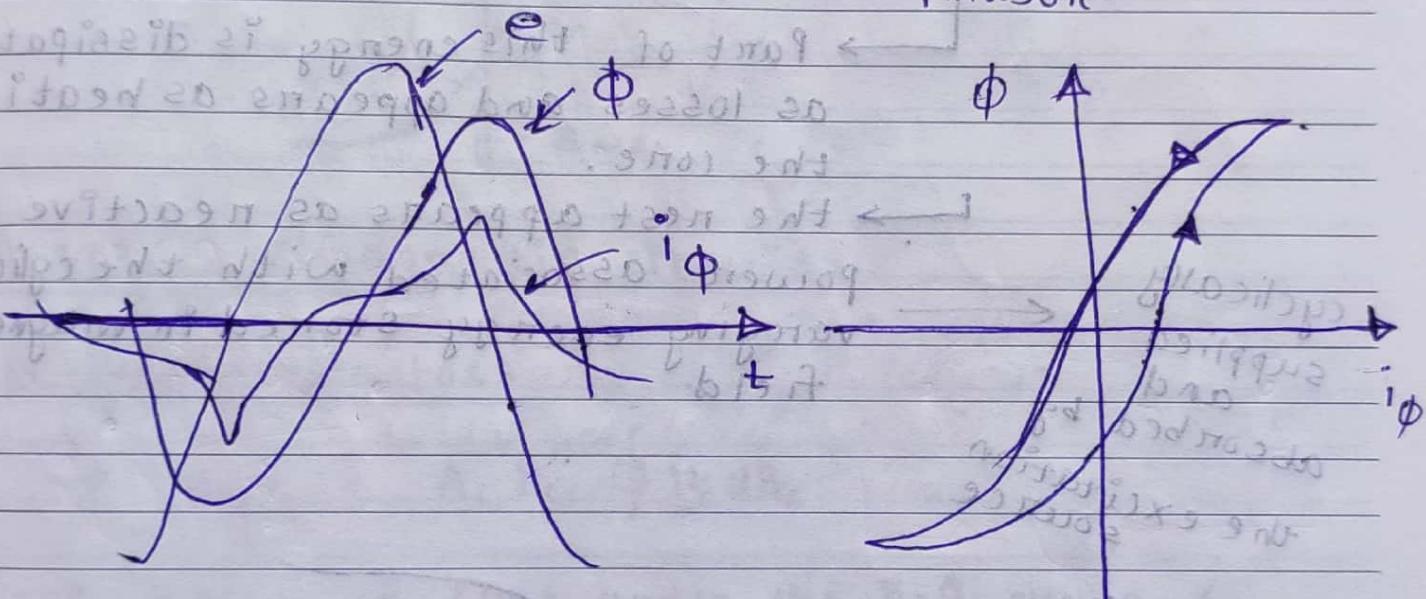

- $I_{\phi, \text{RMS}} = \frac{\Phi_c H_{\text{RMS}}}{N} = \text{exciting current}$ ($\text{A/m}^2 \text{A/mm}^2$)

- The RMS VA reqd. to excite the core to a specified flux density is

$$\begin{aligned}
 E_{\text{RMS}} I_{\text{RMS}, \phi} &= 4.44 B_m A_c N f \cdot \frac{\Phi_c H_{\text{RMS}}}{N} \\
 &= 4.44 A_c I_c f B_{\max.} H_{\text{RMS}}
 \end{aligned}$$

Wk	M	T	W	T	F	S	S
09				1	2	3	4
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	

'18 MARCH

06

 Wk 10 • 065 Day
TUESDAY


For magnetic material of density f_c , the weight of the core is $A \cdot h_c f_c$, and the RMS voltamperes P_a per unit weight -

$$P_a = \frac{4.44 f}{f_c} B_{\max} H_{\text{RMS}} \quad (\text{VA/kg})$$

Part of this energy is dissipated as losses and appears as heat in the core.

the rest appears as reactive power associated with the cyclically varying energy stored in magnetic field

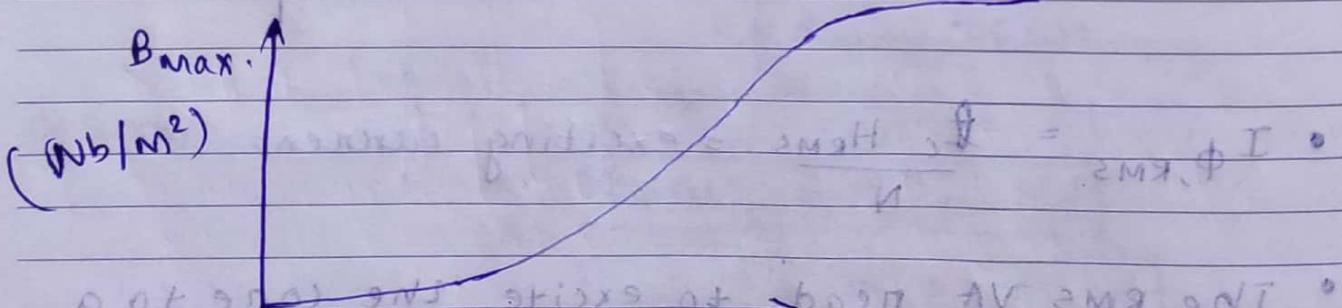cyclically supplied and absorbed by the excitation source



$$\text{H}_{\text{RMS}} = \frac{\pi M_{\text{RMS}} \Phi I}{A}$$

$$P_a(\text{RMS}) \quad (\text{VA/kg})$$

$\frac{d\Phi}{dt} = B_{\text{RMS}} A \cdot B_{\text{RMS}} = \Phi_{\text{RMS}} I_{\text{RMS}}$


04 April 2018

Wk/M	T	W	T	F	S	S
13	30			6	7	8
14	2	3	4	5	6	7
15	9	10	11	12	13	14
16	16	17	18	19	20	21
17	23	24	25	26	27	28
18						29

Wk 10 • 066 Day
WEDNESDAY

07

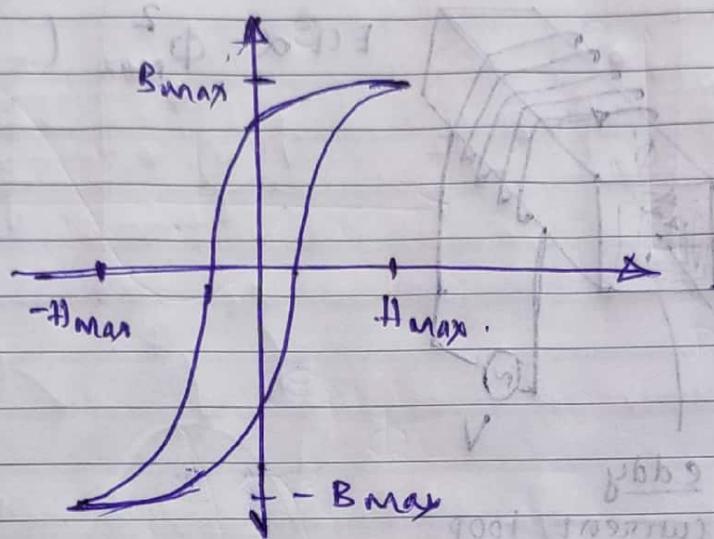B - H loop on hysteresis loop (AC excitation)



Losses in magnetic circuits

Hysteresis loss

$$\rightarrow H_{\text{Loss}} = A_c l_c \oint H d B_c$$

$\rightarrow H_{\text{Loss}} \approx \text{Area under the } B-A \text{ curve} \times \text{Volume of the core}$

$\rightarrow H_{\text{Loss}} \propto \text{Frequency of the applied excitation}$

$P_c = \text{core loss (in W/kg)}$



18 MARCH

08

Wk 10 • 067 Day


THURSDAY

SSP Notes

M	W	OS	2	3	4
10	5	6	7	8	9
11	12	13	14	15	16
12	19	20	21	22	23
13	26	27	28	29	30

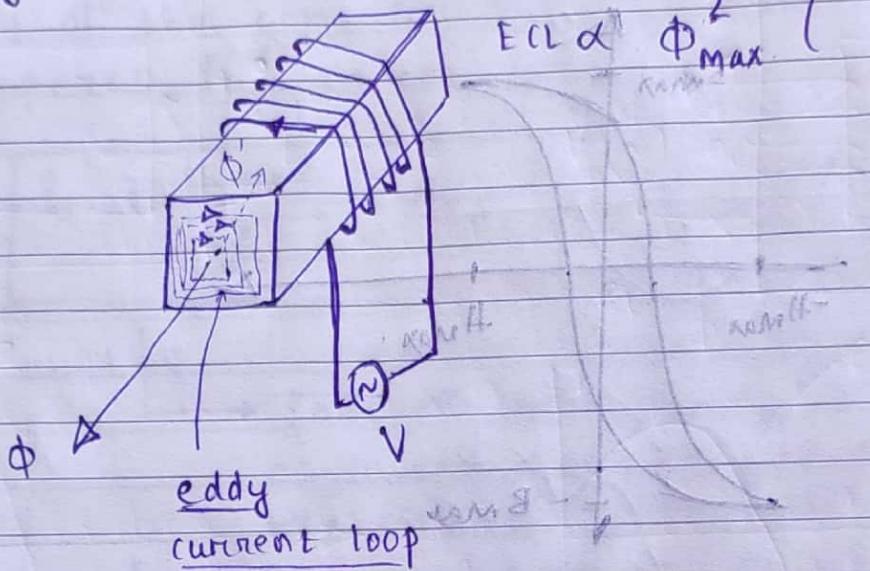2) Eddy current loss $ECL \propto f^2 \cdot \phi^2$ ($f = \text{frequency}$)


$ECL \propto \Phi_{\text{max}}^2$ (flux variation)



To reduce eddy current -

→ Resistivity is increased by using silicon-steel material

→ Laminated core

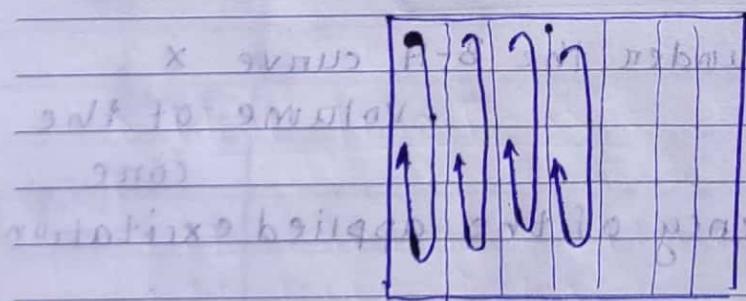

→ increases length of the eddy ct. path
→ reduces the eddy ct.

→ Lamination is done by varnish.

'18 MARCH

10


 Wk 10 • 069 Day
SATURDAY

 1- ϕ TRANSFORMERS

March 2018

Wk	M	T	W	T	F	S	S
09			1	2	3	4	
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	

Wk	M	T	W	T	F	S	S
04							
13	30						
14	2	3	4				
15	9	10	11				
16	16	17	18				
17	23	24	25				

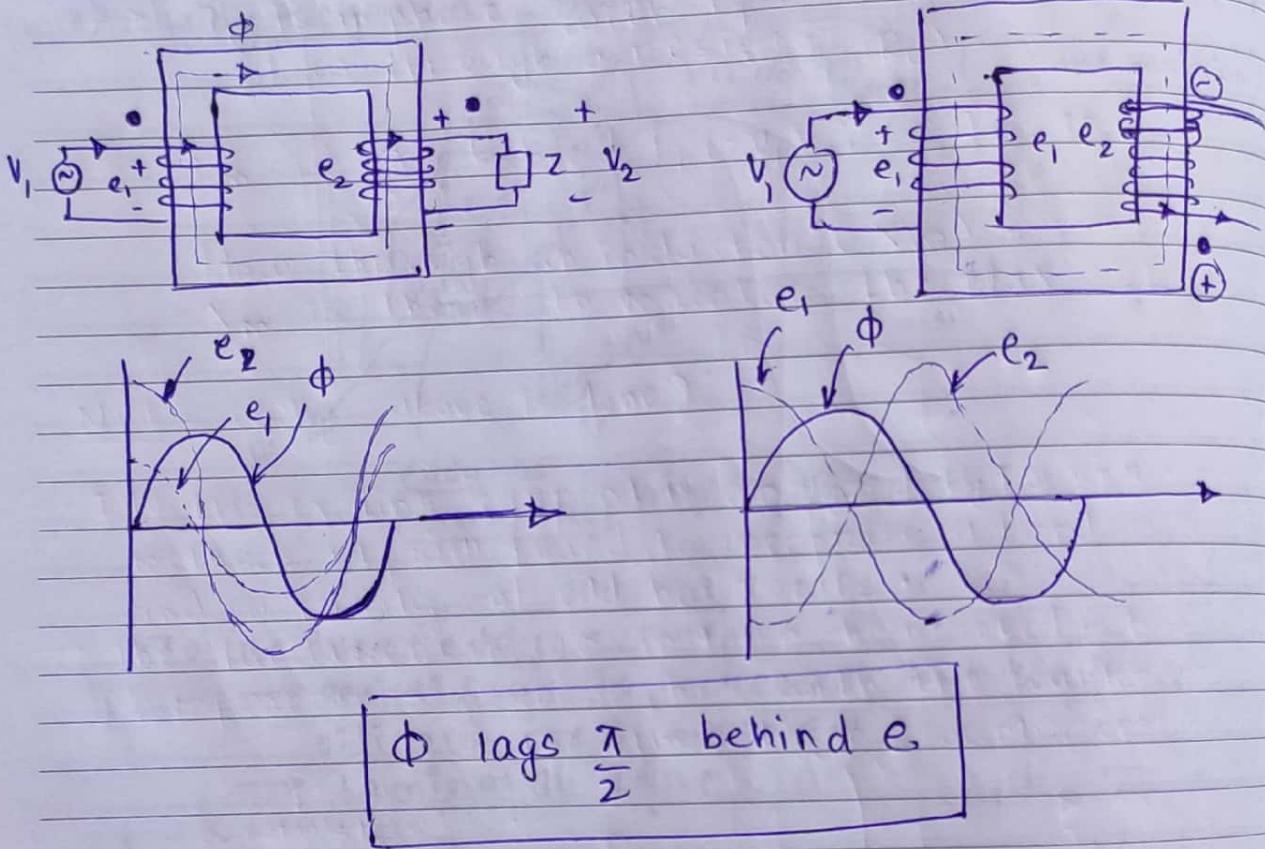
 * Ideal Transformer

11 Sunday

- No winding resistance
- No leakage flux
- No core loss
- Infinite relative permeability

For ideal transformer; $E_{1\text{ RMS}} = V_1 = 4.44 B_m A c N_1 f$
 $E_{2\text{ RMS}} = V_2 = 4.44 B_m A c N_2 f$

Wk	M	T	W	T	F	S	S
13	30	3	4	5	6	7	1
14	2	3	10	11	12	13	14
15	9	10	11	12	13	14	15
16	16	17	18	19	20	21	22
17	23	24	25	26	27	28	29

April 2018

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

ideal transformer

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

for all transformer


$$N_1 I_1 = N_2 I_2$$

ideal

$$\frac{V_1 I_1}{V_2 I_2} = 1$$

input kVA = output kVA


* No load case

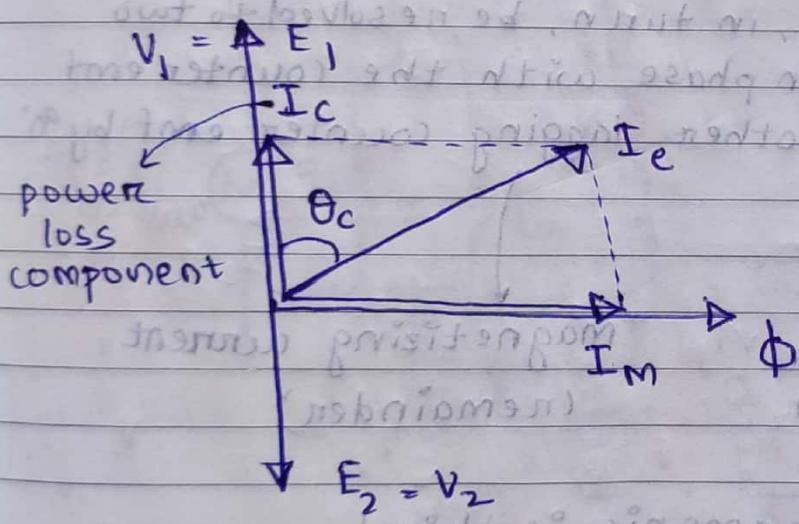 e_1, e_2 - out of phase (ψ)

$\phi = \phi_m \sin \omega t$

$e_1 = e_{1m} \cos \omega t$

$e_2 = -e_{2m} \cos \omega t$

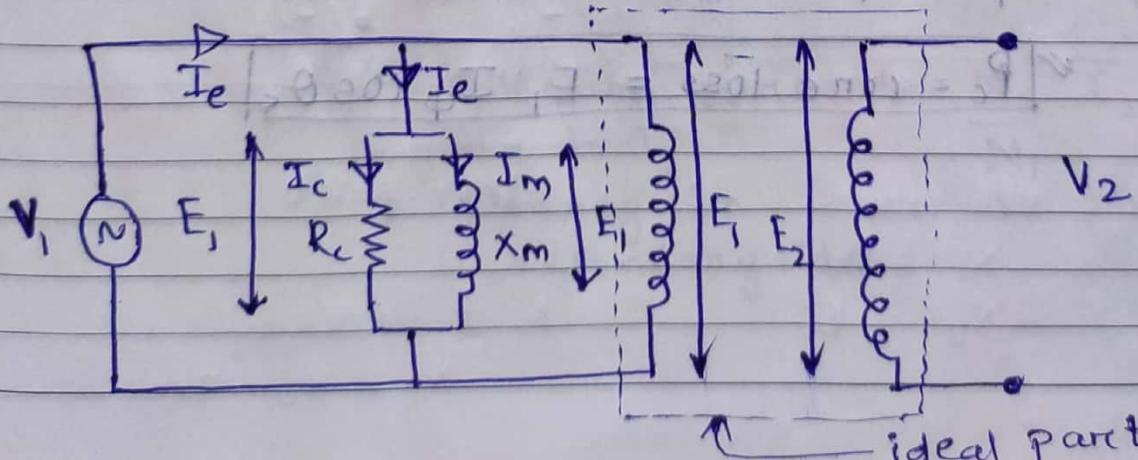 I_M → magnetising current. I_e → exciting current on no load ct.

18 MARCH

13

Wk 11 • 072 Day
TUESDAY

M	W	F	S
09		1	2
10	5	6	3
11	12	13	4
12	19	20	10
13	26	27	11
	28	29	12
	30	31	13

→ I_c is in phase with E_1 ; so the I_c must flow through a resistor (R_c).

→ I_m is $\frac{\pi}{2}$ behind $E_1 (= V_1)$; so I_m must flow through an inductor (X_m). X_m is there to maintain the flux.

NOTE: (Why above is done?)

~~AVR frequency = AVR magnitude~~

→ If the exciting current is analyzed by Fourier series methods, it will found to comprise a fundamental and a family of odd harmonics.

→ The fundamental can, in turn, be resolved to two components - (a) one in phase with the counter emf

(b) the other lagging counter emf by 90°

fundamental

core-loss

component

(hysteresis +

eddy current loss)


Magnetizing current

(remainder)

parts \leftarrow

total no - principle harmonic is third.
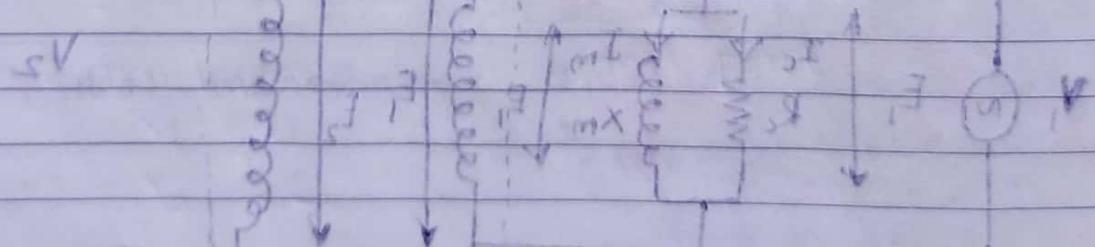
$$P_c = \text{core loss} = E_1 I_\phi \cos \theta_s$$






iron loss

Wk	M	T	W	T	F	S	S
13	30			6	7	8	1
14	2	3	4	5	6	7	8
15	9	10	11	12	13	14	15
16	16	17	18	19	20	21	22
17	23	24	25	26	27	28	29

Wk 11 • 073 Day
WEDNESDAY

14

* Transformer is loaded

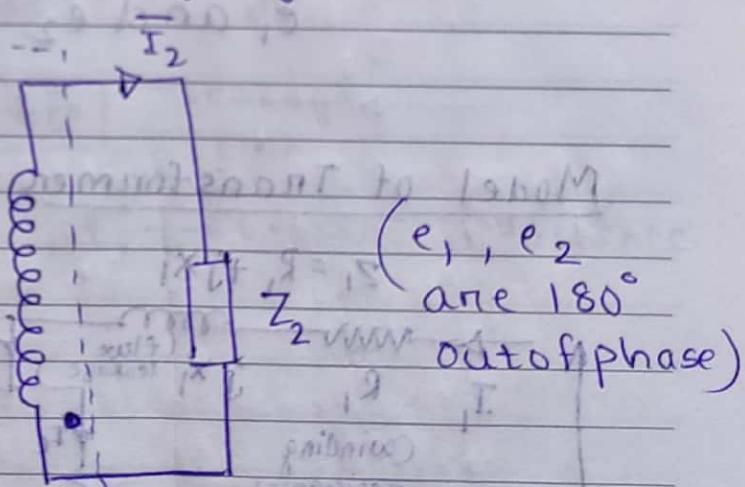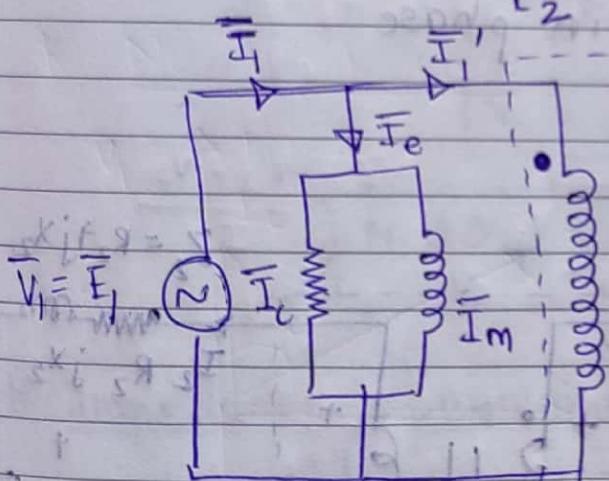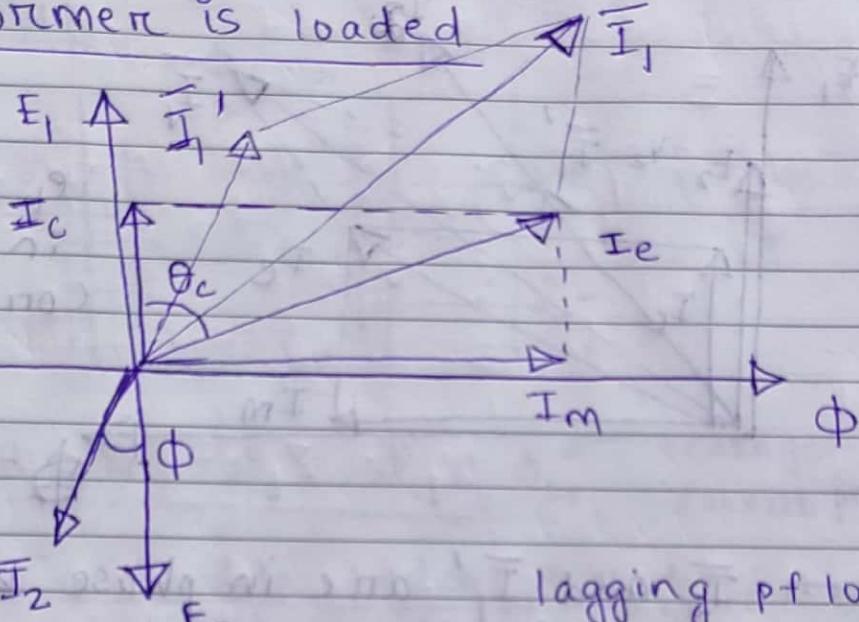

$$\bar{I}_1 = \bar{I}_1' + \bar{I}_e$$


\bar{I}_1' - reflection current = $\frac{N_2}{N_1} \bar{I}_2$
due to \bar{I}_2

flowing in secondary side

	M	T	W	T	F	S	S
09				1	2	3	4
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	


'18 MARCH

15

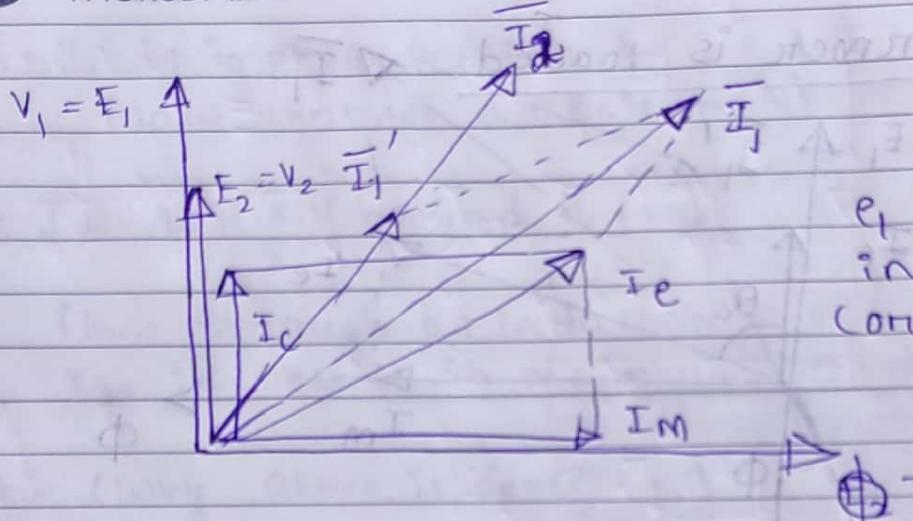 Wk 11 • 074 Day
THURSDAY


→ \bar{I}_2 and \bar{I}_1' are in phase because e_1 and e_2 are in phase

Model of Transformer

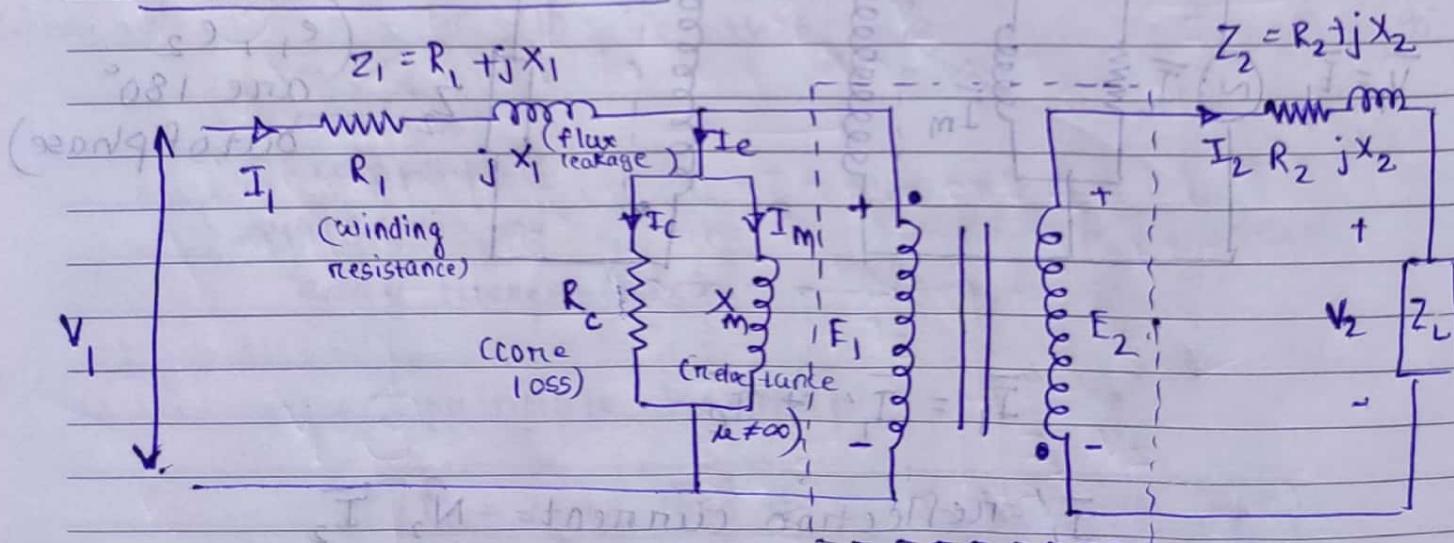

leakage reactances

$$X_1 = \omega L_1$$

$$X_2 = \omega L_2$$

$R_1, R_2 \rightarrow$ winding resistance

ideal part

As f increases,


X_1, X_2 increases.

WEEK	M	T	W	T	F	S	S
13	30		4	5	6	7	8
14	2	3	10	11	12	13	14
15	9	10	17	18	19	20	21
16	16	17	24	25	26	27	28
17	23	24	25	26	27	28	29

Wk 11 • 075 Day

FRIDAY

* Leakage flux

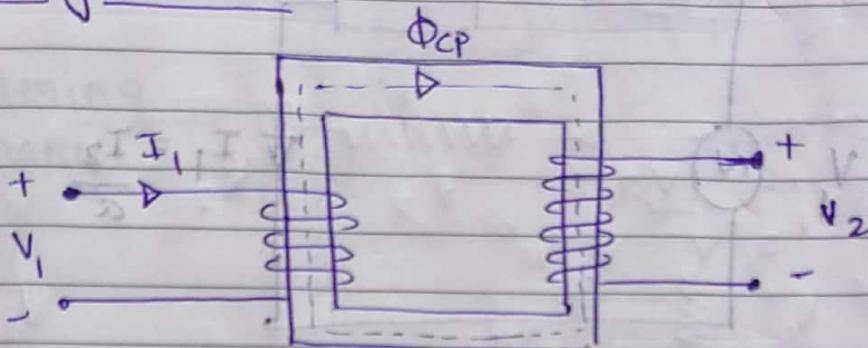

$$\left(\frac{N_1}{N_2} = \frac{\Phi_{CP}}{\Phi_{LP}} \right)$$

Total flux $\Phi_p = \Phi_{CP} + \Phi_{LP}$ ← Leakage flux at primary


$$N_1 \frac{d\Phi_p}{dt} = N_1 \frac{d\Phi_{CP}}{dt} + N_1 \frac{d\Phi_{LP}}{dt}$$

$$V_1 = E_1 + E_{LP}$$
 ← Leakage EMF

$$N_1 \frac{d\Phi_{LP}}{dt} = L_I I_1$$
, L_I → Leakage inductance

* Impedance transformation

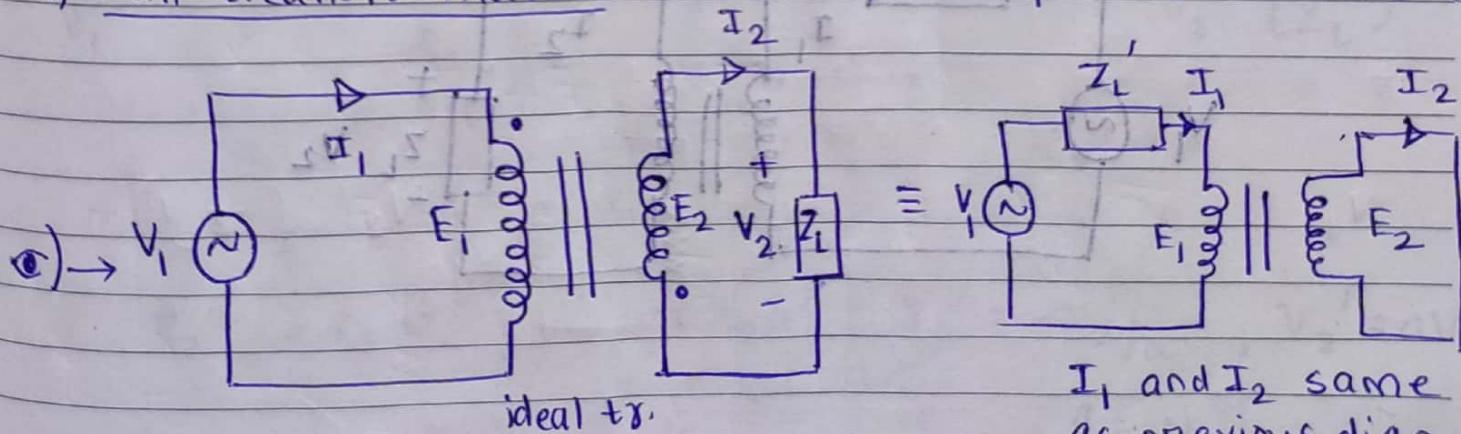a) Full transformation (whole load impedance transferred)




'18 MARCH

17

Wk 11 • 076 Day
SATURDAY

Ma	SSP Notes						
Wk	M	T	W	T	F	S	S
09				1	2	3	4
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	


$$\left(\frac{N_1}{N_2} = a \right)$$

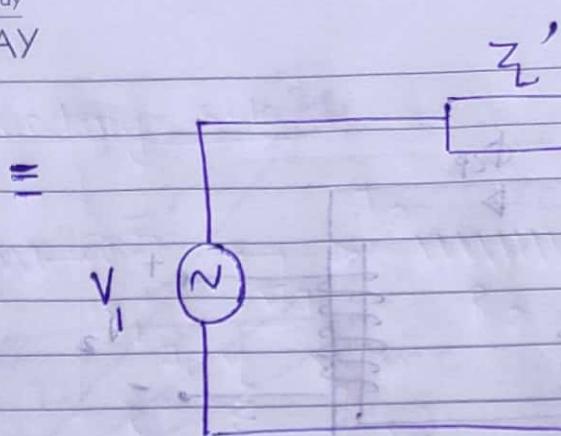

$$I_1 = I_2 \frac{1}{a}$$

$$Z'_L = Z_L a^2$$


b) Partial transformation

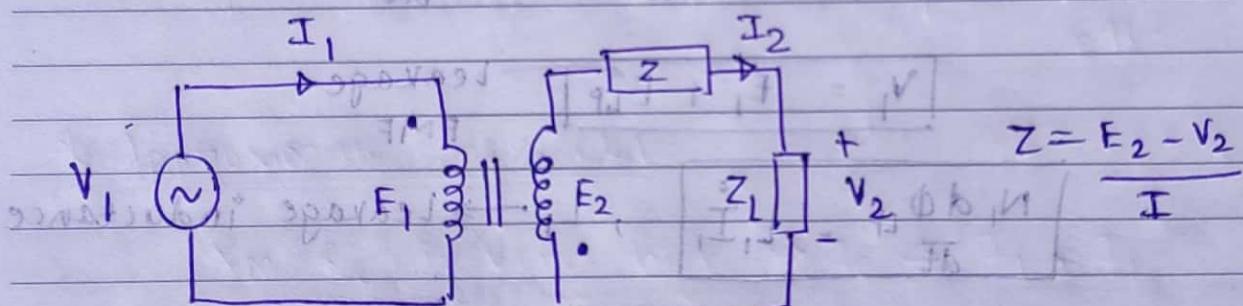

$$Z = E_2 - V_2 / I$$

We want to transfer Z' only not Z_L . \Rightarrow Z' only


We want,

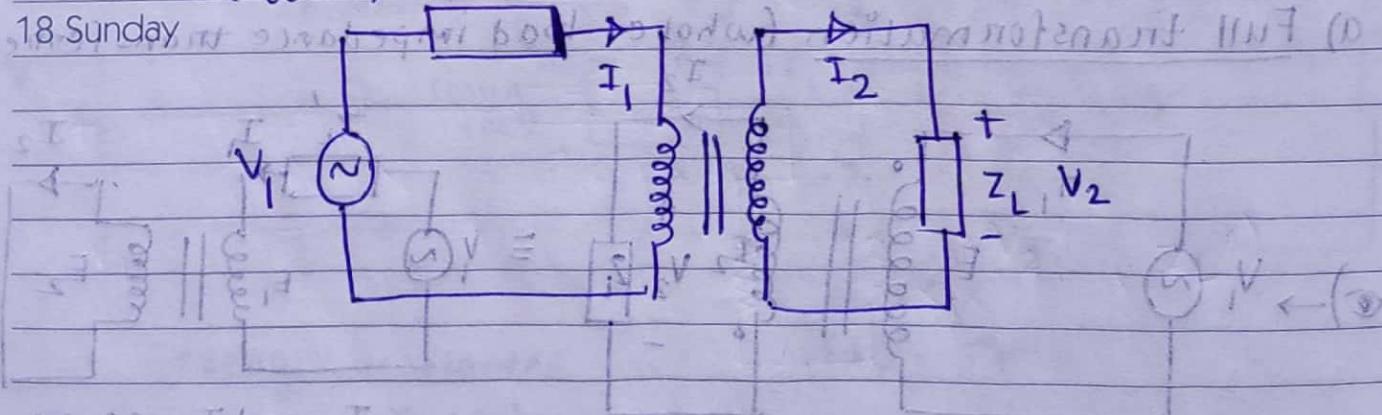

source E_2 & I
gives V_2 giving Z

W	K	M	T	W	T	F	S	S
13	30		4	5	6	7	8	1
14	2	3						8
15	9	10	11	12	13	14	15	
16	16	17	18	19	20	21	22	
17	23	24	25	26	27	28	29	

Wk 12 • 078 Day
MONDAY

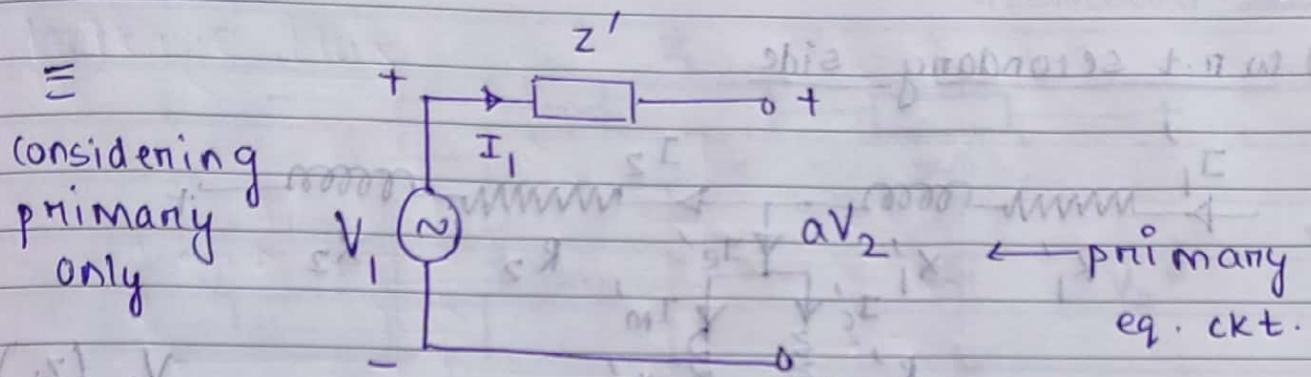


$$\Rightarrow Z' = \frac{V_1 - aV_2}{I_1} = \frac{E_1 - aV_2}{(I_2/a)} = \frac{aE_2 - aV_2}{(I_2/a)}$$

$$\therefore \boxed{Z' = a^2 Z}$$

* Transformer equivalent ckt

(a) w.r.t primary side

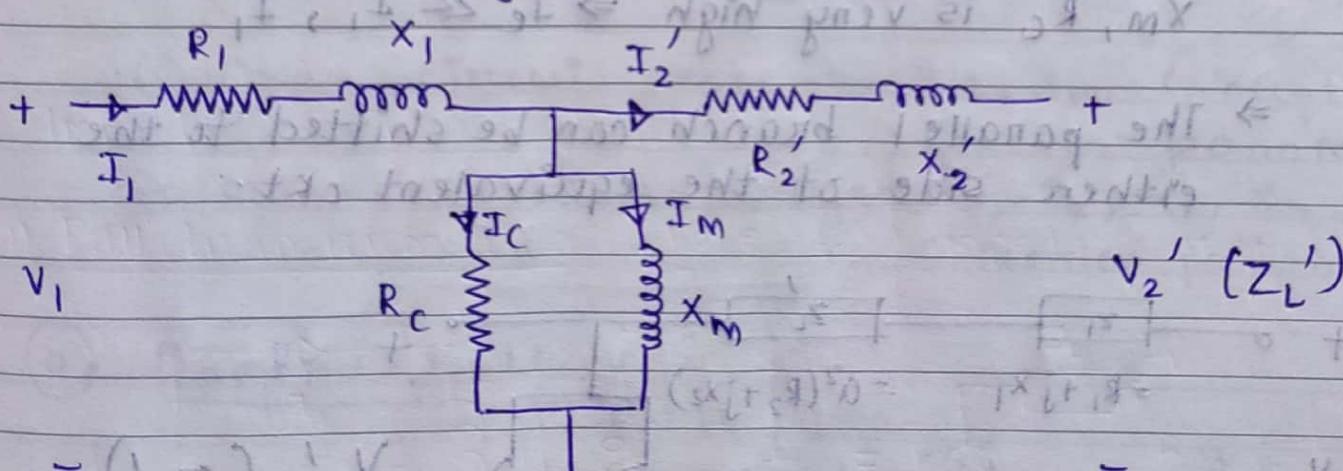

$$R_2' = R_2 a^2 ; X_2' = X_2 a^2 ; I_2' = I_2/a , V_2' = aV_2$$

$$a = \frac{N_1}{N_2} = \frac{\text{turns}}{\text{ratio}}$$


'18 MARCH

20

 Wk 12 • 079 Day
TUESDAY

W	K	M	T	W	T	F	S	S
09					1	2	3	4
10	5	6	7	8	9	10	11	
11	12	13	14	15	16	17	18	
12	19	20	21	22	23	24	25	
13	26	27	28	29	30	31		

(b) w.r.t secondary side

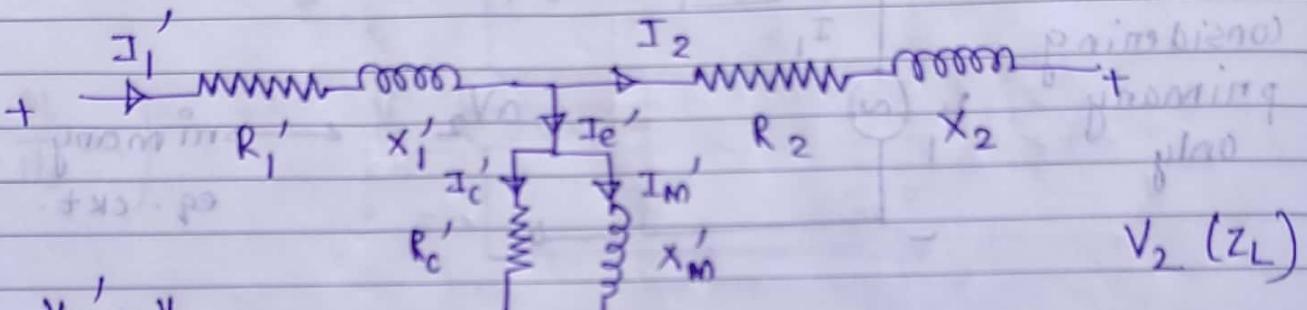

$$V_1' = \frac{V_1}{a}$$


$$X_1' = X_1/a^2; R_1' = R_1/a^2; I_1' = I_1 \cdot a$$

etc.

* Approximate eqv. ckt.

X_M, R_C is very high $\Rightarrow I_e \ll I_1, I_1'$

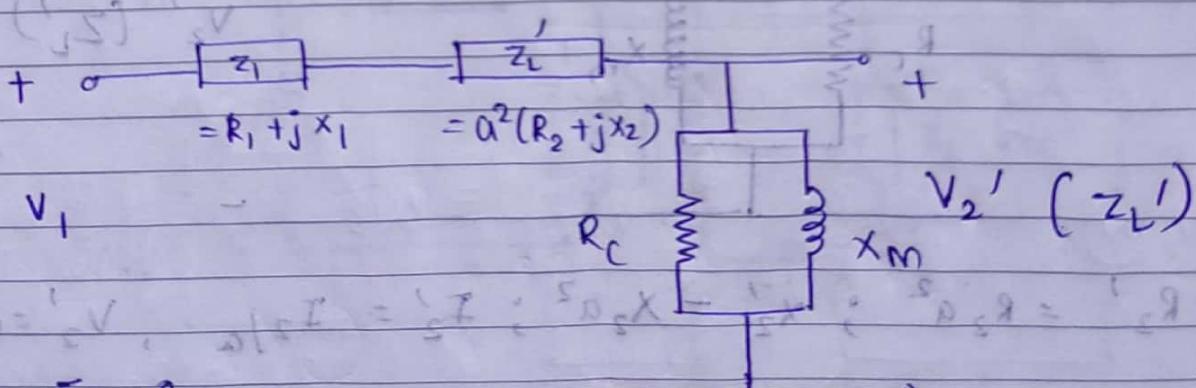\Rightarrow The parallel branch can be shifted to the either side of the equivalent ckt.



04 April 2018


Wk/M	T	W	T	F	S	S
13	30		4	5	6	7
14	2	3	4	5	6	8
15	9	10	11	12	13	14
16	16	17	18	19	20	21
17	23	24	25	26	27	29

Wk 12 • 080 Day


WEDNESDAY

21

(OR)

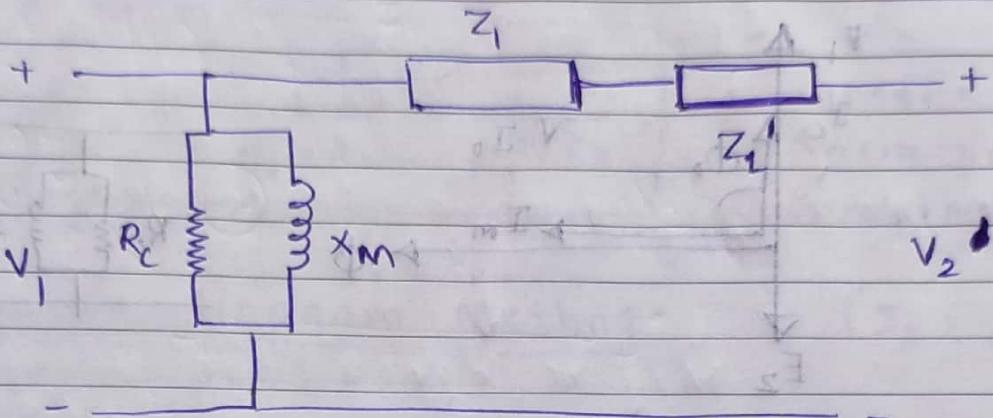

(OR)

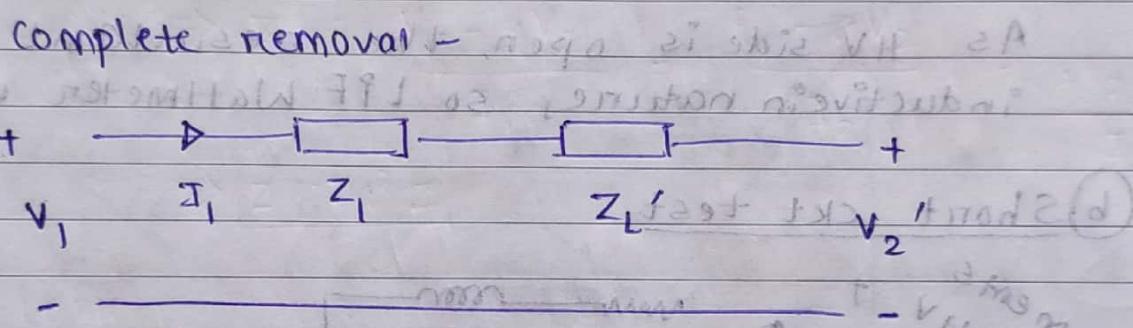

* Parameters of equiv. tn. ckt.

- (1) Open circuit test $\rightarrow R_c, X_m$ (shunt parameters)
- (2) Short circuit test $\rightarrow R_1, R_2, X_1, X_2$ (series parameters)

(a) Open ckt test

Instruments on LV side and HV side kept open.

cone loss \leftarrow
iron loss $W_o = V_o I_o \cos \phi_o \Rightarrow \cos \phi_o = \frac{W_o}{V_o F_o}$
at full

Voltage $I_c = I_o \cos \phi_o \Rightarrow R_c = \frac{V}{I_c}$

$I_m = I_o \sin \phi_o \Rightarrow X_m = \frac{V}{I_m}$


Wk	M	T	W	T	F	S	S
09					1	2	3
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	

'18 MARCH

22


Wk 12 • 081 Day

THURSDAY

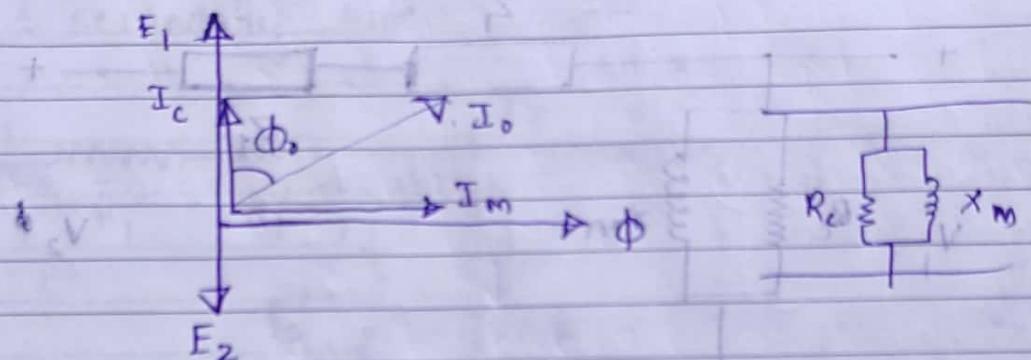

As HV side is open, the resultant is inductive in nature, so LPF Wattmeter used.


(b) Short ckt test

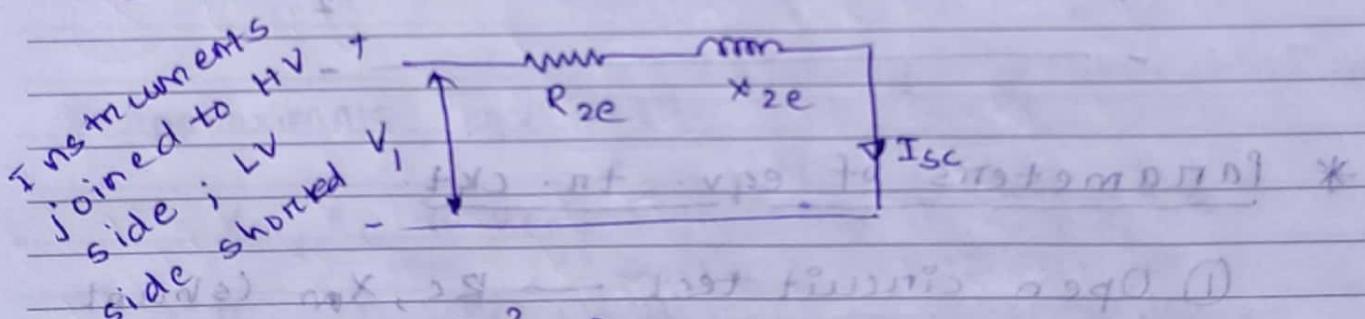

$$W_{sc} = I_{sc}^2 \cdot R_{2e}$$

$$\Rightarrow R_{2e} = \frac{W_{sc}}{I_{sc}^2}$$

$$Z_{2e} = \sqrt{R_{2e}^2 + X_{2e}^2}$$

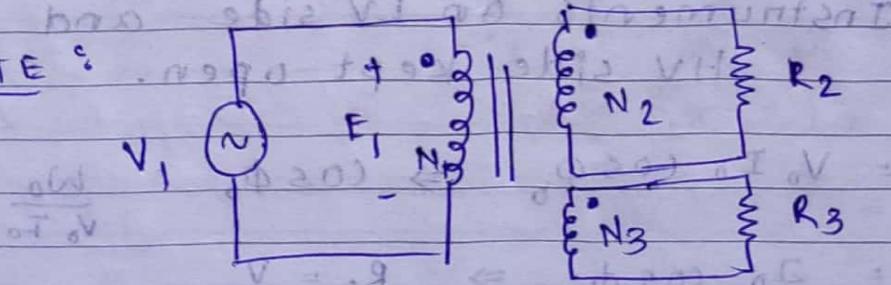NOTE :


W	K	M	T	W	T	F	S	S
13	30		3	4	5	6	7	8
14	2	3	10	11	12	13	14	15
15	9	10	17	18	19	20	21	22
16	16	17	24	25	26	27	28	29
17	23							

Wk 12 • 082 Day
FRIDAY

23


$$\frac{1}{Z_1} = \frac{1}{R_1 + jX_1} + \frac{1}{R_2 + jX_2}$$

(Transfer and their parallel combination)

(*) Phasor diagram method

 I_2 = full load ct.)

a) Lagging

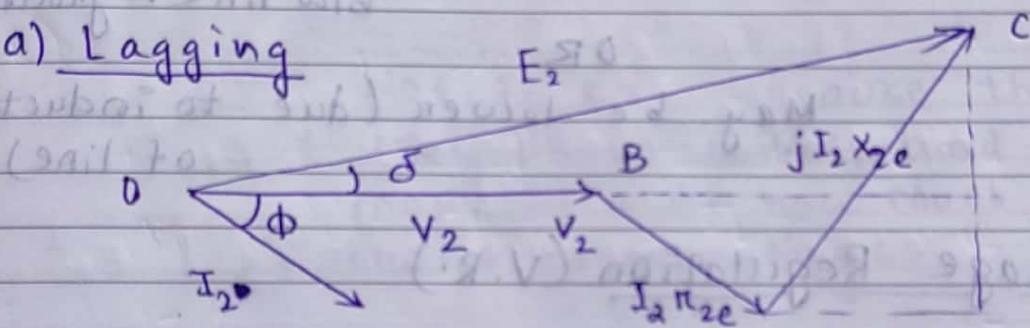

Derive $|E_2|^2 = (V_2 + I_2 \pi_{2e} \cos \phi \mathbf{V}_2 + I_2 X_{2e} \sin \phi)^2$
and use

$+ (I_2 X_{2e} \cos \phi - I_2 \pi_{2e} \sin \phi)$


For worst case regulation or approximation

use $E_2 \approx V_2 + I_2 \pi_{2e} \cos \phi + I_2 X_{2e} \sin \phi$

$$E_2 - V_2 \approx I_2 \pi_{2e} \cos \phi + I_2 X_{2e} \sin \phi$$

$\{\phi \approx 0^\circ + \phi_{20}\}$ OB \propto OC i.e. δ is very small

b) Leading

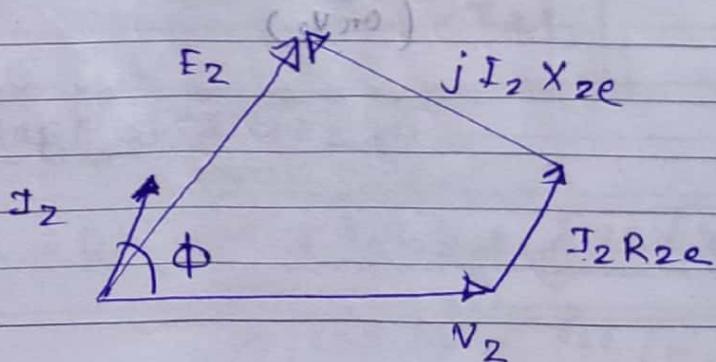

Wk	M	T	W	T	F	S	S
09					1	2	3
10	5	6	7	8	9	10	11
11	12	13	14	15	16	17	18
12	19	20	21	22	23	24	25
13	26	27	28	29	30	31	

18 MARCH

24

Wk 12 • 083 Day
SATURDAY

IMP. $\begin{cases} \rightarrow V_2 < E_2 \text{ for lagging pf load} \\ \rightarrow V_2 > E_2 \text{ for leading pf load} \end{cases}$

\rightarrow The receiving voltage from generating station

May be higher (due to capacitance between line & ground)

OR

May be lower (due to inductance of line)

(*) Voltage Regulation (V.R.)

$$\% \text{ V.R.} = \frac{E_2 - V_2}{E_2} \times 100 \quad \text{on } E_2 - V_2$$

Reading P & Q (Use Any formula ; but mention clearly)

\rightarrow V.R. should be as less as possible for a good transformer (i.e., near zero)

$$\text{V.R.} = \frac{I_2}{E_2} \left\{ R_{2e} \cos \phi + X_{2e} \sin \phi \right\}$$

(on V_2)

Wk/M	T	W	T	F	S	S
13	30		4	5	6	7
14	2	3	4	5	6	8
15	9	10	11	12	13	14
16	16	17	18	19	20	21
17	23	24	25	26	27	28
						29

Wk 13 • 085 Day

MONDAY

26

- * Transformer Rating
- maximum voltage we can give $kVA, \frac{V_1}{V_2}$ (voltage ratio), frequency
 - Φ_f = constant for a fixed voltage supply
 - ⇒ As $f \uparrow, \Phi \downarrow$ & vice-versa
 - OR $f \downarrow, \Phi \uparrow$ & saturation may reach (India-USA)
 - Not in kW, because the load may draw KVAR, and we couldn't make idea of how much KVAR is transformer rating.

$$\rightarrow \text{Primary - side rated ct} = \frac{kVA}{V_1}$$

$$\rightarrow \text{Secondary - side rated ct} = \frac{kVA}{V_2}$$

1) Zero voltages regulation

$$IN, R.D=0 \Rightarrow \left| \tan \phi = \frac{x_{2e}}{z_{2e}} \right|$$

$$\text{Additional f} \Rightarrow \left| \cos \phi = \frac{x_{2e}}{z_{2e}} \right|$$

2) Maxm. voltage regulation

$$\begin{aligned} d V.R = 0 &\Rightarrow \left| \tan \phi = x_{2e} / z_{2e} \right| \\ \frac{d \phi}{d \Phi} &\Rightarrow \left| \cos \phi = z_{2e} / x_{2e} \right| \end{aligned}$$

18 MARCH


SSP Notes

M					S
09			1	2	3
10	5	6	7	8	9
11	12	13	14	15	16
12	19	20	21	22	23
13	26	27	28	29	30

27

 Wk 13 • 086 Day
TUESDAY

* Losses in transformer

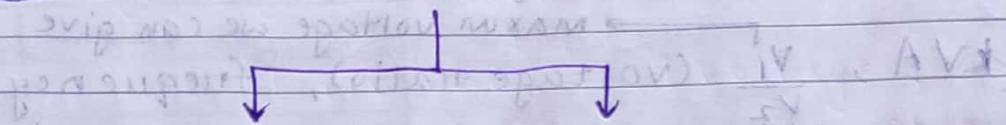

$(I_c E_1)$ Core loss Ohmic (Copper) loss.

Hysteresis loss Eddy ct. loss

(A_{2U}) (P_h) (P_e)

$$\rightarrow P_h = \text{hysteresis loss} = K_h \cdot f \cdot B_m^x$$

$$\rightarrow P_e = \text{eddy current loss} = K_e f^2 B_m^2$$

$$\rightarrow B_m \propto f \propto N$$

$$\begin{aligned} \frac{P_h}{V} &\Rightarrow P_h \propto V^x \cdot f^{1-x} \\ \frac{P_e}{V} &\Rightarrow P_e \propto V^2 \end{aligned}$$

$x \rightarrow$ Steinmetz's constant

$K_h \rightarrow$ hysteresis constant, depends on the magnetic material

$K_e \rightarrow$ eddy ct. constant, depends on thickness of lamination.

$$\rightarrow P_{\text{iron}} / P_{\text{core}} = P_h + P_e = K_h f B_m^x + K_e f^2 B_m^2$$

assuming $K_h \propto f^x$ and $K_e \propto f^2$ (as $B_m = \text{constant}$)

$$100 \times 100 = 100 + 1 \Leftrightarrow 0 = 9. V B$$

$$100 \times 100 = 100 + 1 \Leftrightarrow 0 = 9. V B$$

Wk	Wk	M	I	T	W	F	S	S
13	13	30	3	4	5	6	7	8
14	14	2	10	11	12	13	14	15
15	15	9	17	18	19	20	21	22
16	16	16	24	25	26	27	28	29
17	17	23						

Wk 13 • 087 Day
WEDNESDAY

* Efficiency

$$\eta = \frac{\text{Output power}}{\text{Input power}} = \frac{\text{Output power}}{\text{Output power} + \text{losses}}$$

$$= \frac{x \times (\text{kVA}) \times \cos \phi}{x \times (\text{kVA}) \times \cos \phi + P_c + x^2 P_{cu, fl}}$$

Max^m η, - at constant cos φ

$$\rightarrow + n = \sqrt{\frac{P_c}{P_{cu, fl}}} \Rightarrow P_c = n^2 P_{cu, fl}$$

$$\Rightarrow P_c = P_{cu}$$

⇒ Fixed value = variable value

$$\rightarrow \eta_{\max} = \frac{x(\text{kVA}) \cos \phi}{x(\text{kVA}) (\cos \phi + 2P_c)}$$

(True for power transformer, not for distribution transformer)

• Energy efficiency (or all-day efficiency)

→ Useful for distribution tn. when load is varying over the day.

$$\rightarrow \eta = \frac{\text{Output KWH}}{\text{Output KWH} + \text{loss in KWH}}$$

→ Core loss
(primary side - so fixed)

→ Copper loss
(vary throughout day)

29

Wk 13 • 088 Day


THURSDAY

Ma	1	2	3	4
W	5	6	7	8
10	12	13	14	15
11	19	20	21	22
12	26	27	28	29
13	28	29	30	31

* Voltage regulation under the rated load voltage

(We would fix the load voltage, and we) would derive it by increasing primary side voltage

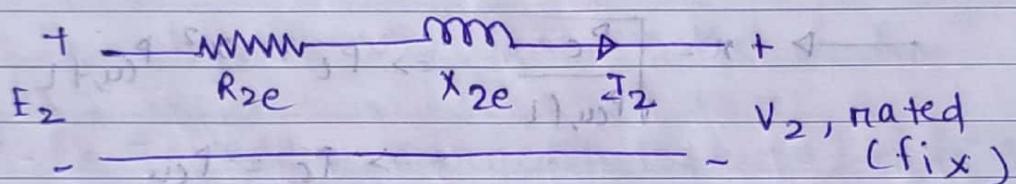
$$V.R. = \frac{V_2 \text{ at no load} - V_2 \text{, rated}}{V_2 \text{, rated}}$$



$$E_2 = V_2, \text{ rated} + I_2 (R_{2e} + j X_{2e})$$

$$\rightarrow E_2 = V_2, \text{ rated } 0^\circ + I_2 (R_{2e} + j X_{2e})$$

* Efficiency curve (no annotations)

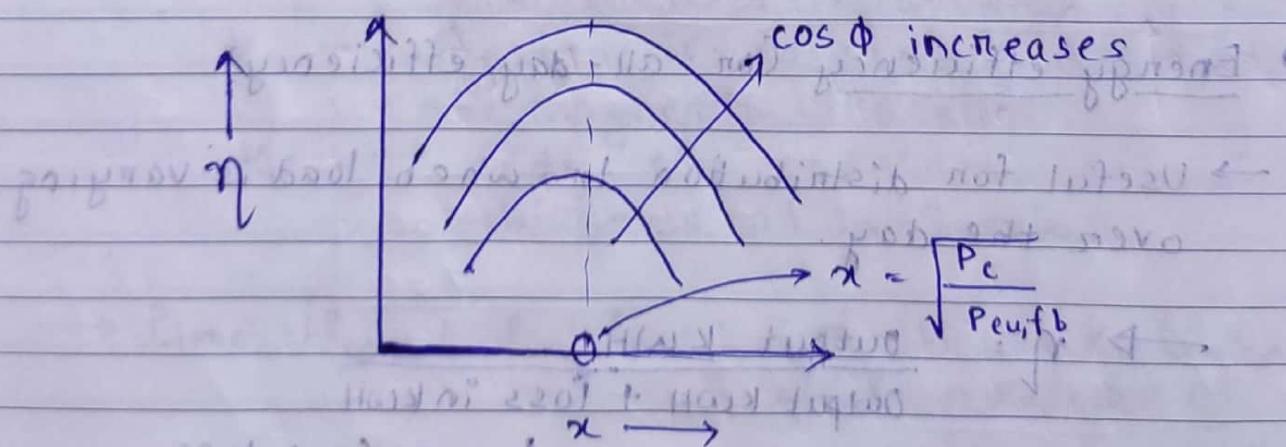

→ At fixed α , η_{\max} occurs at unity power factor (UPF). (no annotations)

Wk 13 • 089 Day
FRIDAY

30

SUN	MON	TUE	WED	THU	FRI	SAT
30	1	2	3	4	5	6
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

* Per-unit resistance drop of a transformer
 $= (\text{full-load primary current}) \times (\text{eq. resistance referred to primary circuit})$

Multiply by 100 to convert it to percentage


Primary voltage

$= (\text{full-load secondary ct.}) \times (\text{eqv. resistance referred to secondary ckt.})$

secondary voltage.

* Cases of Voltage Regulation

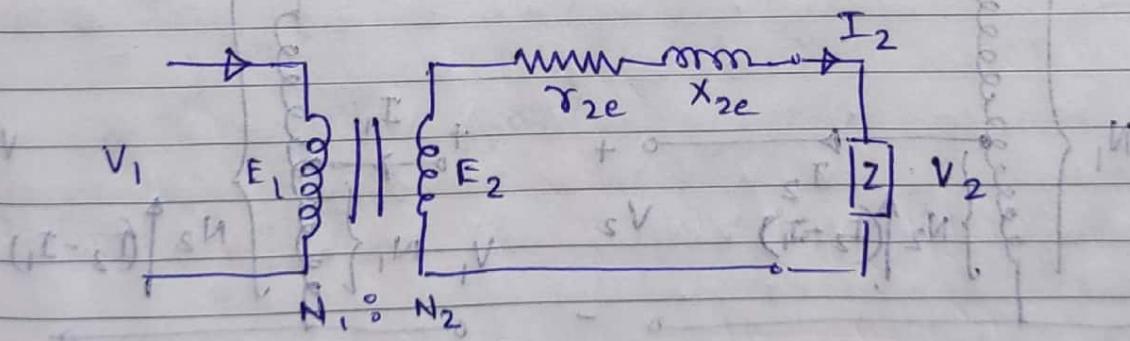- V.R. when Tr. primary side is supplied rated voltage



$$\% \text{V.R.} = \frac{E_2 - V_2}{E_2} \rightarrow ①$$

(nominal) voltage of intended load ←
 (nominal) voltage of load (existing)




SSP Notes									
09	10	11	12	13	14	15	16	17	18
10	5	6	7	8	9	10	11		
11	12	13	14	15	16	17	18		
12	19	20	21	22	23	24	25		
13	26	27	28	29	30	31			

31


Wk 13 • 090 Day
SATURDAY

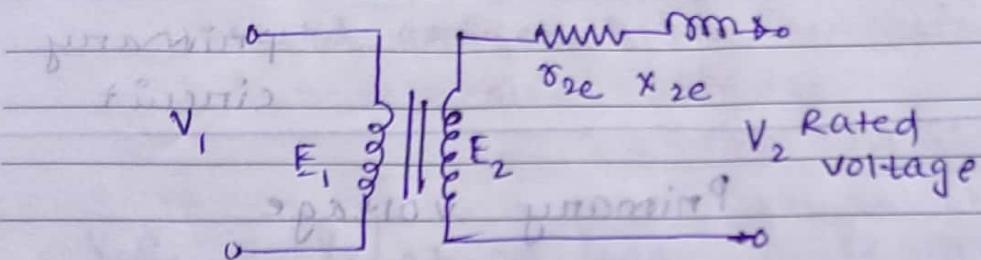- V.R. when rated voltage is reqd. at the t.r. secondary stage -



$$N_1 \circ N_2 = \frac{E_2 - V_2}{V_2} \text{ variable}$$

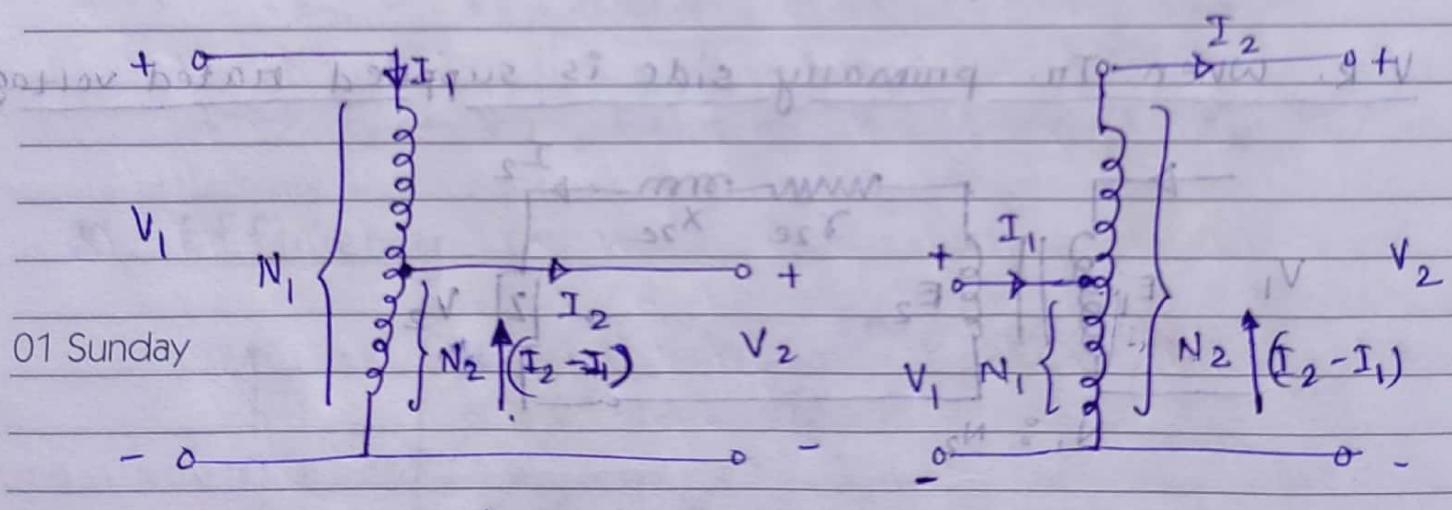* 1 - φ Transformer (single-winding transformer)
→ mit nur einer Spule von 2000



→ Energy transfer by conduction (common portion) and by magnetic coupling.

03

 Wk 14 • 093 Day
TUESDAY

NPTEL
THREE PHASE INDUCTION
MOTORS

$$(I - \frac{1}{2} I_s) V = AV$$

- Two main parts: $I_1 V - I_2 V = AV$ (motor)
 1) a stationary stator
 2) a revolving motor.

The rotor is separated from the stator by a small air-gap which ranges from 0.4 mm to 4 mm depending upon the power of the motor.

→ Principle: The operation of a three-phase induction motor is based upon the application of Faraday's Law and the Lorentz force on a conductor.

- 1) A voltage $BLV = E$ is induced in each conductor while it is being cut by the flux (Faraday's law)
- 2) The induced voltage immediately produces a current I , which flows down the conductor, through the end bars, and back through the other conductors.
- 3) Because the current-carrying conductor lies in the magnetic field of the permanent magnet it experiences a mechanical force (Lorentz force)

May 2018						
W	K	M	T	W	T	F
18	1	2	3	4	5	6
19	7	8	9	10	11	12
20	14	15	16	17	18	19
21	21	22	23	24	25	26
22	28	29	30	31		

APR

Wk 14 • 094 Day
WEDNESDAY

04

4) The force always acts in a direction to drag the conductor along with the magnetic field.

→ In an induction motor, the ladder is closed upon itself to form a squirrel - cage, and the moving magnet is replaced by a rotating field.

$$N_s = \text{synchronous speed} = \frac{120 f}{P}$$

N_s = synchronous speed = $\frac{120 f}{P}$
 n = motor speed

Infinite bus = V , f are constant

→ The machine acts merely as a transformer where the stator (primary) and the rotor (secondary) have EMFs of the same frequency induced in them by the rotating magnetic flux rather than time-varying flux.

→

Rotor is short-circuited and stationary

W	K	M	T	W	T	F	S	S
13	30							1
14	2	3	4	5	6	7	8	
15	9	10	11	12	13	14	15	
16	16	17	18	19	20	21	22	
17	23	24	25	26	27	28	29	

'18 APRIL

05

Wk 14 • 095 Day

THURSDAY

$\rightarrow S = \frac{n_s - n}{n_s}$

\rightarrow Motor frequency ~~speed~~ -

$f_2 = sf$ (Motor frequency)

$$n = (1-s) n_s \quad \text{--- (3)}$$

$$120sf = n_s - n \quad \text{--- (4)}$$

- The slip 's' is the per unit speed (w.r.t. synchronous speed) at which the motor slips behind the stator field.

←

A ²⁴ motor
is running
at 1200 rpm
per min.

Wk	M	T	W	T	F	S
13	30					8
14	2	3	4	5	6	7
15	9	10	11	12	13	14
16	16	17	18	19	20	21
17	23	24	25	26	27	28

'18 APRIL


07

 Wk 14 • 097 Day
SATURDAY

THREE-PHASE INDUCTION MOTOR

* Main parts -

- ① Stator
- ② Rotor

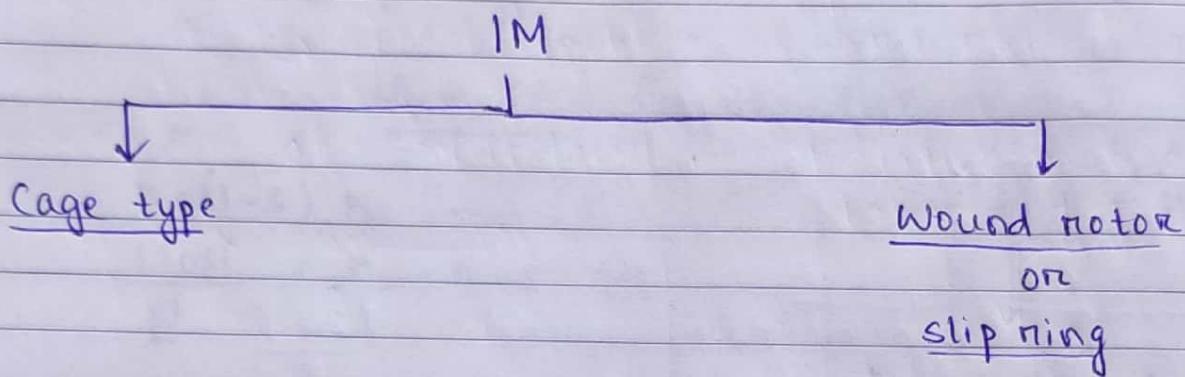


- Less maintenance cost
- More robust
- Starting torque is less


- High starting torque
(Ext. resistance can be added)
- Better speed control
- Frequent maintenance

Working Principle: Rotating Magnetic Field

08 Sunday

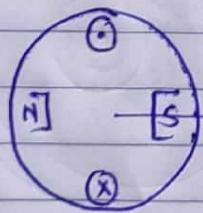

mmf

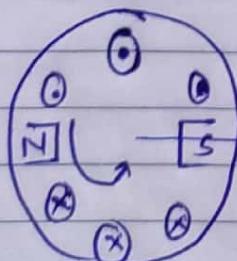 (pulsating magnetic field;
 $1 - \phi$)


mmf

(pulsating + rotating magnetic field)

 ↓
 SYNCHRONOUS speed
 (N_s)

May 2018

Wk	M	T	W	T	F	S	S
18	1	2	3	4	5	6	
19	7	8	9	10	11	12	13
20	14	15	16	17	18	19	20
21	21	22	23	24	25	26	27
22	28	29	30	31			

 Wk 15 • 099 Day
MONDAY

09

$$N_s = \frac{120f}{P \text{ (no. of poles)}}$$

$$\rightarrow \Omega_m = \frac{2}{P} \theta_e$$

→ electrical angle


is angle between poles
(motor vs stator)

Mechanical angle is

angle of motor shaft.

vs stator

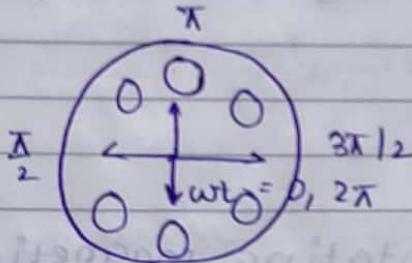→ The MMF rotates (poles) but with a constant magnitude of $1.5 F_m$.



→ speed of rotating magnetic field = ω_m
 $(\because \theta_m = \theta_e)$ = ω_e
 $= 2\pi f$

$$\text{For a } P\text{-pole m/c } \omega_m = \frac{2}{P} \omega_e$$

$$\omega_m = \frac{4\pi f}{P} \text{ rad/s}$$

$$\Rightarrow \frac{2\pi}{60} N_s = \frac{4\pi f}{P}$$

rev/min.

$$N_s = \frac{120f}{P}$$

14	2	3	4	5	6	7
15	9	10	11	12	13	14
16	16	17	18	19	20	21
17	23	24	25	26	27	28

'18 APRIL

10

Wk 15 • 100 Day

TUESDAY


- The flux of stator magnetic field cuts rotor; produces three phase voltage in rotor due to 3-φ windings on it, current flows, torque experienced
 ↗ produces → Rotating magnetic field produced by motor at N_{sr} speed (synchronous w.r.t motor)
- Cause of emf induced → relative motion b/w stator and rotor

→ Motor rotates to signs

motor thus moves

$$\text{slip (s)} = 0$$

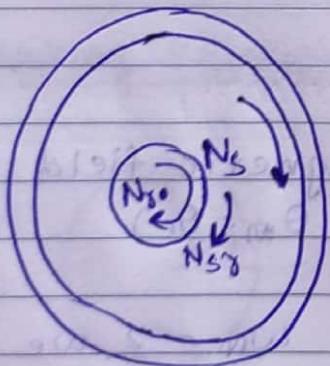$N_r = N_s$ (Not possible) ← as to catch up
 ↓ as there is no N_s but not possible
 no magnetic locking)



N_c = stator rotating magnetic field $N_s = \frac{120f}{P}$ wrt stator

N_{sr} = motor rotating magnetic field $N_{sr} = \frac{120sf}{P} = sN_s = \frac{120f}{P}$

Speed of motor rotating magnetic field wrt stator

$$N_{sr} = N_{sr} + N_r = sN_s + (1-s)N_s = N_s$$

(synchronous wrt stator)

May 2018

Wk/M	T	W	T	F	S	S
18	1	2	3	4	5	6
19	7	8	9	10	11	12
20	14	15	16	17	18	19
21	21	22	23	24	25	26
22	28	29	30	31		

AP

Wk 15 • 101 Day

WEDNESDAY

speed of motor rotating magnetic field wrt stator rotating magnetic field = 0


$$S = \text{slip} = \frac{N_s - N_r}{N_s}$$

$$N_r = (1-s) N_s \quad \text{and} \quad N_{sr} = s N_s$$

→ $f_r = \text{frequency of induced emf in motor} = sf$

$$f_r = sf$$

* Ckt. diagrams

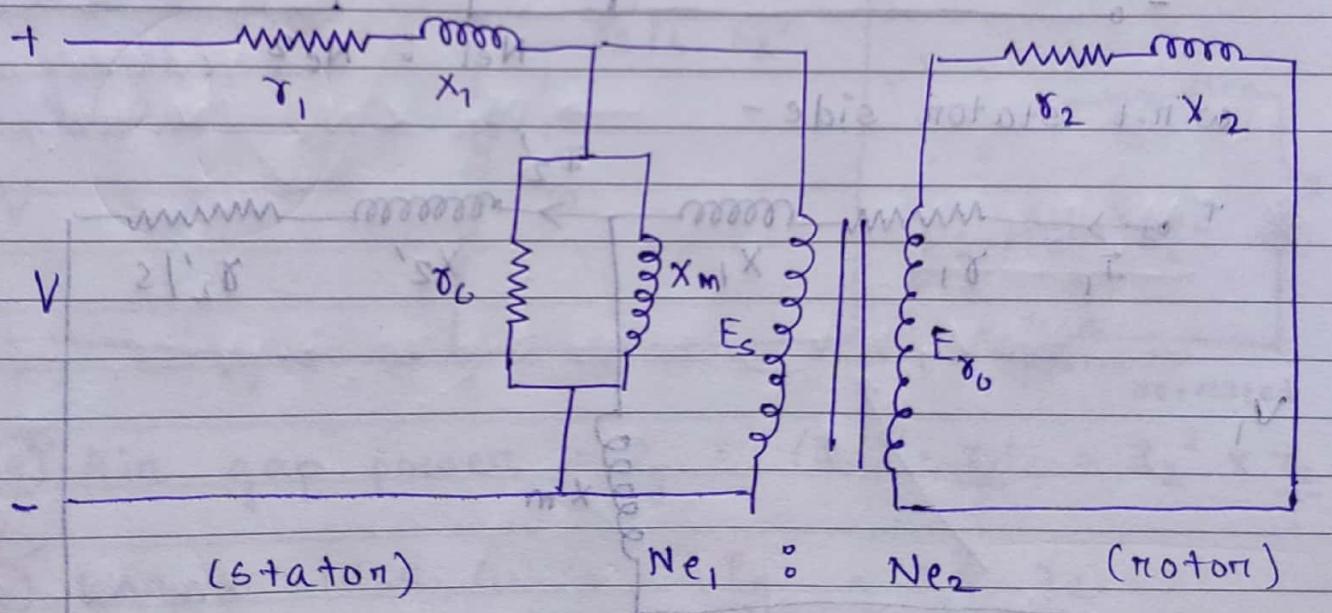

$$\rightarrow E_s = 4.44 \phi f N_s \cdot (K_{ws}) \quad , \quad (K_{ws}) \rightarrow \text{distribution factor for stator}$$

$$\rightarrow E_r = 4.44 \phi f_r N_r \cdot (K_{wr})$$

winding
 $\phi \rightarrow \text{flux in the air gap}$




Ap	
W	
13	
14	2 3 4 5 6 7 8
15	9 10 11 12 13 14 15
16	16 17 18 19 20 21 22
17	23 24 25 26 27 28 29

$$\frac{E_S}{E_{T_0}} = \frac{N_{e1}}{N_{e2}}$$


(N_{e1} & N_{e2} are effective no. of turn)

At standstill, the equivalent ckt is as shown ($S = 1$, just going to start) above.

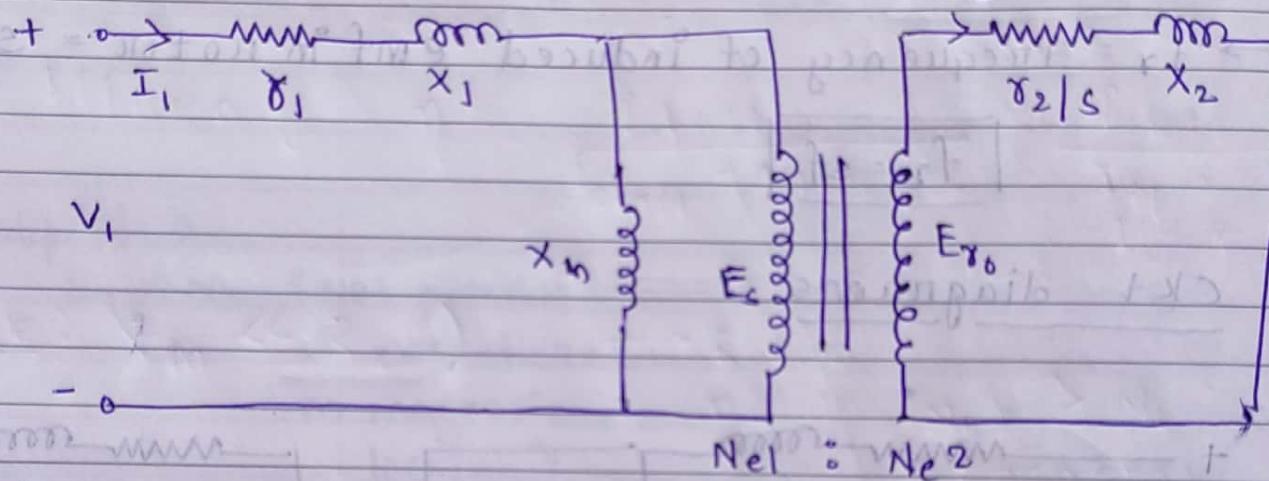→ When m/c revolves, eqn. of motion is $I_2 \ddot{\theta} = M$



w.r.t stator side -

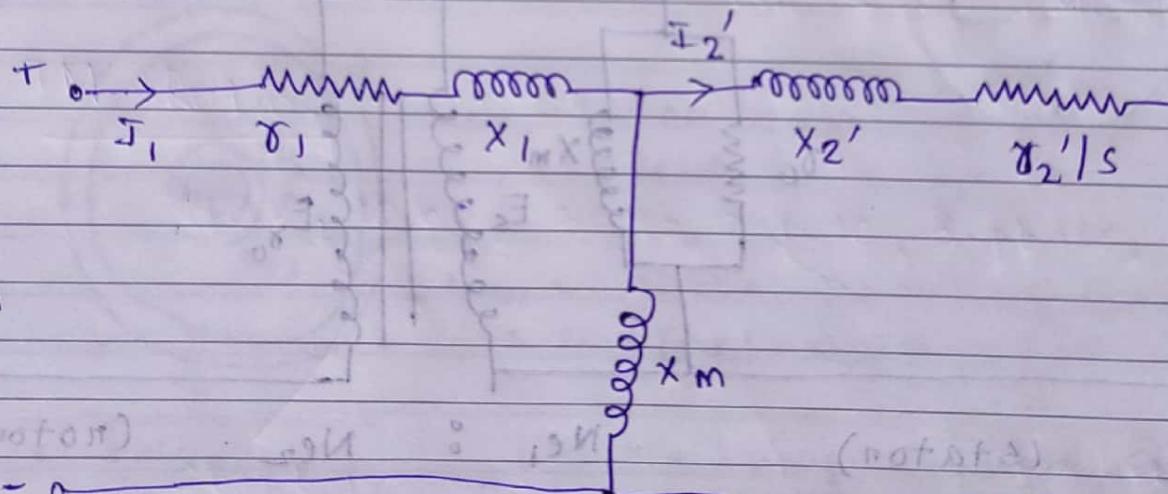

$$\text{notat} \leftarrow (\text{notat}) \cup \{x_1\}, \quad (\text{notat}) \cup \{x_1\} \neq \emptyset \Rightarrow \exists x_2' \in \text{notat} \quad x_2' = x_2 \left(\frac{N_{e1}}{N_{e2}} \right)^2$$

water
babies

5. 11. 2017 - 4
9:00 AM


Wk	M	T	W	T	F	S	S
18		1	2	3	4	5	6
19	7	8	9	10	11	12	13
20	14	15	16	17	18	19	20
21	21	22	23	24	25	26	27
22	28	29	30	31			

Wk 15 • 103 Day
FRIDAY

13

* Power and torque

Power flow in IM:

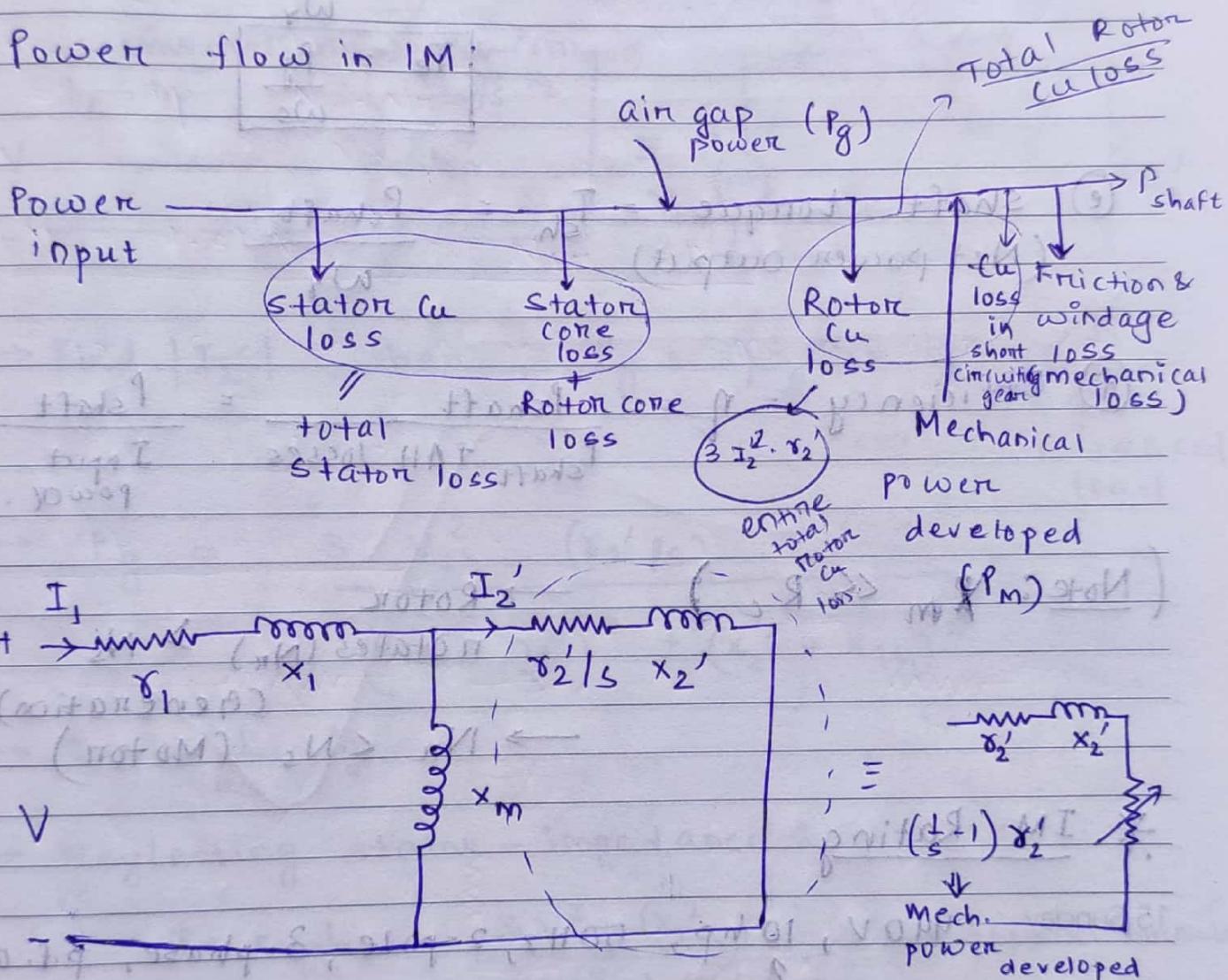

a) Air gap power = $P_g = (I_2')^2 \cdot \frac{\gamma_2'}{s} = I_2^2 \cdot \frac{\gamma_2}{s}$

b) Rotor loss, Cu = $s P_g = I_2^2 \cdot \gamma_2$

c) Mechanical power developed (gross power output)

$$\begin{aligned}
 P_m &= P_g - s P_g \\
 &= (1-s) P_g \\
 &= \left(\frac{1}{s} - 1\right) I_2^2 \cdot \gamma_2
 \end{aligned}$$

13	30
14	2
15	9
16	16
17	23
18	3
19	10
20	17
21	24
22	25
23	26
24	27
25	28
26	29
27	30
28	1
29	8
30	15

14

Wk 15 • 104 Day
SATURDAY

(d) Electromagnetic Torque = $T_e = \frac{P_m}{\omega_r}$

$$T_e = \frac{P_g}{\omega_s}$$

(e) Shaft torque = $T_{sh} = \frac{P_{shaft}}{\omega_s}$
(Net power output)

(f) Efficiency = $\eta = \frac{P_{shaft}}{P_{shaft} + \text{All losses}} = \frac{P_{shaft}}{\text{Input power}}$

(Note: $X_m \ll R_c$)

→ Rotor

rotates (N_r) > N_s

(Generation)

→ $N_r < N_s$ (Motor)

* IM (Rating)

15 Sunday 440V, 10 hp, 50Hz, 2-pole, 3-phase, p.f. of

0.85

if p ct

$\frac{P \times f \times S}{2} = \frac{P}{2} (e-1) = \frac{P}{2} = \text{rating gap in A cos} \phi$

OR

shaft power

Rated Et. also specified,

at rated load,

on Δ - connected

rated slip.

(of stator)

$$\frac{P \times f \times S}{2} (e-1) =$$

$$\frac{P \times f \times S}{2} (1-1) =$$


May 2018

Wk	M	T	W	T	F	S	S
18		1	2	3	4	5	6
19	7	8	9	10	11	12	13
20	14	15	16	17	18	19	20
21	21	22	23	24	25	26	27
22	28	29	30	31			

 Wk 16 • 106 Day
 MONDAY

16

* Torque ~ speed characteristics

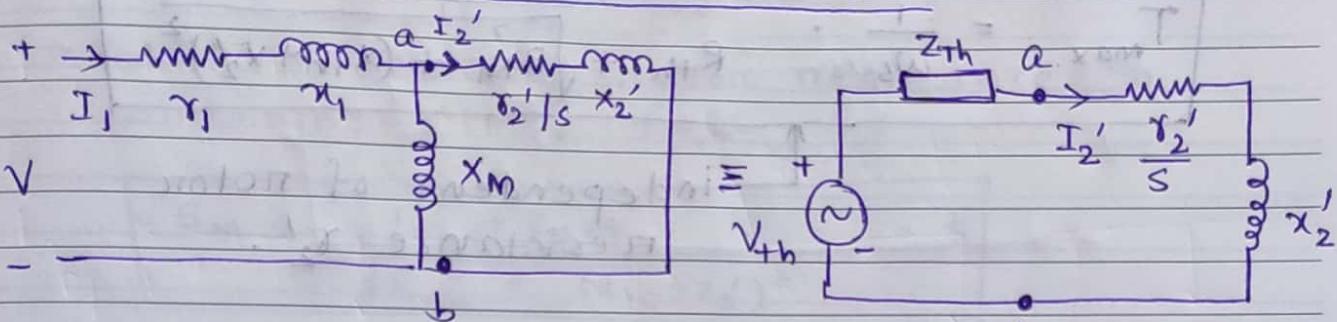

$$\rightarrow \text{Find } |I_2'|, \text{ then, } P_g = |I_2'|^2 \times \frac{R_2'}{s} \times 3$$

Balanced load

$$\rightarrow P_g = \frac{3 \cdot V_{th}^2 \cdot (R_2' / s)}{\left(R_{th} + \frac{R_2'}{s} \right)^2 + (X_2' + X_{th})^2}$$

$$\rightarrow T_e = \frac{1}{\omega_s} \cdot P_g$$

→ Neglecting stator - impedance:

$$T_e = \frac{1}{\omega_s} \cdot \frac{3V^2 \cdot (R_2' / s)}{\left(\frac{R_2'}{s} \right)^2 + (X_2')^2} \rightarrow \text{Approx. formula}$$

* Max^m torque & the corresponding slip

$$\frac{dT_e}{ds} \Big|_{s=s_m} \neq 0 \Rightarrow S_m = \frac{R_2'}{\sqrt{R_{th}^2 + (X_{th} + X_2')^2}}$$

'18 APRIL

17


 Wk 16 • 107 Day
TUESDAY

WEEK	M	T	W	T	F	S	S
13	30						8
14	2	3	4	5	6	7	1
15	9	10	11	12	13	14	8
16	16	17	18	19	20	21	15
17	23	24	25	26	27	28	22


$$T_{\max} = \frac{1}{\omega_s} \cdot \frac{1.5 V_{th}^2}{R_{th} + \sqrt{R_{th}^2 + (x_{th} + x_2')^2}}$$

independent of motor resistance R_2' .

* Plot of torque - speed ch.

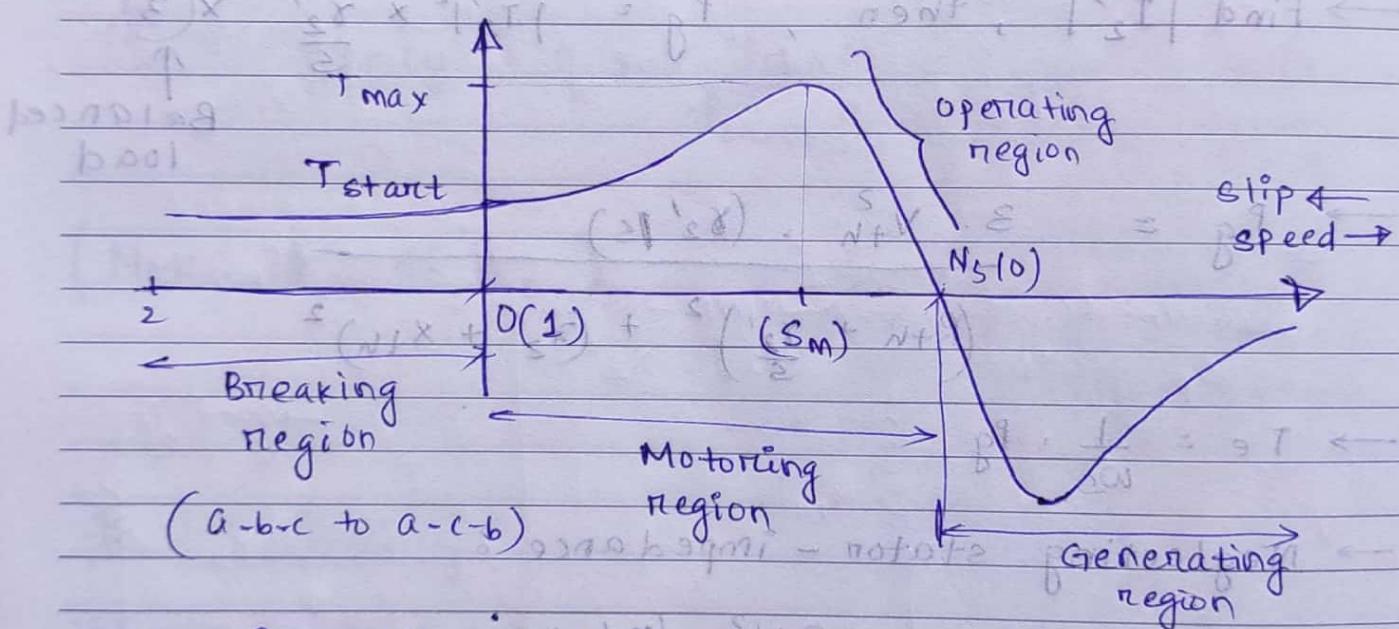

• Operating Region

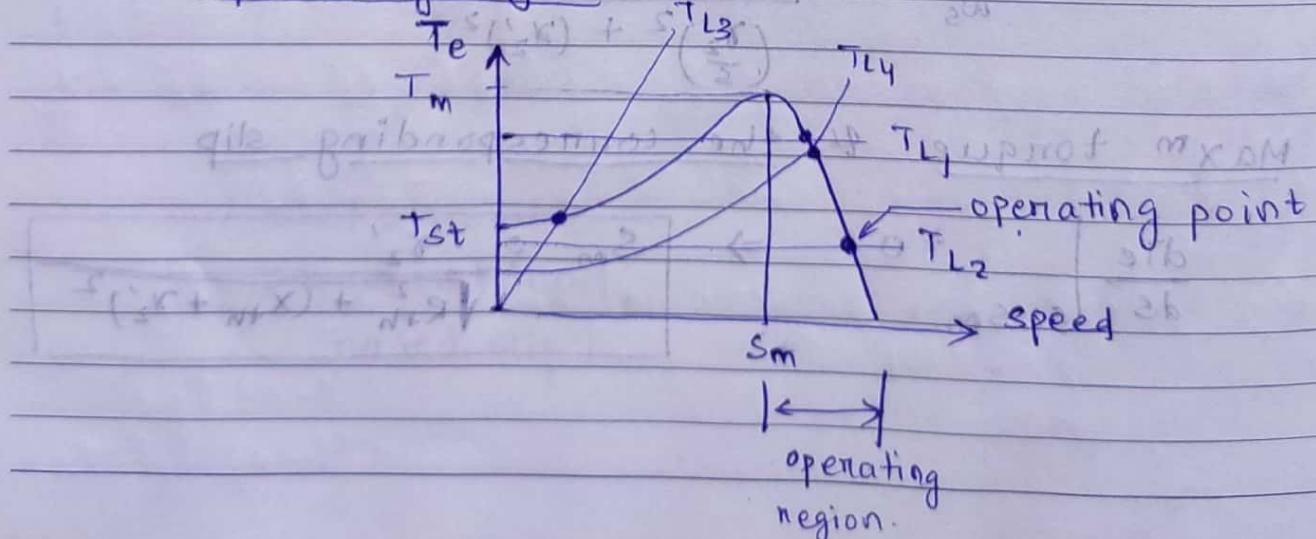

May 2018

WEEK	M	T	W	T	F	S	S
18	1	2	3	4	5	6	
19	7	8	9	10	11	12	13
20	14	15	16	17	18	19	20
21	21	22	23	24	25	26	27
22	28	29	30	31			

Wk 16 • 108 Day


WEDNESDAY

* Increase in starting torque
($s = 1$)

→ Adding externally rotor resistance to slip-rings IM. ($= R_{ext.}$)

$$S_M = \frac{R_2' + R_{ext}}{\sqrt{R_{th}^2 + (x_{th} + x_2')^2}} = 1$$
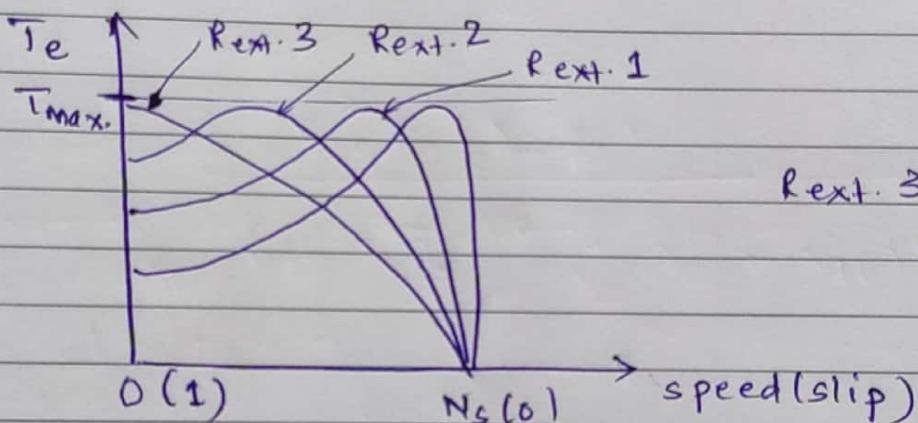
$$\approx \frac{R_2' + R_{ext}}{x_2'} = 1 \quad (\text{Neglect. stator impd})$$



* IMP. FORMULAE

$$I_{fl}^2 \propto T_{fl} = \frac{3}{\omega_s} \cdot \frac{V^2 (R_2' / s_{fl})}{(R_2' / s_{fl})^2 + (x_2')^2} \rightarrow \text{At } T_{fl}$$

$$\frac{R_2'}{s_{fl}} \gg x_2'$$

V is taken since stator impedance is not there And use

$$I_{start}^2 \propto T_{start} = \frac{3}{\omega_s} \cdot \frac{V^2 R_2'}{(R_2')^2 + (x_2')^2}$$

$$I_{max}^2 \propto T_{max} = \frac{3}{\omega_s} \cdot \frac{0.5 V^2}{x_2'}$$

$$S_{max} = \frac{R_2'}{x_2'}$$

W	K	M	T	W	T	F	S	S
13		30						1
14	2	3	4	5	6	7	8	
15	9	10	11	12	13	14	15	
16	16	17	18	19	20	21	22	
17	23	24	25	26	27	28	29	


'18 APRIL

19


Wk 16 • 109 Day

THURSDAY

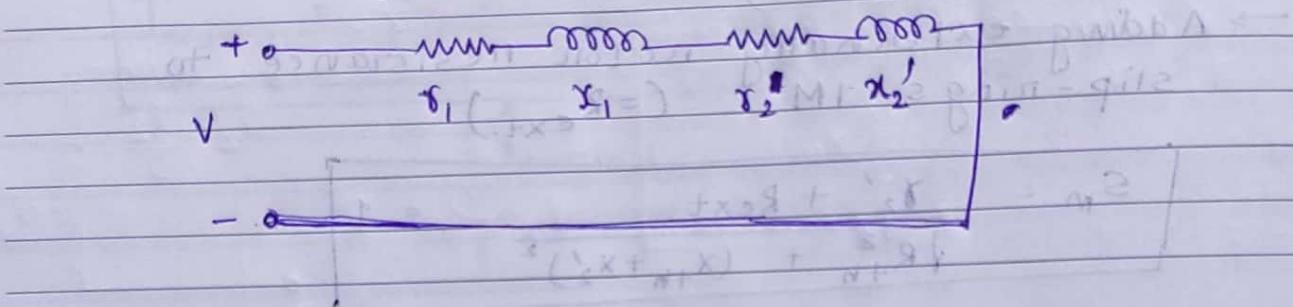* For starting of IM, the ckt diagram becomes -



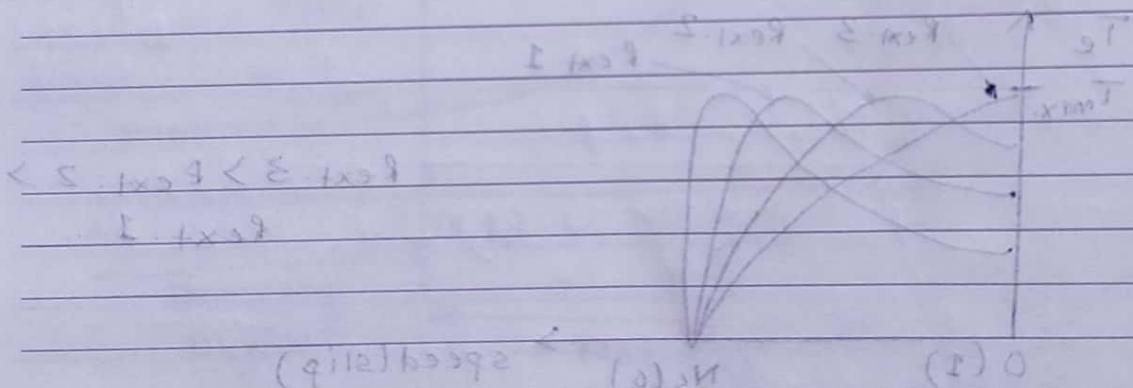(approximate analysis) $I = \frac{V}{R + j(X_1 + X_2)}$



$\omega_T / \omega_s < \frac{1}{2}$

motor is V

starts

not synchronized

starts from standstill

as usual

 $\omega_T = 0.33\pi \text{ rad/s}$
 ω_T

$$\frac{\omega_T}{\omega_s} \cdot \frac{s}{(s+1)} \cdot \frac{V}{(s+1)^2} = \frac{\omega_T}{\omega_s} \cdot \frac{V}{s^2 + 2s + 1}$$

$$sV = 0$$

$$s = 0$$

$$\omega_T = \omega_s$$

$$T = \frac{C}{\omega_s}$$