

RESONANCE

A circuit is said to be in resonance when the applied voltage V and the resulting current I are in phase.

Thus at resonance, the equivalent complex impedance of the circuit consists of only R .

Since V & I are in phase, the power factor of a resonant circuit is Unity.


Whenever the natural frequency of oscillation of a system (could be electrical, mechanical or a civil structure or a hydraulic) coincides with the frequency of the driving force (a voltage source in an electric circuit or a wind force in civil structure etc.), the two systems resonate with respect

to each other and the system has maximum response to a fixed magnitude of driving force. This phenomenon is known as resonance.

Two types of resonance in the electric circuits.

- i) Series Resonance
- ii) Parallel Resonance

SERIES RESONANCE

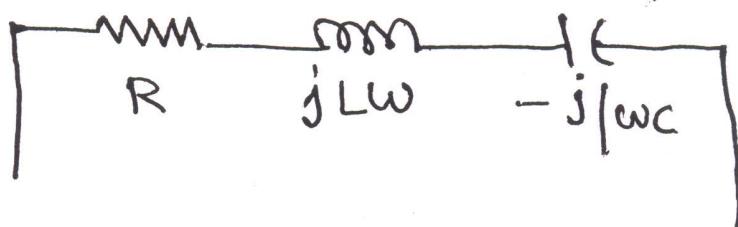

$$Z = R + j(L\omega - \frac{1}{\omega_c}) = (R + jX).$$

The circuit is in resonance


When $X=0$, i.e., when $L\omega = \frac{1}{\omega_c}$

$$\therefore \omega = \frac{1}{\sqrt{LC}} = \omega_0$$

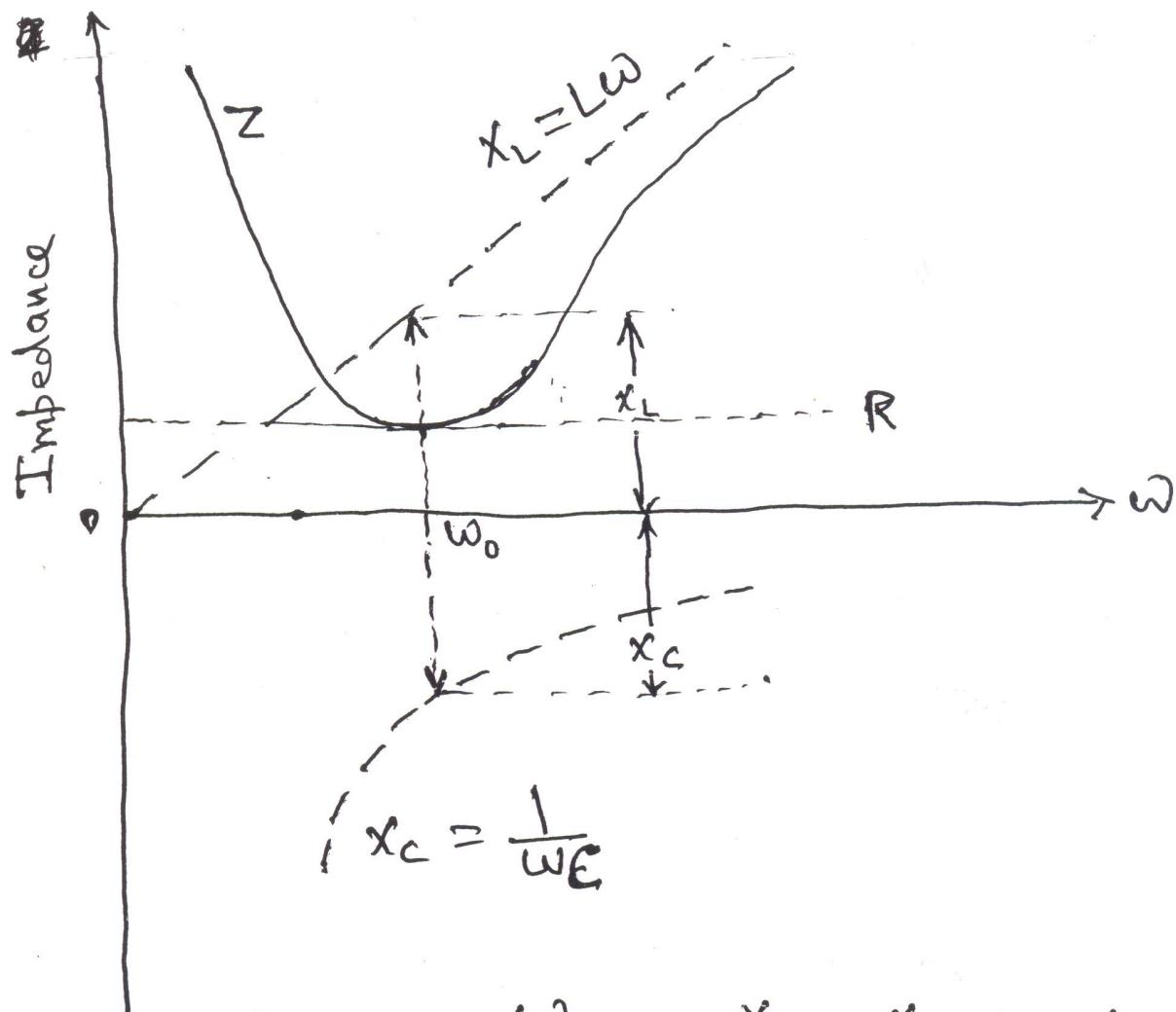(3)

Then, since $\omega = 2\pi f$, the resonant frequency is given by,

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz.}$$



$$\text{At } \omega = \omega_0, X_L = X_C ; X = 0$$

$$\therefore \text{Thus, } Z = \sqrt{R^2 + X^2} = R$$

Thus at resonance, the impedance Z is a minimum, since $I = \frac{V}{Z}$, the current is maximum.

$$\theta = \tan^{-1} \left(\frac{L\omega - \frac{1}{\omega C}}{R} \right)$$


(4)

$L\omega - \frac{1}{\omega C} < 0$
 $\omega^2 < \frac{1}{LC}$


$\omega < \frac{1}{\sqrt{LC}}$
 $\omega < \omega_0$

At frequencies below ω_0 ($\omega < \omega_0$), the capacitive reactance is greater than the inductive reactance ($\frac{1}{\omega C} > L\omega$) and θ is negative.

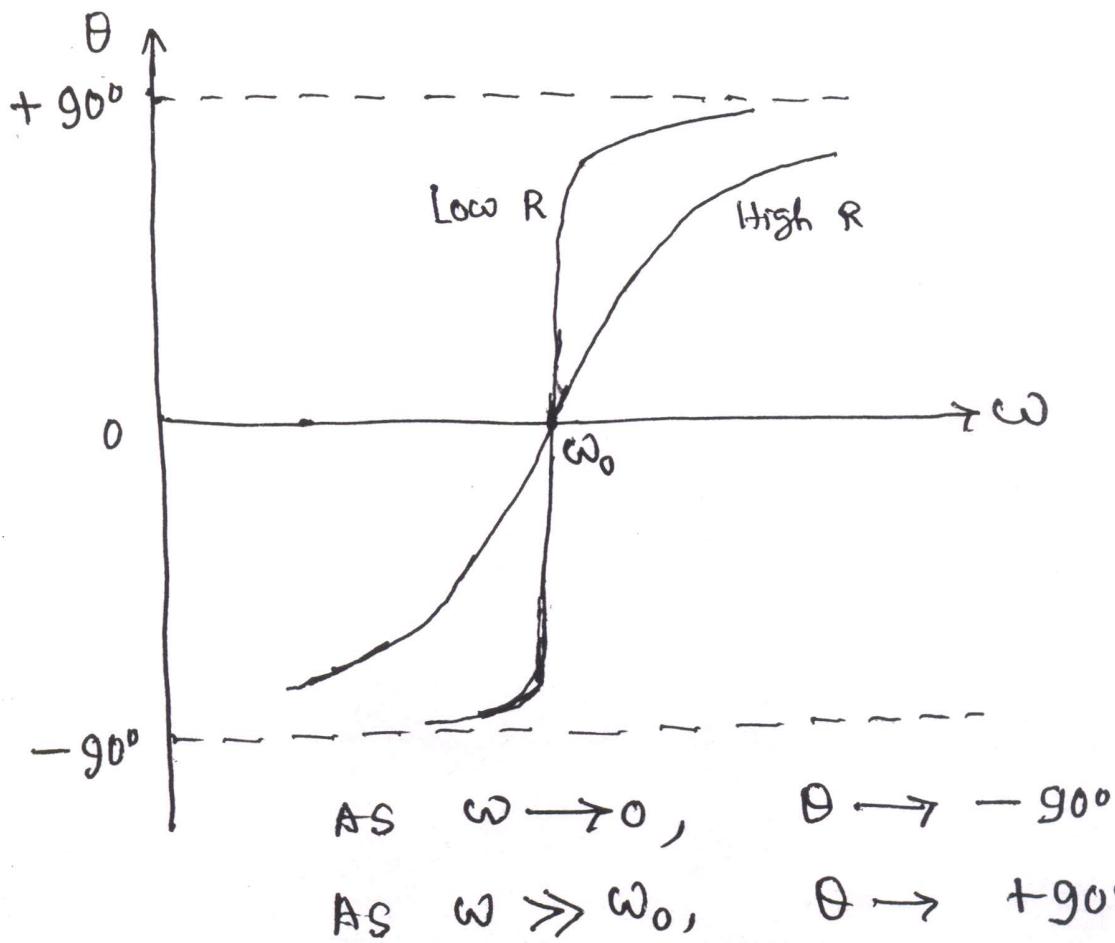If the resistance is low, the angle changes more rapidly with frequency as shown in Figure below.


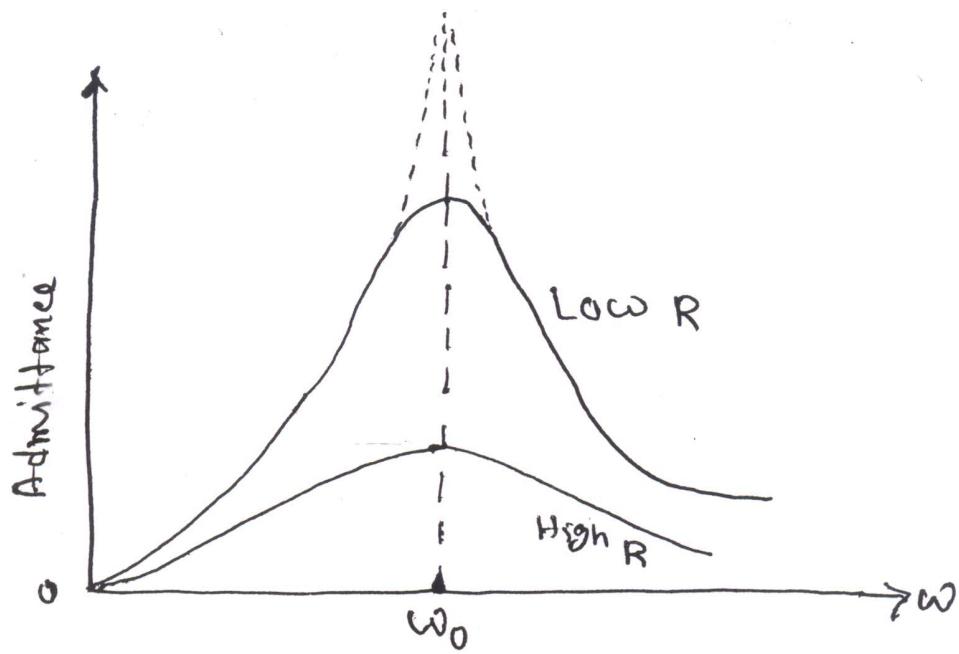
$$Y = \frac{1}{Z} ; \quad I = YV \quad (5)$$



The above plot is also an indication of
Current Versus ω .



Maximum current occurs at ω_0
and that a low resistance results in a
higher current.

The dotted curve shows the
limiting case where $R \rightarrow 0$

(6)

PARALLEL RESONANCE, PURE RLC

CIRCUIT.

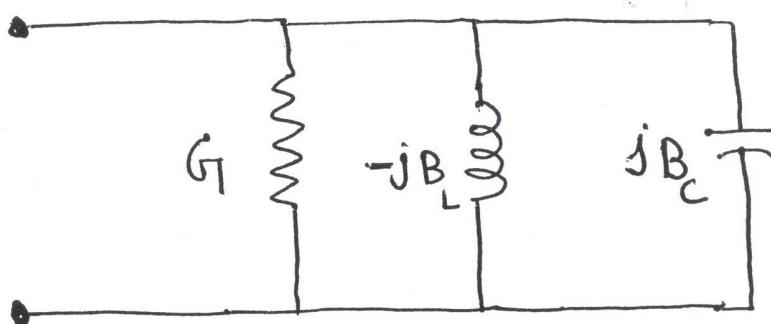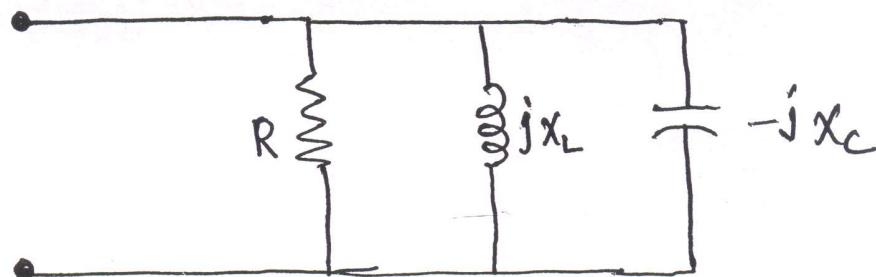

$$\boxed{\begin{aligned} G &= \frac{1}{R} \\ B_L &= \frac{1}{x_L} \\ B_C &= \frac{1}{x_C} \end{aligned}}$$

$$G = \frac{1}{R} ; \quad \boxed{\frac{1}{jx_L} = -\frac{j}{x_L} = -jB_L}$$

$$\boxed{\frac{1}{-jx_C} = \frac{j}{x_C} = jB_C}$$

$$Y = G + j(B_C - B_L) = G + j\left(\frac{1}{x_C} - \frac{1}{x_L}\right)$$

$$\boxed{Y = G + j\left(\omega_C - \frac{1}{L\omega}\right)}$$

(7)

$$\therefore Y = G + jB$$

$$\text{where } B = (B_C - B_L)$$


The circuit is in resonance when

$$B = 0, \text{ i.e., }$$

$$\omega_C = \frac{1}{L\omega} \\ \therefore \omega = \frac{1}{\sqrt{LC}} = \omega_0$$

As in the series RLC circuit, the resonant frequency is
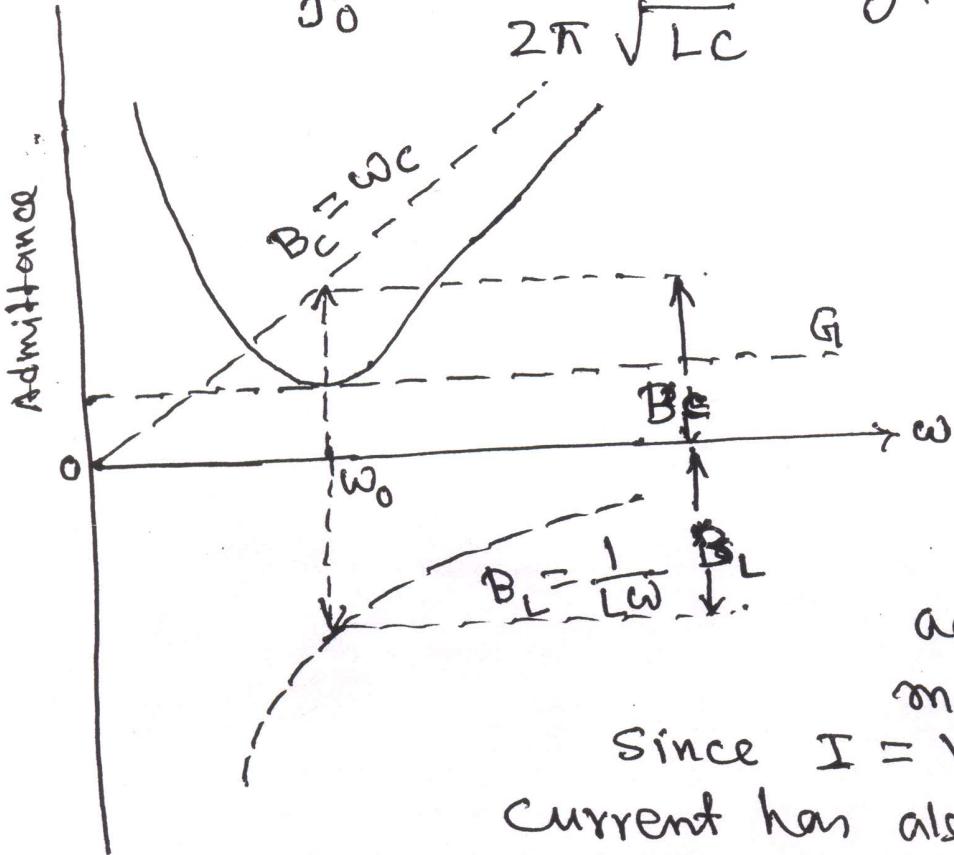
$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz.}$$




$$\text{At } \omega = \omega_0$$

$$B_C = B_L$$

$$\therefore Y = G$$


At resonance, admittance is minimum and
since $I = YV$, the current has also minimum value.

(8)

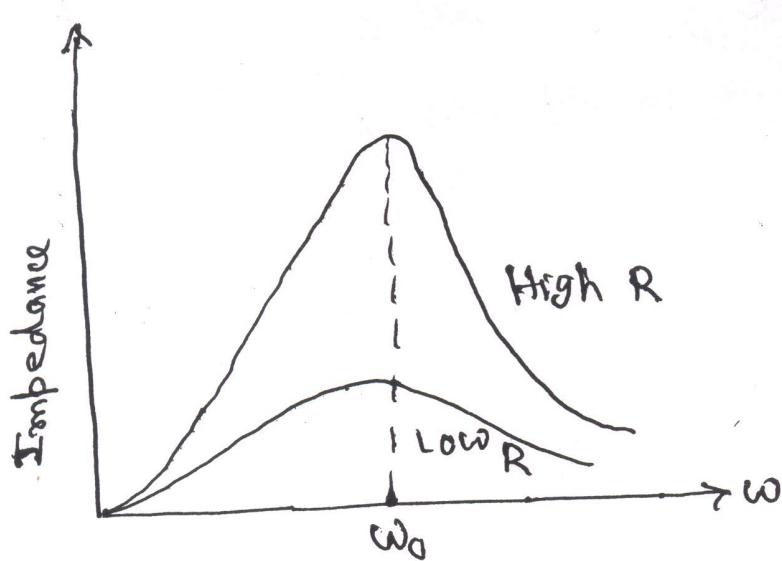

NOW, angle of admittance is given by
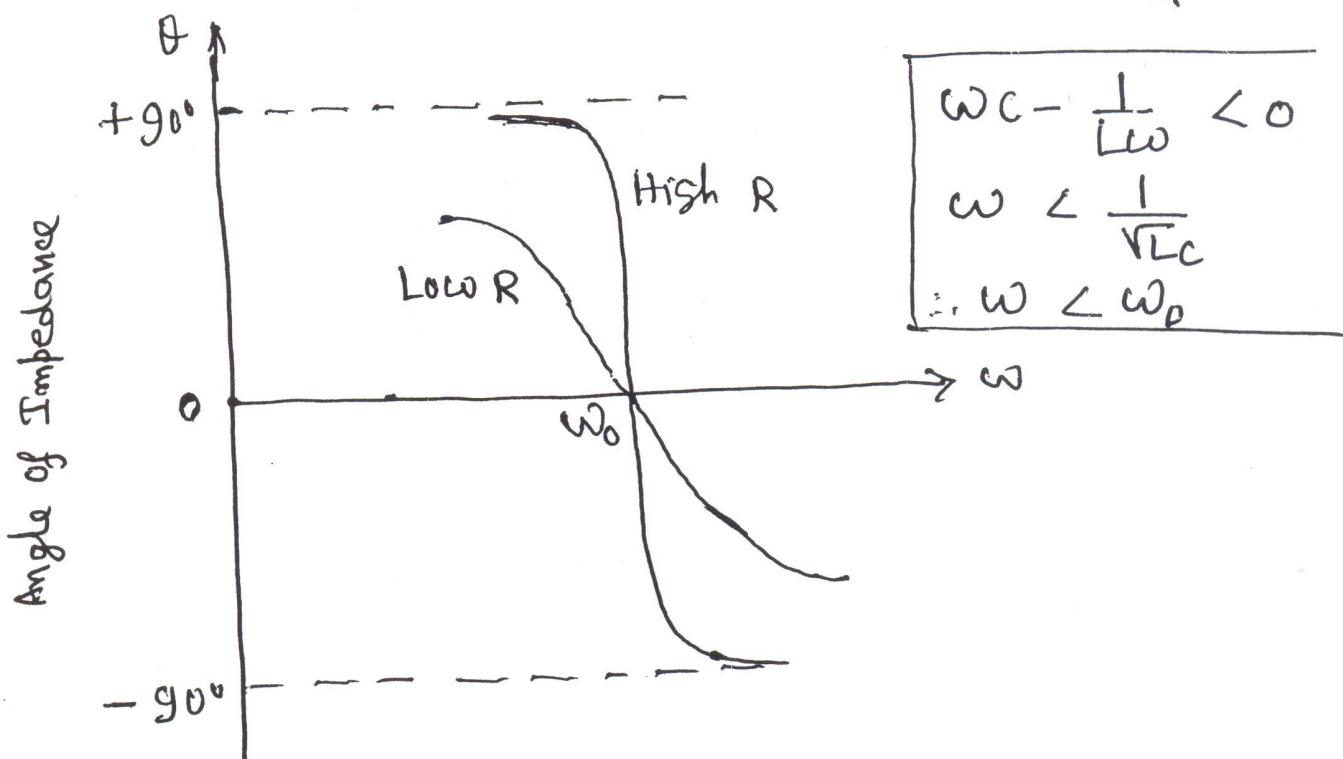
$$\theta_y = \tan^{-1} \left(\frac{B_C - B_L}{G_I} \right) = \tan^{-1} \left(\omega_C - \frac{1}{L\omega} \right)$$




At $\omega < \omega_0$, $B_L > B_C$, $\theta_y \rightarrow$ Negative.

Angle of Impedance $\theta \rightarrow$ Positive

As $\omega \rightarrow 0$, $\theta_y \rightarrow -90^\circ$, $\theta \rightarrow +90^\circ$

(9)

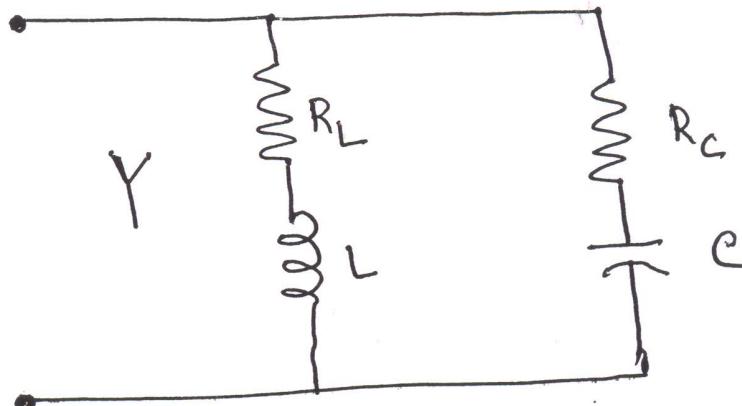At $\omega < \omega_0$ At $\omega > \omega_0$, $B_C > B_L$, $\theta_p \rightarrow$ PositiveAngle of Impedance $\theta \rightarrow$ ~~Positive~~, NegativeAs $\omega \gg \omega_0$, $\theta_p \rightarrow +90^\circ$, $\theta \rightarrow -90^\circ$ PARALLEL RESONANCE, TWO-BRANCHCIRCUIT

$$Y = Y_L + Y_C = \frac{1}{R_L + jX_L} + \frac{1}{R_C - jX_C}$$

$$= \left(\frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} \right) + j \left(\frac{X_C}{R_C^2 + X_C^2} - \frac{X_L}{R_L^2 + X_L^2} \right)$$

(10)

The circuit is at resonance when the complex admittance is a real number.

Then

$$\frac{x_c}{(R_c^2 + x_c^2)} = \frac{x_L}{(R_L^2 + x_L^2)} \quad \rightarrow (1)$$

$$\therefore \frac{1}{\omega_0 C} \left(R_L^2 + L^2 \omega_0^2 \right) = \omega_0 L \left(R_c^2 + \frac{1}{\omega_0^2 C^2} \right) \quad \rightarrow (2)$$

Each of the five quantities in Eqn.(2) may be made variable in order to obtain resonance.

Solving eqn.(1) for ω_0 , we obtain

$$\omega_0 = \frac{1}{\sqrt{LC}} \sqrt{\frac{R_L^2 - L/C}{R_c^2 - L/C}}$$

Thus the resonant frequency ω_0 of the two-branch parallel circuit differs

(11)

from that of the pure R, L and C
in parallel by the factor

$$\sqrt{\frac{R_L^2 - 4/c}{R_C^2 - 4/c}}$$

Frequency must be a real positive number

Hence the circuit will have a resonant frequency ω_0 when

$$R_L^2 > \frac{L}{c} \quad \text{and} \quad R_C^2 > \frac{L}{c}$$

OR

$$R_L^2 < \frac{L}{c} \quad \text{and} \quad R_C^2 < \frac{L}{c}$$

When $R_L^2 = R_C^2 = \frac{L}{c}$

The circuit is resonant at all frequencies

(12)

Solving Eqn.(1) for L , we obtain

$$L = \frac{1}{2}C \left[Z_c^2 \pm \sqrt{Z_c^4 - 4R_L^2 X_c^2} \right] \quad \dots \quad (3)$$

Where

$$Z_c^2 = (R_c^2 + X_c^2), \quad Z_c^4 = (R_c^2 + X_c^2)^2$$

Now if in Eqn.(3),

$$Z_c^4 > 4R_L^2 X_c^2,$$

We obtain two values of L for which the circuit is resonant.

$$\text{If } Z_c^4 = 4R_L^2 X_c^2,$$

the circuit is in resonance at

$$L = \frac{1}{2}C Z_c^2$$

$$\text{When } Z_c^4 < 4R_L^2 X_c^2,$$

No value of L will make the circuit resonant.

(13)

Similarly,
Solving Eqn.(1) for C , we obtain

$$C = \frac{2L}{Z_L^2 \pm \sqrt{Z_L^4 - 4R_C^2 X_L^2}} \quad \text{--- (4)}$$

Here if $Z_L^4 > 4R_C^2 X_L^2$, we obtain
two values of C for which the circuit
is resonant.

If $Z_L^4 = 4R_C^2 X_L^2$,

The circuit is in resonance at

$$C = \frac{2L}{Z_L^2}$$

Solving Eqn.(1) for R_L , we obtain

$$R_L = \sqrt{\omega^2 L C R_C^2 - \omega^2 L^2 + 4/C} \quad \text{--- (5)}$$

and Solving for R_C ,

$$R_C = \sqrt{\frac{R_L^2}{(\omega^2 L C)} - \frac{1}{\omega^2 C^2} + 4/C} \quad \text{--- (6)}$$



(14)

If the radicand in Eqn.(5) or (6) is positive, then we have a value for R_L or R_C for which the two-branch circuit is in resonance.

QUALITY FACTOR Q

The quality factor of coils, capacitors and circuits is defined by
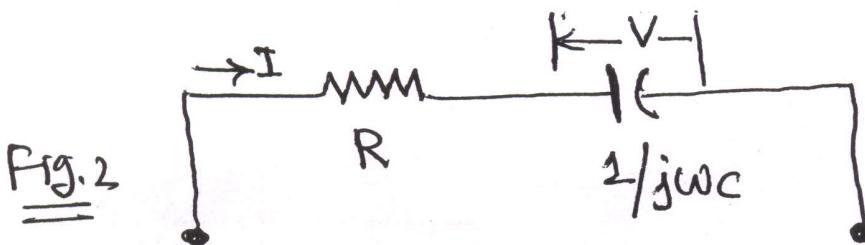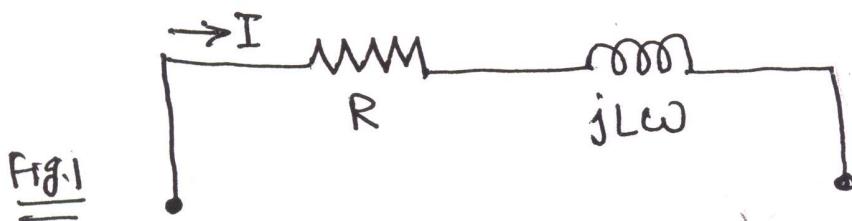
$$Q = 2\pi \left(\frac{\text{Maximum stored energy}}{\text{Energy dissipated per cycle}} \right)$$



(15)

The energy dissipated per cycle in the circuits of Fig. 1 and Fig. 2 is given by the product of the average power in the resistor $\left(\frac{I_{\max}}{\sqrt{2}}\right)^2 R$ and the period T or $\frac{1}{f}$

In the RL series circuit of Fig. 1, the maximum stored energy is $\frac{1}{2} L I_{\max}^2$. Then

$$\alpha = 2\pi \left(\frac{\frac{1}{2} L I_{\max}^2}{\left(\frac{I_{\max}}{\sqrt{2}}\right)^2 R \times \left(\frac{1}{f}\right)} \right)$$

$$\therefore \alpha = \frac{2\pi f L}{R} = \frac{L\omega}{R}$$

In the RC series circuit of Fig. 2, the maximum stored energy is $\frac{1}{2} C V_{\max}^2$ OR $\frac{1}{2} I_{\max}^2 / \omega_C^2$

$$\boxed{V_{\max} = I_{\max} \cdot R}$$


(16)

Then

$$\alpha = 2\pi \left(\frac{\frac{1}{2} I_{\text{max}}^2 / \omega^2 C}{\left(\frac{I_{\text{max}}^2}{2} \right) \cdot R \cdot \left(\frac{1}{f} \right)} \right)$$

$$\therefore Q = \frac{1}{\omega C R}$$


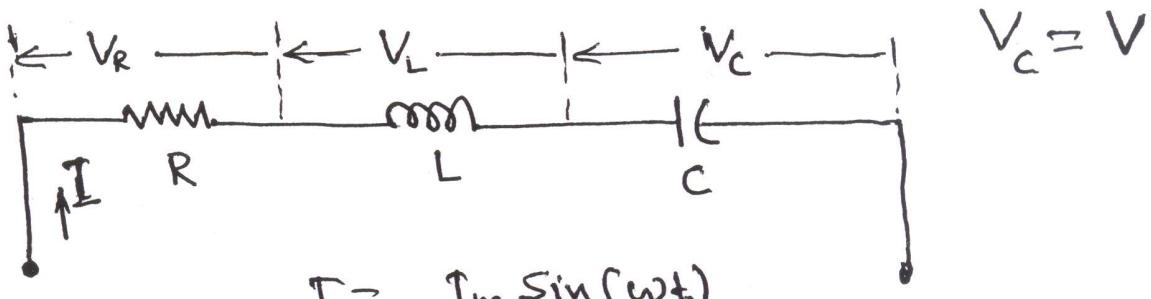
A series RLC circuit at resonance stores a constant amount of energy.



$$I = I_m \sin(\omega t)$$

$$V = V_C = \frac{1}{C} \int I_m \sin(\omega t) dt = \frac{I_m}{\omega C} (-\cos \omega t)$$
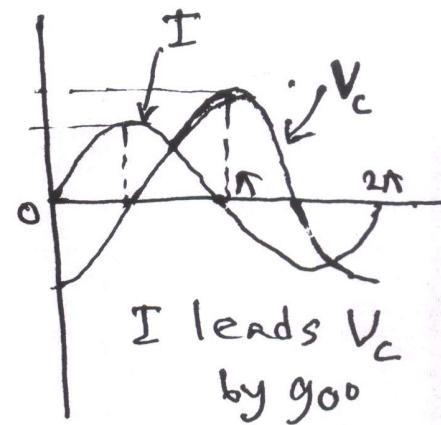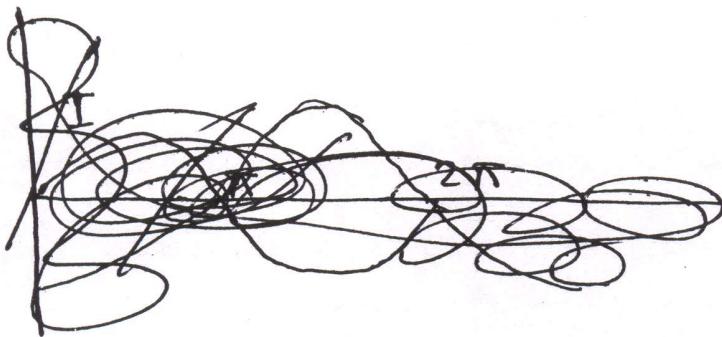
$$\therefore V = \frac{I_m}{\omega C} \sin(\omega t - 90^\circ)$$




(17)

Since when the capacitor voltage is maximum, the inductor current is zero, and vice versa, $\frac{1}{2} CV_{\max}^2 = \frac{1}{2} L I_{\max}^2$,

Then

$$Q_0 = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$
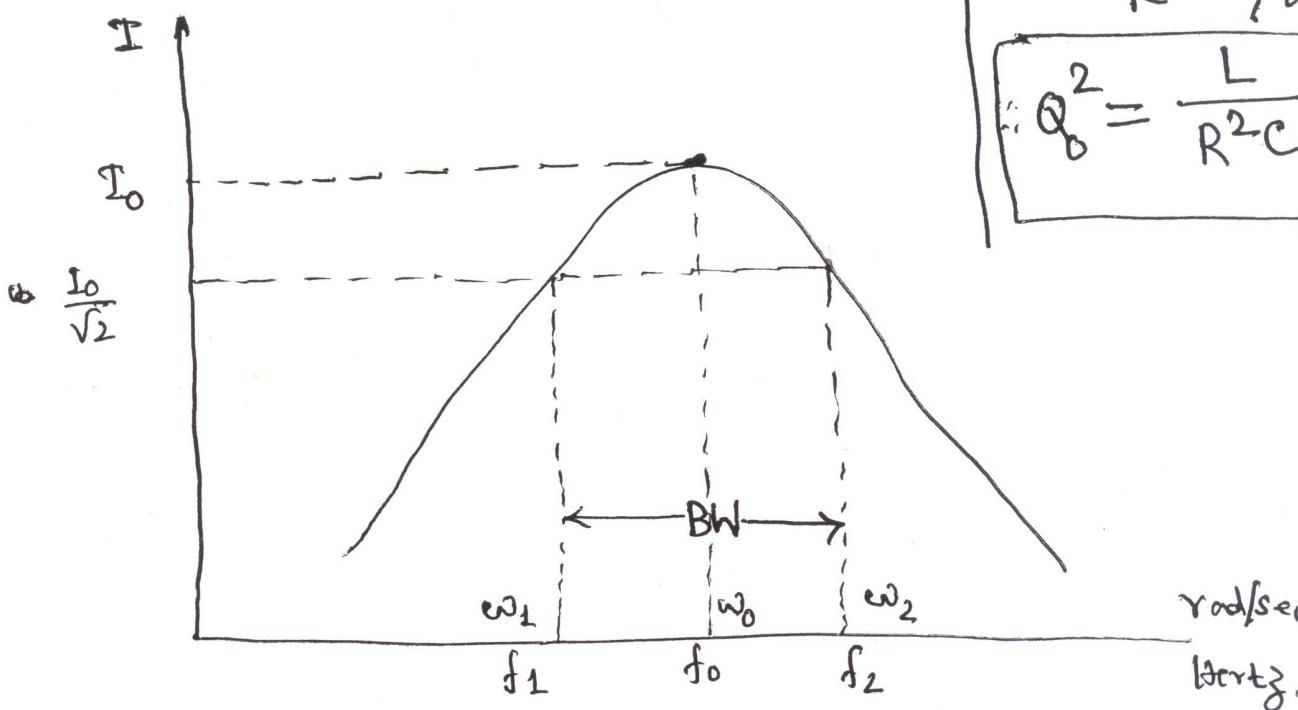
$$\begin{aligned} Q_0 \times Q_0 \\ = \frac{\omega_0 L}{R} \times \frac{1}{\omega_0 C R} \\ \therefore Q_0^2 = \frac{L}{R^2 C} \end{aligned}$$



At ω_0 , current is maximum

Since the power delivered to the circuit is $I^2 R$, at $I = \frac{I_0}{\sqrt{2}}$, the power is one-half of the maximum value which occurs at ω_0 . The points corresponding

to ω_1 and ω_2 are called the half-power points. The distance between these points is called the bandwidth.

BW.

At half-power frequencies, the net reactance is equal to the resistance

A circuit with high Q will have a very sharp current response curve as compared to one which has a low value of Q .

~~Set up~~ We specify two frequencies ω_1 & ω_2 at which $|X_L - X_C| = R$

Since at ω_1 , the circuit is capacitive ($X_C > X_L$), therefore at ω_1 ,

$$X_C - X_L = R \quad \dots \text{(i)}$$

at ω_2

$$X_L - X_C = R \quad \dots \text{(ii)}$$

The corresponding impedances are:

(19)

At ω_1

$$Z_1 = R + j(x_L - x_C) = R - jR$$

$$\therefore Z_1 = \sqrt{2} R \angle -45^\circ$$

At ω_2

$$Z_2 = \sqrt{2} R \angle 45^\circ$$

$$\text{At } \omega_1, I_1 = \frac{V \angle 0^\circ}{\sqrt{2} R \angle -45^\circ} = \frac{V}{\sqrt{2} R} \angle 45^\circ$$

Similarly, at ω_2

$$I_2 = \frac{V}{\sqrt{2} R} \angle -45^\circ$$

Since $\frac{V}{R} = I_0$, the current at resonance frequency ω_0 .

$$\begin{aligned} \therefore I_1 &= 0.707 I_0 \angle 45^\circ \\ I_2 &= 0.707 I_0 \angle -45^\circ \end{aligned} \quad \left. \right\}$$

At ω_1 ,

$$x_C - x_L = R$$

(20)

$$\frac{1}{\omega_1 C} = \infty \quad L\omega_1 = R \quad \text{--- (iii)}$$

At ω_2

$$X_L - X_C = R$$

$$\therefore L\omega_2 - \frac{1}{\omega_2 C} = R \quad \text{--- (iv)}$$

Eqn. (iii) - Eqn. (iv)

$$\therefore \left(\frac{1}{\omega_1} + \frac{1}{\omega_2} \right) \frac{1}{C} - (\omega_1 + \omega_2) L = 0$$

$$\therefore \frac{1}{\omega_1 \omega_2} = LC = \frac{1}{\omega_0^2}$$

$$\therefore \boxed{\omega_0 = \sqrt{\omega_1 \omega_2} \quad \text{--- (v)}}$$

Again

Eqn (iii) + Eqn. (iv)

$$\frac{1}{\omega_1 C} - L\omega_1 + L\omega_2 - \frac{1}{\omega_2 C} = 2R$$

$$\therefore \frac{\omega_2 - \omega_1}{\omega_1 \omega_2 C} + (\omega_2 - \omega_1) L = 2R$$

(21)

$$(\omega_2 - \omega_1) \left(\frac{1}{\omega_0^2 C} + L \right) = 2R$$


$$\therefore \frac{(\omega_2 - \omega_1) (1 + LC\omega_0^2)}{\omega_0^2 C} = 2R$$

$$\therefore (\omega_2 - \omega_1) \left(\frac{1}{\omega_0^2 C} \right) = 2R$$

$$\therefore \omega_2 - \omega_1 = \omega_0^2 CR$$

$$\therefore \frac{\omega_2 - \omega_1}{\omega_0} = \omega_0 CR = \frac{1}{Q_0}$$

$$\therefore Q_0 = \frac{\omega_0}{\omega_2 - \omega_1} \quad \text{--- (vi)}$$

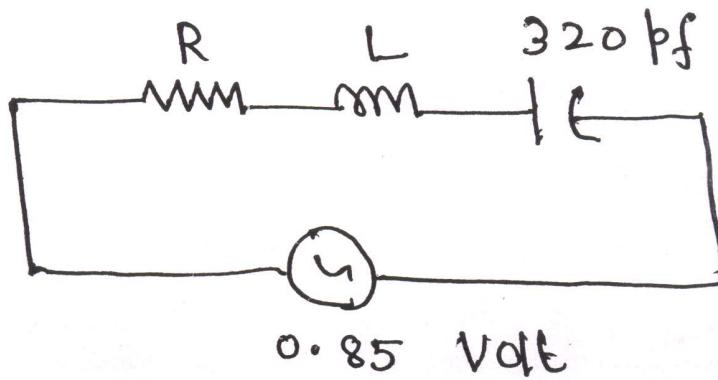EX-1

(22)

Determine the value of L for resonance if $Q = 50$ and $f_0 = 175 \text{ kHz}$. Also find the circuit current, the voltage across the capacitor and the bandwidth of the circuit.

Sohm

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\therefore 175 \times 10^3 = \frac{1}{2\pi\sqrt{320 \times 10^{-12} L}}$$

$$\therefore L = 2.58 \text{ mH}$$

~~The \rightarrow case done~~

$$X_L = L\omega = 2.58 \times 10^{-3} \times 2\pi \times 175 \times 10^3 \text{ v2}$$

$$\therefore X_L = 2840 \text{ v2}$$

$$\text{Since } Q = \frac{\omega_0 L}{R}$$

$$\therefore R = \frac{\omega_0 L}{Q} = \frac{175 \times 10^3 \times 2.58 \times 10^{-3}}{50}$$

$$\therefore R = 56.8 \text{ v2}$$

(23)

The impedance of the circuit at resonance is

$$Z = R = 56.8 \Omega.$$

$$\therefore I_0 = \frac{V}{R} = \frac{0.85}{56.8} = 14.96 \text{ mA.}$$

Also

$$V_C = \frac{I_0}{\omega_0 C} = \frac{R I_0}{\omega_0 C R} = \cancel{\text{scratches}}$$

$\therefore V_C = QV$

Voltage across the capacitor

$$= QV = 50 \times 0.85 = 42.5 \text{ Volt.}$$

B Bandwidth, $= (\omega_2 - \omega_1)$

~~BW~~ ~~scratches~~ ~~scratches~~

$$Q = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{f_0}{f_2 - f_1} = \frac{f_0}{BW}$$

$\therefore BW = \frac{f_0}{Q} = \frac{175 \times 10^3}{50} = 3.5 \text{ kHz.}$

(24)


Ex-2: For the circuit shown in Figure,

$$R_1 = 0.5\Omega, R_2 = 1.5\Omega, R_3 = 0.5\Omega,$$

$$C_1 = 6\mu F \text{ and } C_2 = 12\mu F, L_1 = 25\text{mH}$$

$$\text{and } L_2 = 15\text{mH}.$$

Determine (i) the frequency of resonance
(ii) Q of the circuit (iii) Q of coil 1
and coil 2, individually.

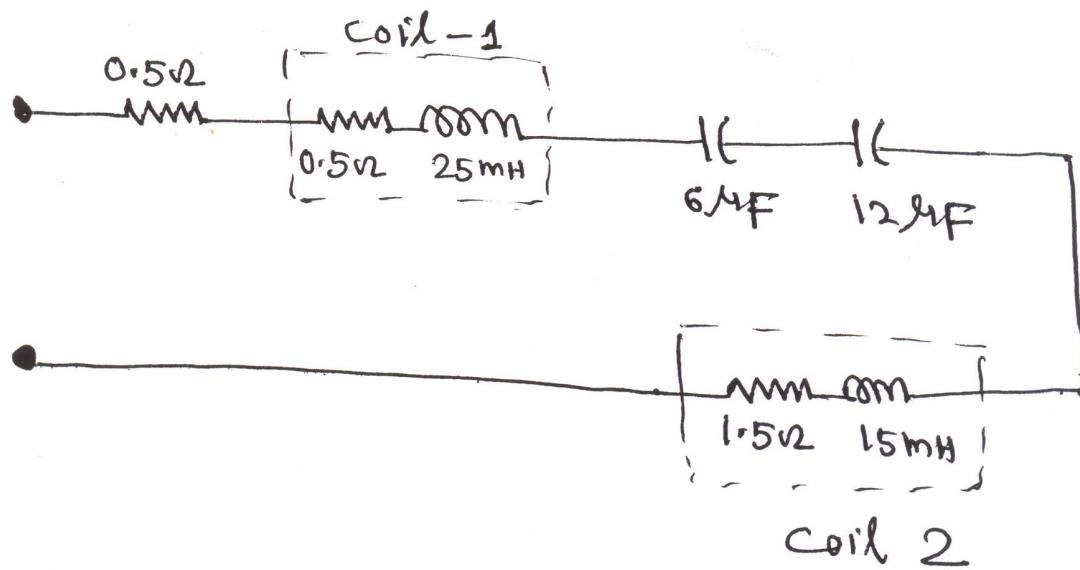Sohm.

Total inductance of the circuit

$$L = (25 + 15) = 40\text{mH}$$

$$\text{Total } C = \frac{6 \times 12}{(6+12)} = 4\mu F.$$

(25)

$$\therefore f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{40 \times 10^{-3} \times 4 \times 10^{-6}}} \quad \text{Ans}$$

$$\therefore f_0 = \frac{10^4}{8\pi} \text{ Hz.}$$

OR $\omega_0 = 2.5 \times 10^3 \text{ rad/sec.}$

$$Q \text{ of the circuit} = \frac{L\omega_0}{R}$$

$$= -\cancel{2.5} \times \cancel{2.5} \times 10^3 \times 40 \times 10^{-3} = 125 \text{ Ans} \checkmark$$

$$Q = 125 \text{ Ans} \checkmark$$

$$Q \text{ of coil 1} = \frac{L_1 \omega_0}{R_1} = \frac{2.5 \times 10^{-3} \times 2.5 \times 10^3}{0.5} = 125 \text{ Ans}$$

$$Q \text{ of coil 2} = \frac{L_2 \omega_0}{R_2} = \frac{25 \times 10^{-3} \times 2.5 \times 10^3}{1.5}$$

$$= 25$$

$$BW = \frac{f_0}{Q} = \frac{10^4}{8\pi \times 125} \text{ Hertz.} \approx 10 \text{ Hz.}$$

Ex-3

A coil having a 5Ω resistor is connected in series with a $50\mu F$ capacitor. The circuit resonates at 100 Hz. (a) determine the inductance of the coil (b) If the circuit is connected across a 200 Volt, 100 Hz source, determine the power delivered to the coil (c) voltage across the capacitor and the coil (d) BW of the circuit.

Soln.

$$\text{At resonance, } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\therefore 2\pi f_0 = \frac{1}{\sqrt{LC}}$$

$$\therefore 2\pi \times 100 = \frac{1}{\sqrt{50 \times 10^{-6} \times L}}$$

$$\boxed{\therefore L = 50 \text{ mH}}$$

$$\text{The current at resonance } \frac{V}{R} = \frac{200}{5} = 40 \text{ Amp}$$

(27)

Power dissipated = $(40)^2 \times 5 = 8000$ Watts,
 $= 8\text{ kW.}$

Voltage across capacitor = $I \times C$

$$= \frac{40}{50 \times 10^{-6} \times 100 \times 2\pi} = \frac{8000 \text{ Volt}}{2\pi}$$

$$= 127.32 \text{ Volt} \Rightarrow 1273.2 \text{ V.}$$

The Impedance of the coil

$$= R + jL\omega$$

$$= 5 + j 50 \times 10^3 \times 2\pi \times 100 = (5 + j 31.4) \Omega$$

$$V_L = \cancel{I_k} \cdot 40 \times (5 + j 31.4) = 1256 \text{ Volt}$$

$$\text{Q}_0 \text{ if the coil} = \frac{31.4}{5} = 6.3$$

$$BW = \frac{f_0}{Q_0} = \frac{100}{6.3} = 16 \text{ Hz.}$$

(28)

Ex-4: A Series circuit with $R = 50\Omega$, $L = 0.05H$ and $C = 20\mu F$ has an applied voltage $V = 100 \angle 0^\circ$ Volt with a variable frequency. Find the maximum voltage across the inductor as the frequency is varied.

Soh

$$Z = \sqrt{R^2 + (L\omega - \frac{1}{\omega C})^2}$$

$$I = \frac{V}{\sqrt{R^2 + (L\omega - \frac{1}{\omega C})^2}}$$

Magnitude of the voltage across L is

$$V_L = I(L\omega) = \frac{\omega L V}{\sqrt{R^2 + (L\omega - \frac{1}{\omega C})^2}}$$

Setting the derivative $\frac{dV_L}{d\omega}$ of eqn-(1) equal to zero and solving for ω , we obtain the value of ω when V_L is a maximum

$$\frac{dV_L}{d\omega} = \frac{d}{d\omega} \left[\omega L V \left(R^2 + \omega^2 L^2 - \frac{2L}{C} + \frac{1}{\omega^2 C^2} \right)^{-\frac{1}{2}} \right] \quad (29)$$

$$1. \quad R^2 - \frac{2L}{C} + \frac{2}{\omega^2 C^2} = 0$$

$$\therefore \omega = \frac{1}{\sqrt{LC}} \sqrt{\frac{2}{2 - \frac{R^2 C}{L}}} \quad (2)$$

Since $Q_0 = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$

$$\therefore Q_0^2 = \frac{L}{R^2 C} \quad \dots \quad (3)$$

$$\therefore \frac{R^2 C}{L} = \frac{1}{Q_0^2} \quad \dots \quad (4)$$

$$\therefore \omega = \frac{1}{\sqrt{LC}} \sqrt{\frac{2}{2 - \frac{1}{Q_0^2}}}$$

$$\therefore \omega = \frac{1}{\sqrt{LC}} \sqrt{\frac{2Q_0^2}{(2Q_0^2 - 1)}} \quad \dots \quad (5)$$

Eqn.(5) shows that for high Q , the maximum voltage across L occurs at

(30)

$$\omega_0 \approx \frac{1}{\sqrt{LC}}$$

If Q is high, maximum voltage are also obtained across R and C at ω_0 .

With low Q , V_C maximum occurs below ω_0 and V_L maximum occurs above ω_0 .

From eqn.(2),

$$\omega = \sqrt{\frac{2}{2LC - R^2 C^2}}$$

$$\therefore \omega = \left[\frac{2}{2(0.05)(20 \times 10^{-6}) - (50 \times 20 \times 10^{-6})^2} \right]^{\frac{1}{2}}$$

$$\therefore \omega = 1414 \text{ rad/sec.}$$

(31)

$$X_L = L\omega = 70.7 \Omega$$

$$X_C = \frac{1}{\omega C} = 35.4 \Omega$$


$$Z = 50 + j(70.7 - 35.4)$$

$$\therefore Z = 61.2 \sqrt{35.3^2} \Omega$$

$$I = \frac{V}{Z} = \frac{100}{61.2} = 1.635 \text{ Amp.}$$

$$V_L(\max) = 1.635 \times 70.7 \text{ Volt}$$

$$1. V_L(\max) = 115.5 \text{ Volt.}$$

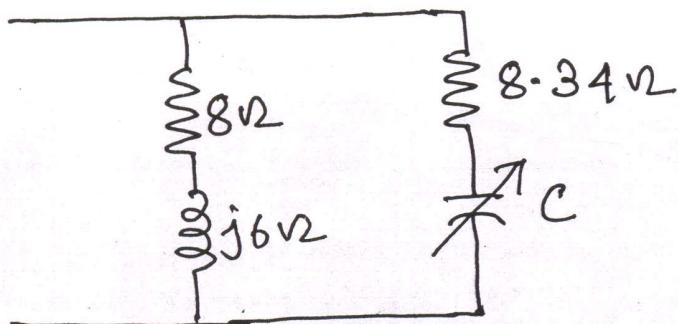EX-5

Find C
which results
in resonance
when
 $\omega_0 = 5000 \text{ rad/sec.}$

(32)

$$Y = \frac{1}{8+j6} + \frac{1}{8.34-jX_C}$$

$$\therefore Y = \left(\frac{8}{100} + \frac{8.34}{69.5+X_C^2} \right) + j \left(\frac{X_C}{69.5+X_C^2} - \frac{6}{100} \right)$$


At resonance

$$\frac{X_C}{69.5+X_C^2} - \frac{6}{100} = 0$$

$$\therefore X_C = 8.35 \Omega = \frac{1}{\omega_0 C}$$

$$\therefore C = \frac{1}{5000 \times 8.35} = 29 \mu F$$


E* - 6

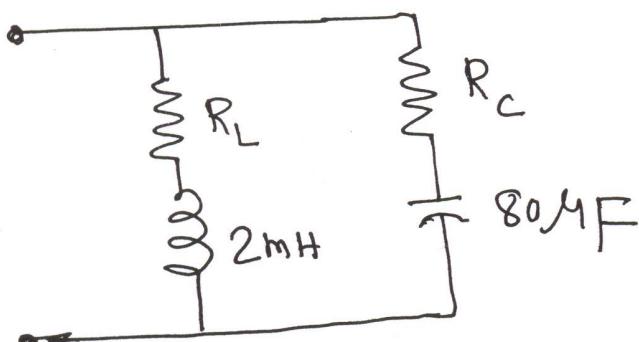

Determine R_L & R_C which cause the circuit to be resonant at all frequencies.

Maximum Power Transfer Theorems

Case-1: Load : Variable resistance R_L

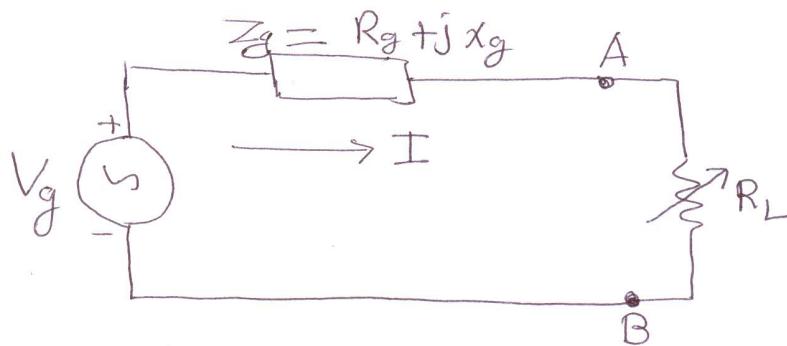

$$I = \frac{V_g}{(R_g + R_L) + jx_g}$$

$$\therefore |I| = \frac{V_g}{\sqrt{(R_g + R_L)^2 + x_g^2}}$$

$$P = |I|^2 R_L = \frac{V_g^2 R_L}{(R_g + R_L)^2 + x_g^2}$$


$$\frac{dP}{dR_L} = 0$$

$$\therefore R_L^2 = R_g^2 + x_g^2$$

$$\therefore R_L = \sqrt{R_g^2 + x_g^2} = |Z_g|$$

$$\text{If } x_g = 0, \quad \therefore R_L = R_g.$$

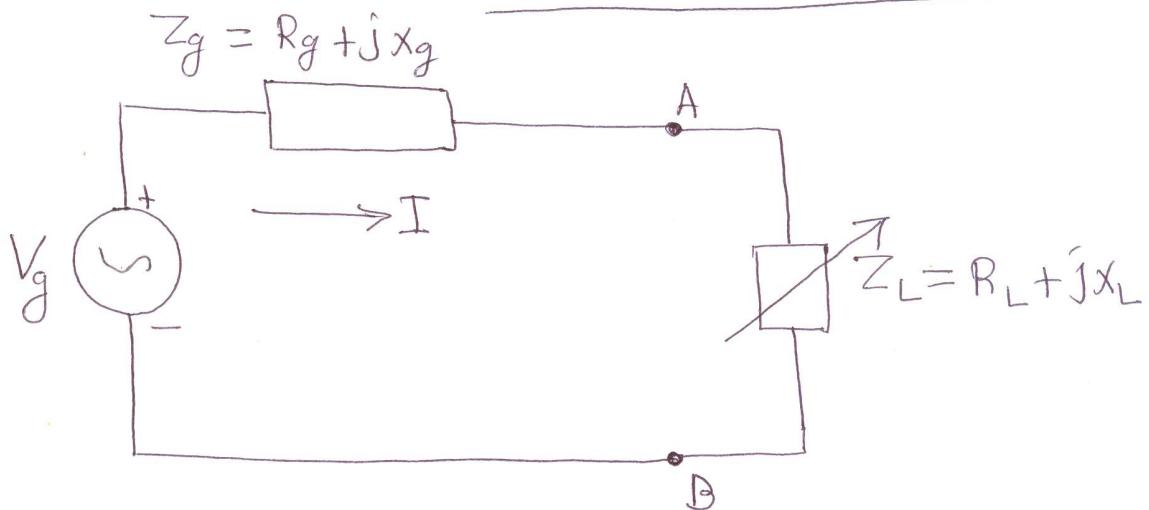Case 2: Load: Impedance Z_L with
Variable resistance and
Variable reactance.



$$I = \frac{V_g}{(R_g + R_L) + j(x_g + x_L)}$$

$$\therefore |I|^2 = \frac{V_g^2}{\sqrt{(R_g + R_L)^2 + (x_g + x_L)^2}}$$

$$\therefore P = |I|^2 R_L = \frac{V_g^2 R_L}{(R_g + R_L)^2 + (x_g + x_L)^2} \quad \dots \text{(i)}$$

If R_L in Eqn.(i) is held fixed, the value of P is maximum when $x_g = -x_L$.

Then Eqn.(i) becomes

$$P = \frac{V_g^2 R_L}{(R_g + R_L)^2} \quad \dots \text{(ii)}$$

Consider now R_L to be variable.

As shown in Case-1, the maximum power is delivered to the load when $R_L = R_g$.

If $R_L = R_g$ and $X_L = -X_g$,


then $Z_L = R_L + jX_L = R_g - jX_g$

$$\therefore Z_L = Z_g^* \quad \dots \text{(iii)}$$

Case-3:

$$R_L = |Z_g + jX_L|$$

$$\therefore R_L = |R_g + j(X_g + X_L)|$$

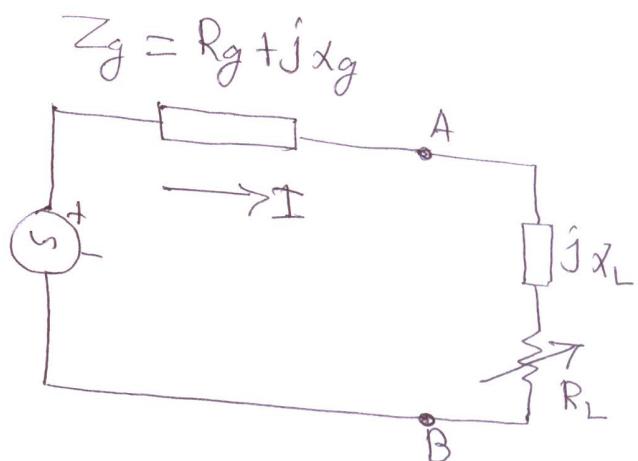

Ex-1:

(36)

In the circuit of Fig. 1, the load Z_L consists of a pure resistance R_L .

Find the value of R_L for which the source delivers maximum to the load.

Determine the value of the maximum power P .

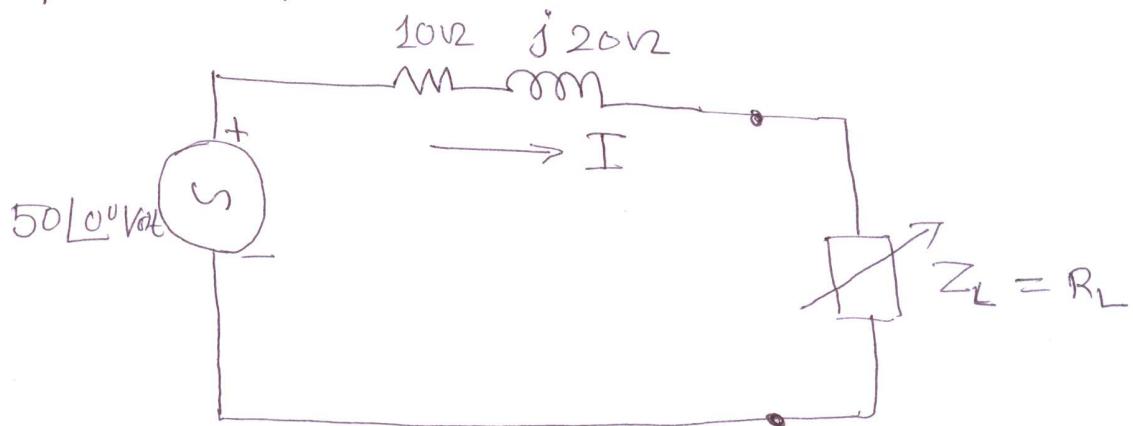


Fig. 1.

Sohm

$$R_L = |Z_g| = |10 + j20| = 22.4 \Omega$$

$$I = \frac{V_g}{(Z_g + R_L)} = \frac{50\angle 0^\circ}{(10 + j20 + 22.4)} = 1.31\angle -31.7^\circ \text{ A}$$

$$P = (1.31)^2 \times 22.4 = 38.5 \text{ Watt.}$$

Ex-2:

Repeat Ex-1, with $Z_L = R_L + jX_L$, ~~and~~

R_L & X_L are both variable.

Sohm.

$$Z_L = Z_g^* = 10 - j20$$

Total Impedance,


$$Z_T = Z_g + Z_L = 10 + j20 + 10 - j20 = 20\ \Omega$$

$$I = \frac{50 \angle 0^\circ}{20} = 2.5 \angle 0^\circ \text{ Amp.}$$

$$P = (2.5)^2 \times 10 = 62.5 \text{ Watt.}$$

Ex-3:

In the circuit shown in Fig. 2, the resistance R_g is variable between 2 and $55\ \Omega$. What value of R_g results in maximum power transfer across the terminals AB?

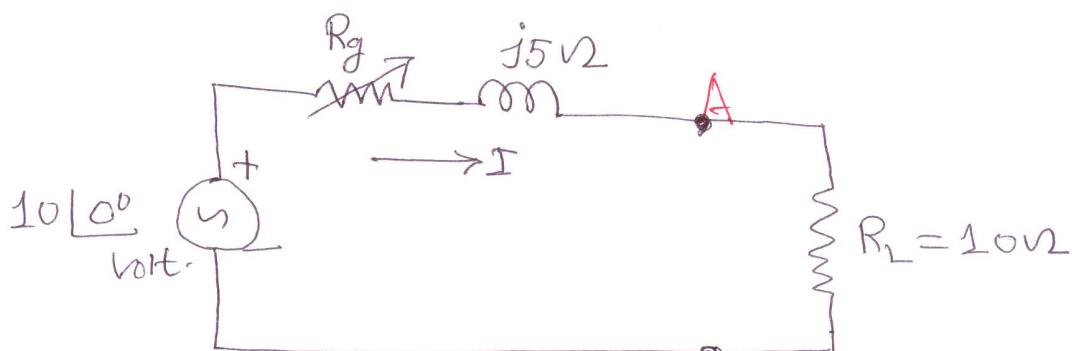Fig. 2

Ex-4:

(38) (b)

In the network shown in Fig. 3, the load connected across terminals AB consists of a variable resistance R_L and a capacitive reactance $-jX_C$ which is variable between 2Ω and 8Ω . Determine the values of R_L and X_C which result in maximum power transfer. Calculate the maximum power P delivered to the load.


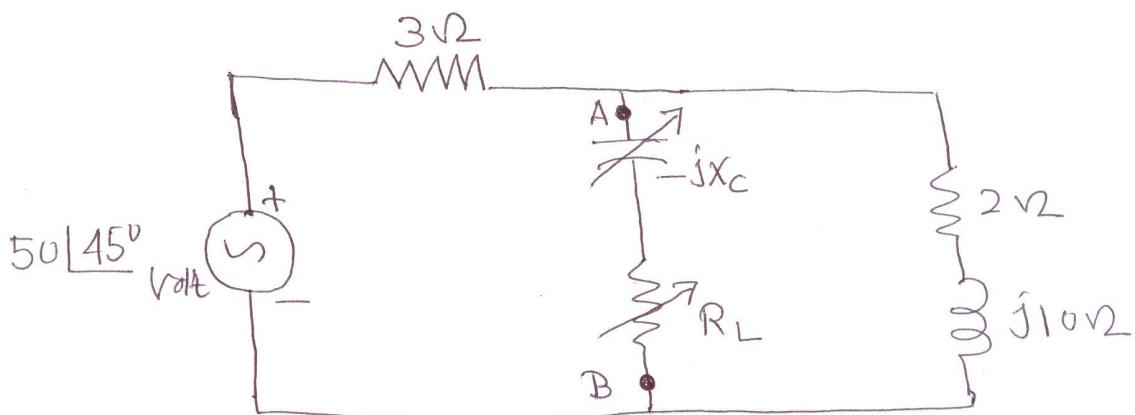


Fig. 3

Soln

$$V_{TH} = V_{AB} = \frac{50\angle 45^\circ}{(5+j10)} (2+j10) \\ = 45.6 [60.3^\circ] \text{ volt.}$$
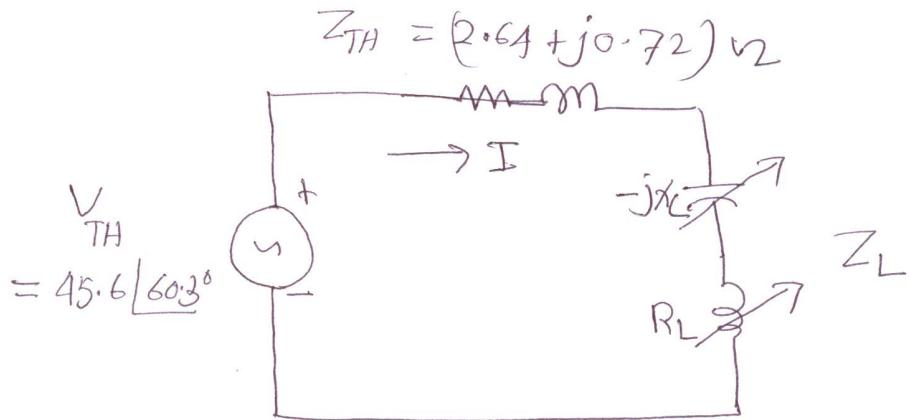
$$Z_{TH} = Z_{AB} = \frac{3 \times (2+j10)}{(5+j10)} = (2.64 + j0.72) \Omega$$



Maximum power transfer occurs,

when $Z_L = Z_{TH}^* = (2.64 - j0.72) \text{ } \Omega$

X_C is adjustable between 2Ω and 8Ω .

Hence the closest value of X_C is 2Ω

and

$$R_L = |Z_g - jX_C| = |2.64 + j0.72 - j2|$$

$$\therefore R_L = |2.64 - j1.28| = 2.93 \text{ } \Omega$$

$$Z_T = Z_{TH} + Z_L = \underline{2.64 + j0.72} + \underline{2.93 - j2}$$

$$\therefore Z_T = 5.57 - j1.28 = 5.7 \angle -13^\circ \text{ } \Omega$$

$$\therefore I = \frac{45.6 \angle 60.3^\circ}{5.7 \angle -13^\circ} = 8 \angle 23.9^\circ \text{ Amp.}$$

$$P = (8)^2 \times 2.93 = 187.5 \text{ Watt.}$$